	Multimeter	theory
I	8.26 A	8 A
l ₁	4.72 A	5 A
l ₂	3.20 A	3 A
I ₃	0.58 A	0.6 A

	Multimeter	theory
I	2.05 A	2 A
V ₁	1.40 V	1.4 V
V ₂	2.04 V	2 V
V ₃	11.50 V	11.5 V