

دانشگاه صنعتی امیر کبیر
(پلی تکنیک تهران)

Electrical and Electronic Circuits

chapter 4. Handy Circuit Analysis Techniques

Afarghadan@aut.ac.ir

عظیم فرقدان 

مهر ۱۴۰۳


Objectives of the Lecture

- Common Circuit Analysis Methods
 - Superposition Theorem
 - Practical Sources
 - Source Transformation
 - Thevenin and Norton Circuits
 - Maximum Power Transfer Theorem
 - Star-Delta Transformation

- A linear circuit element has a linear voltage-current relationship:
 - if $i(t)$ produces $v(t)$, then $Ki(t)$ produces $Kv(t)$
 - if $i_1(t)$ produces $v_1(t)$ and $i_2(t)$ produces $v_2(t)$, then $i_1(t) + i_2(t)$ produces $v_1(t) + v_2(t)$,
- resistors, sources are linear elements
- a linear circuit is one with only linear elements

The Superposition Concept

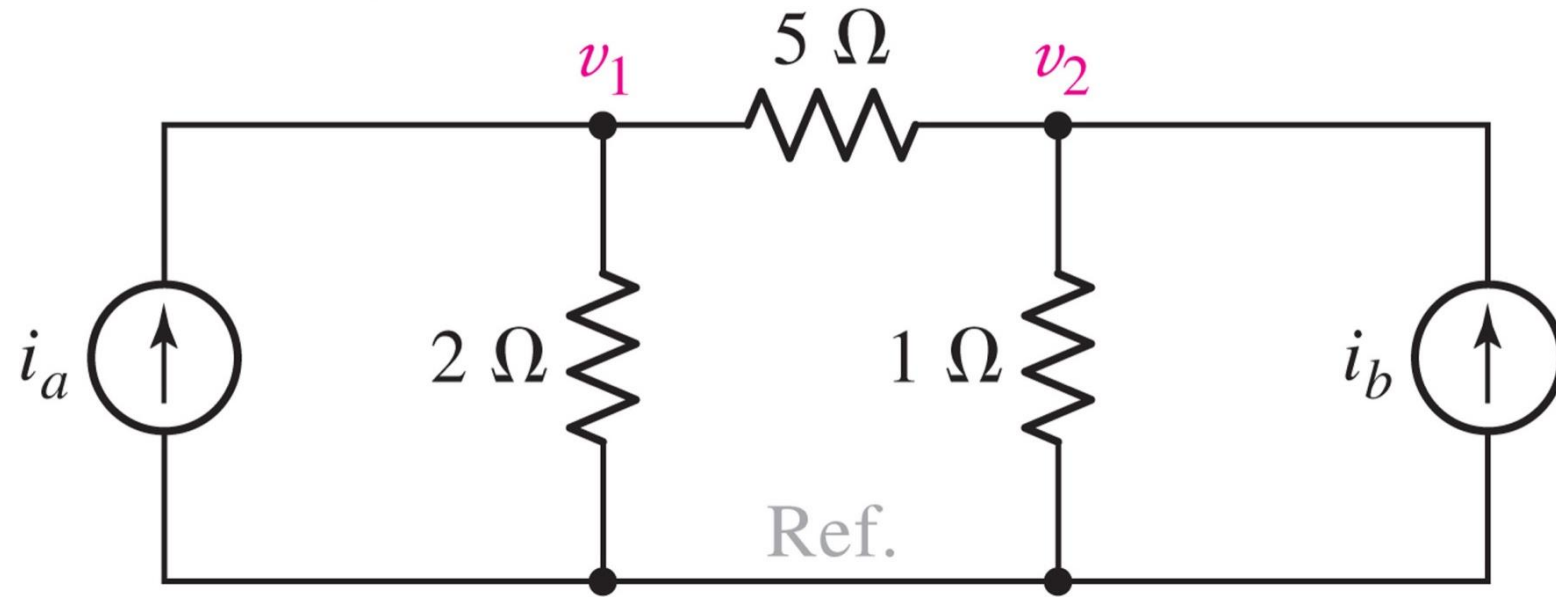For the circuit shown, the solution can be expressed as:



$$\frac{v_1 - v_2}{5} + \frac{v_1}{2} - i_a = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{1} - i_b = 0$$

$$\rightarrow \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 1.2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_a \\ i_b \end{bmatrix}$$


$$\rightarrow A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_a \\ i_b \end{bmatrix} \rightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = A^{-1} \begin{bmatrix} i_a \\ i_b \end{bmatrix}$$

Question: How much of v_1 is due to source i_a , and how much is because of source i_b ?

The Superposition Concept

If we define A as
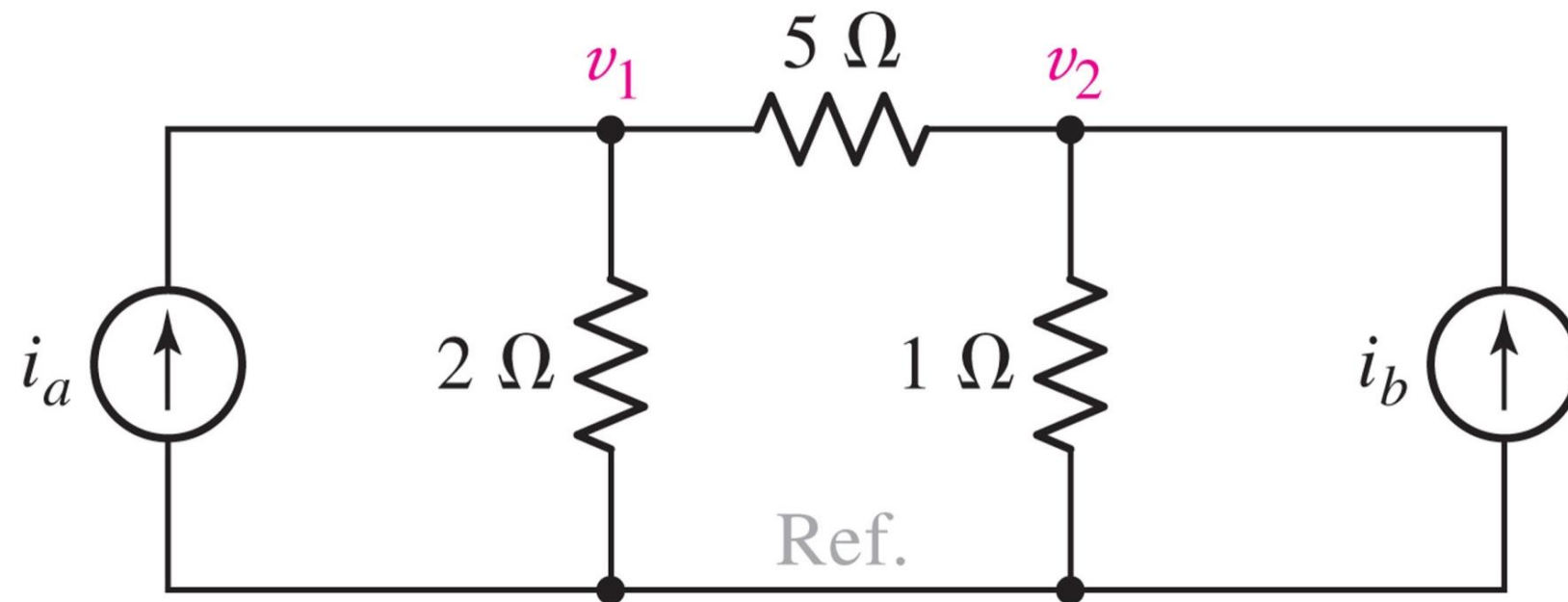
$$A = \begin{bmatrix} 0.7 & -0.2 \\ -0.2 & 1.2 \end{bmatrix}$$



then

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = A^{-1} \begin{bmatrix} i_a \\ i_b \end{bmatrix} = \underbrace{A^{-1} \begin{bmatrix} 0 \\ i_b \end{bmatrix}}_{\text{Experiment 1}} + \underbrace{A^{-1} \begin{bmatrix} i_a \\ 0 \end{bmatrix}}_{\text{Experiment 2}}$$

Superposition:
the response is the sum of
experiments 1 and 2.

The Superposition Theorem

In a linear network, the **voltage across** or the **current through** any element may be calculated by *adding algebraically* all the individual voltages or currents caused by the separate **independent sources** acting “alone”.

In other words, the effect that each independent source has on the circuit parameters is **mutually independent**, and the combined result of their effects is the algebraic sum of their contributions.

Applying Superposition

- Leave **one source ON** and turn all other sources **OFF**:

–voltage sources: *set $v=0$* .

These become *short circuits*.


–current sources: *set $i=0$* .

These become *open circuits*.


Find the response from this source.

- Add the resulting responses

to find the total response.


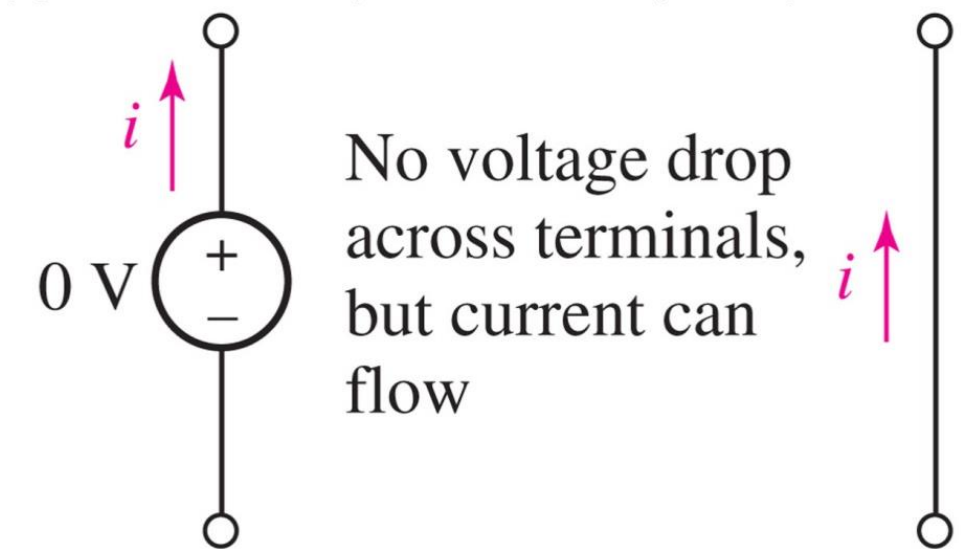


(a)

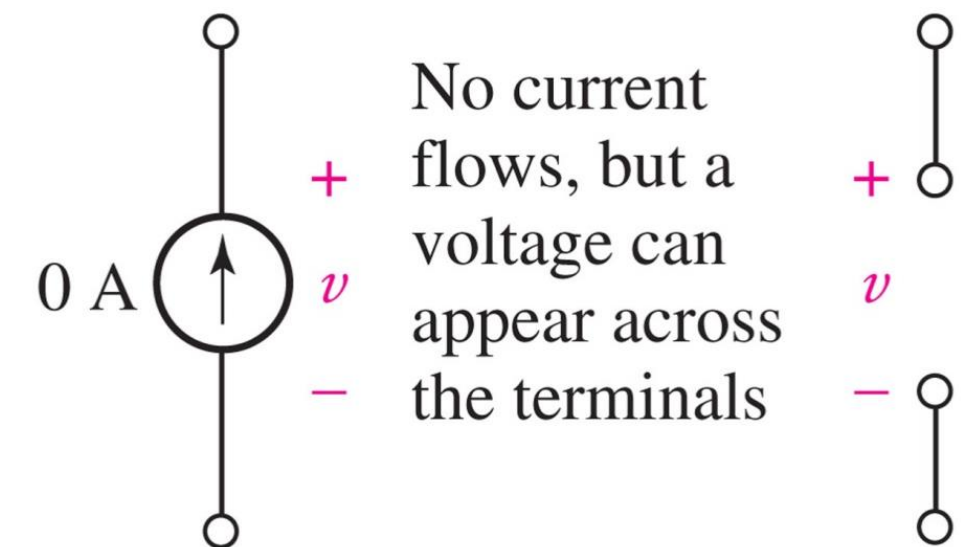


The Superposition Theorem

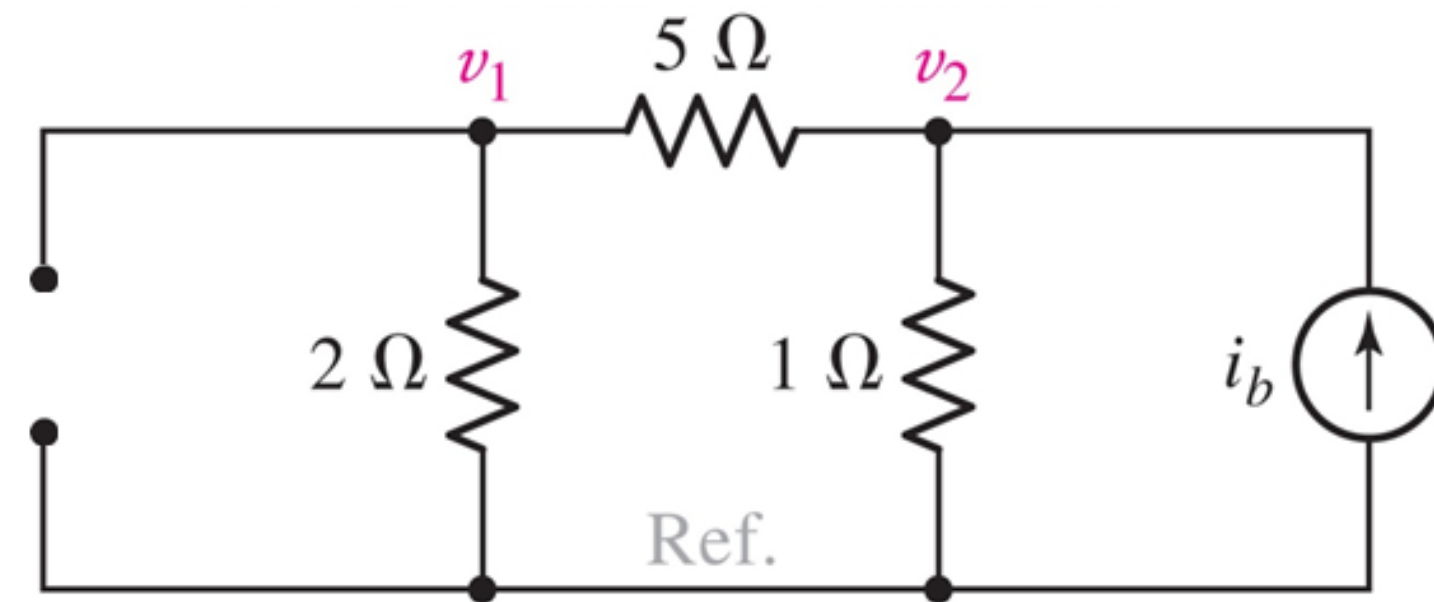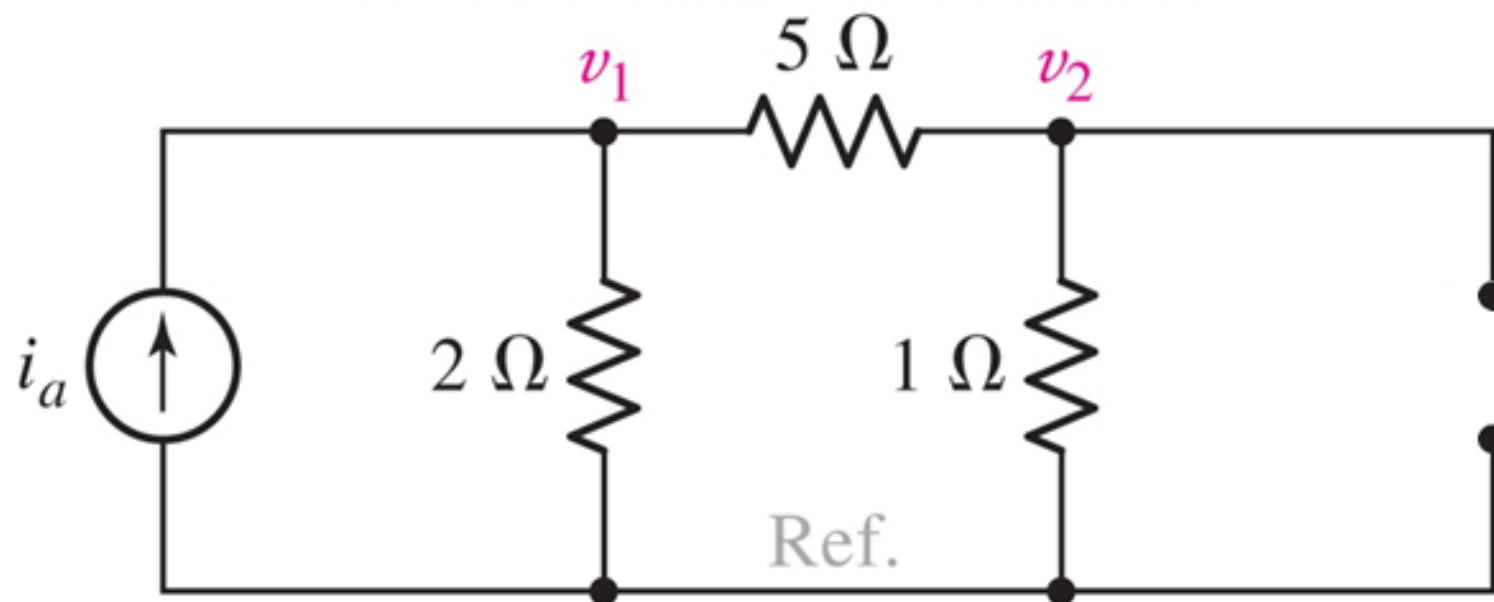- ✓ all other independent **voltage sources** replaced by **short circuits** and
- ✓ all other independent **current sources** replaced by **open circuits**.




Superposition Example (part 1 of 4)

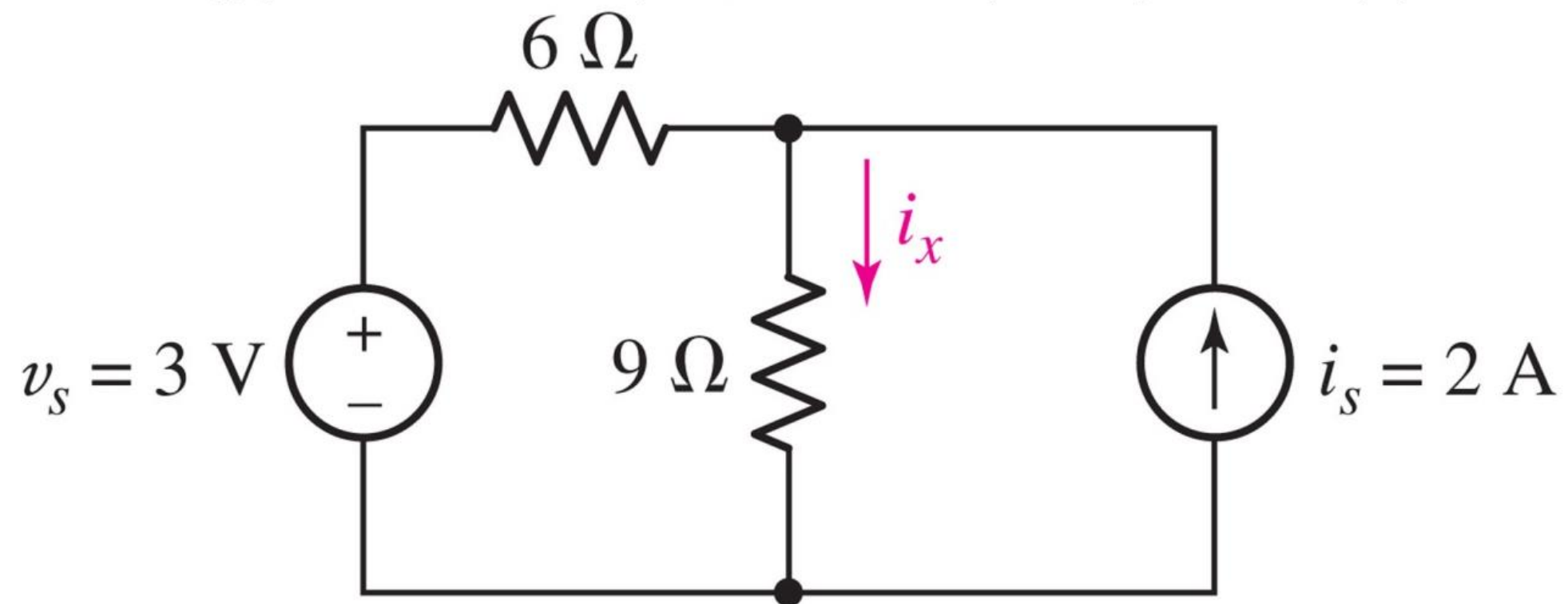Use superposition to solve for the current i_x




Superposition Example (part 2 of 4)

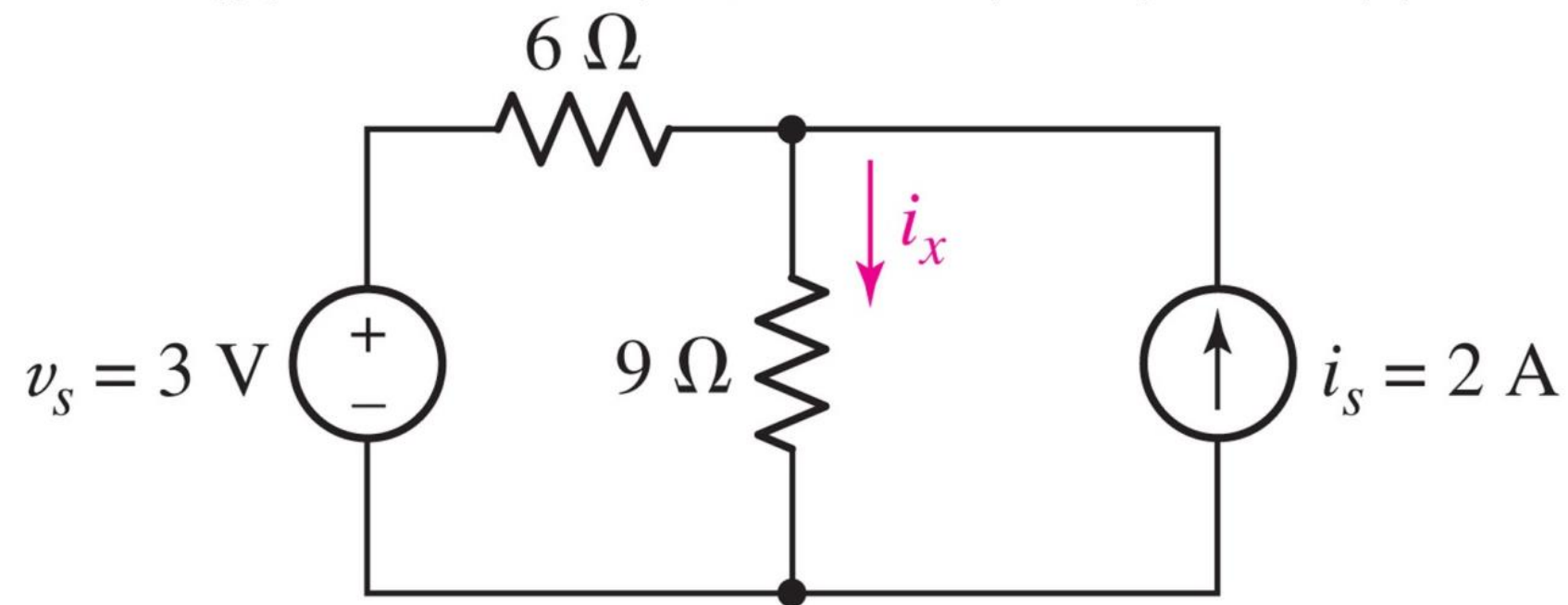


First, turn the current source off:

$$i'_x = \frac{3}{6+9} = 0.2$$

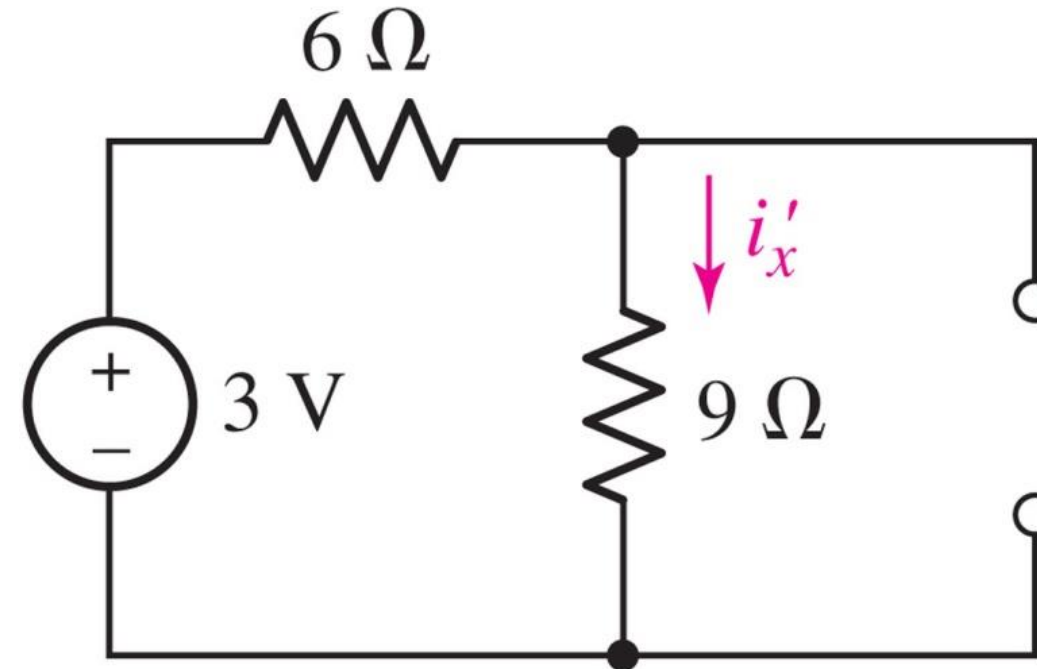


Superposition Example (part 1 of 4)

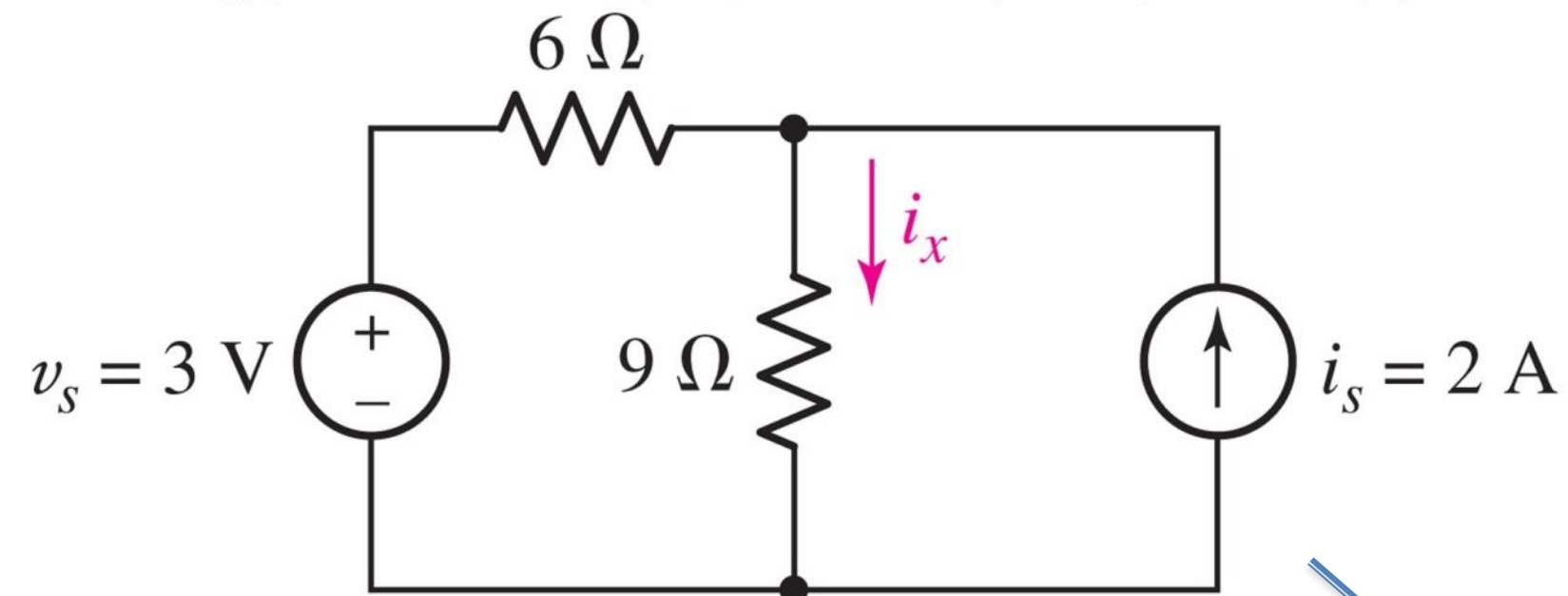


Then, turn the voltage source off:

$$i_x'' = \frac{6}{6+9}(2) = 0.8$$

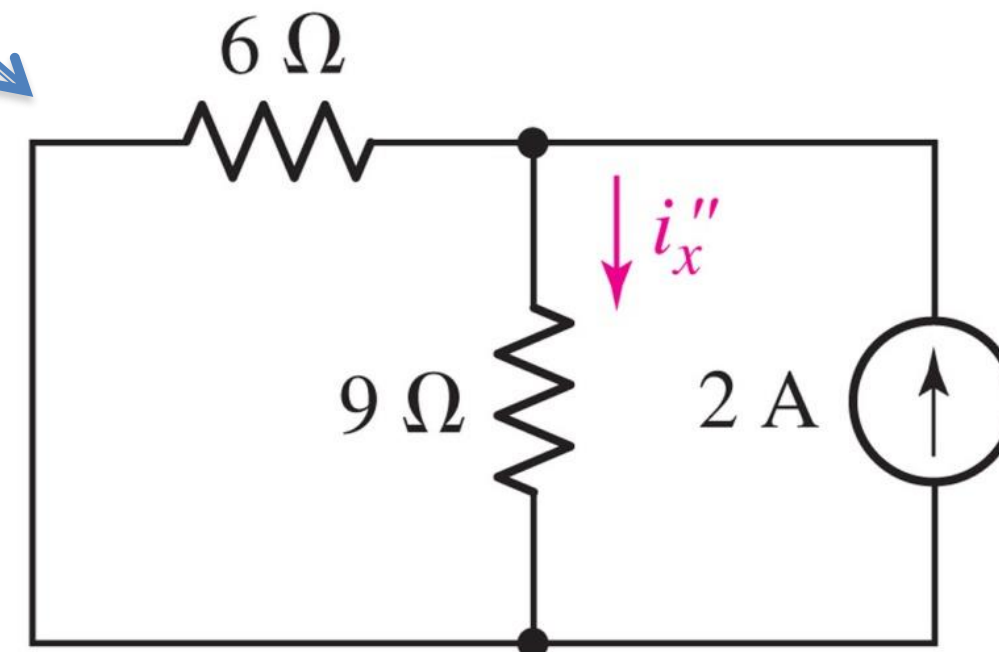

Superposition Example (part 1 of 4)

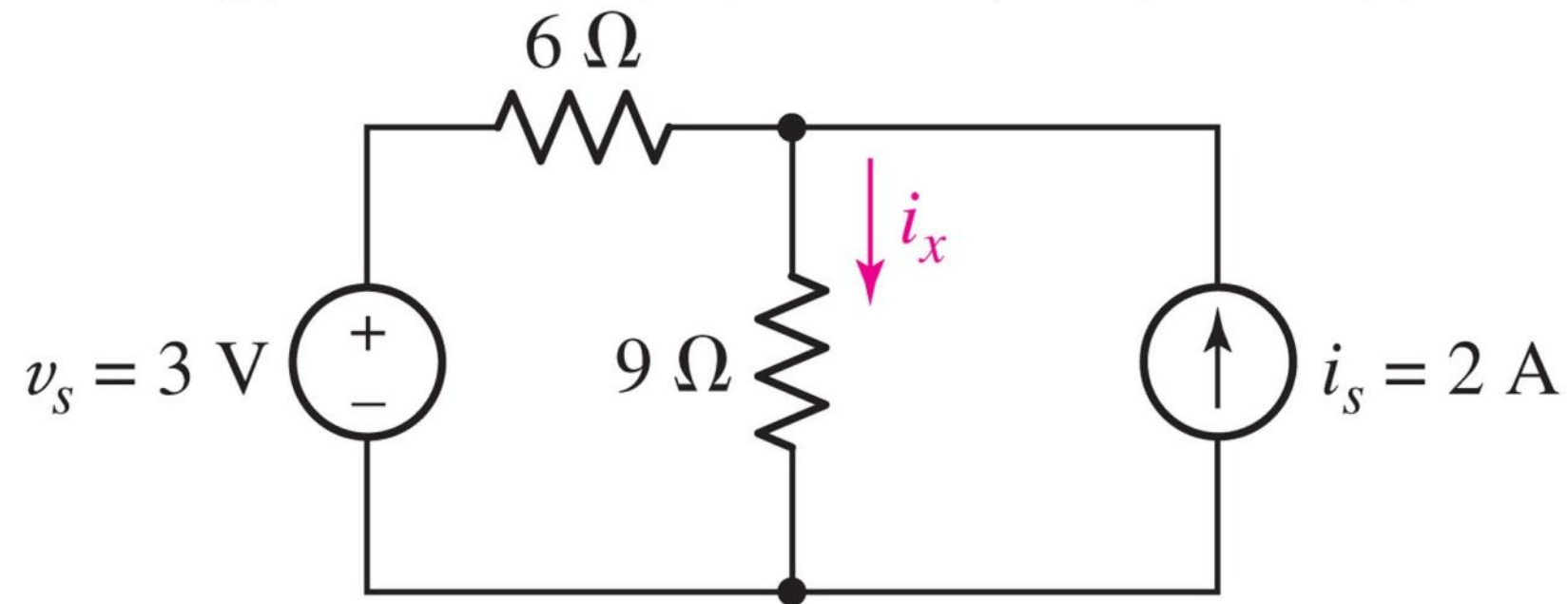


Finally, combine the results:

$$i_x = i_x' + i_x'' = 0.2 + 0.8 = 1.0$$

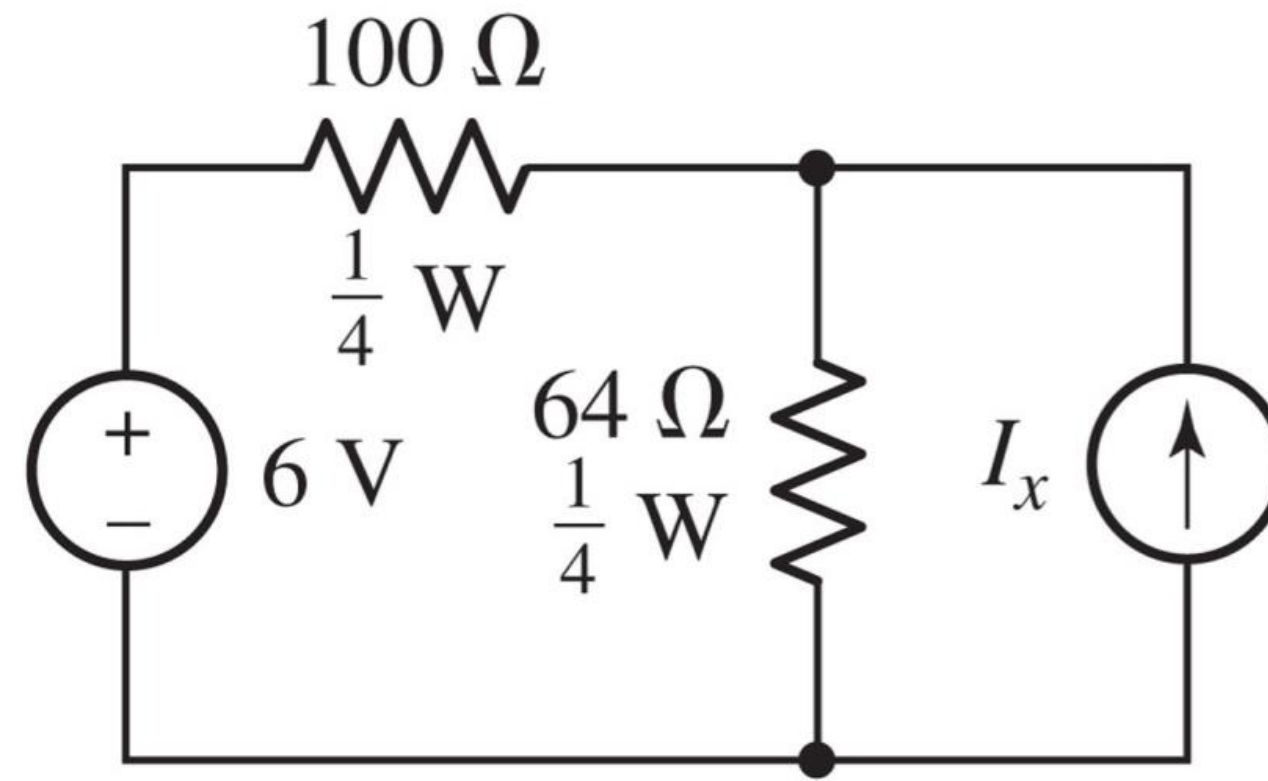Example: Power Ratings

Determine the maximum *positive* current to which the source I_x can be set before any resistor exceeds its power rating.



Answer: $I_x < 42.49 \text{ mA}$

Example: Power Ratings

Maximum current magnitude in 100Ω resistor is $\sqrt{0.25 / 100} = 50\text{mA}$

Maximum current magnitude in 64Ω resistor is $\sqrt{0.25 / 64} = 62.5\text{mA}$

Current from voltage source alone is $6/164 = 36.6\text{mA}$ flowing clockwise

Current in 100Ω from I_x alone is $\frac{64}{164} I_x$ flowing to the left.

$$\text{Therefore } \left| 0.0366 - \frac{64}{164} I_x \right| < 0.05 \text{ or } -0.05 < 0.0366 - \frac{64}{164} I_x < 0.05$$

$$221.9\text{mA} > I_x > -34.33\text{mA}$$


Current in 64Ω from I_x is $\frac{100}{164} I_x$ flowing downward.

$$\text{Therefore } \left| 0.0366 + \frac{100}{164} I_x \right| < 0.0625 \text{ or } -0.0625 < 0.0366 + \frac{100}{164} I_x < 0.0625$$


$$-0.1625 < I_x < 0.04247$$

Superposition with a Dependent Source

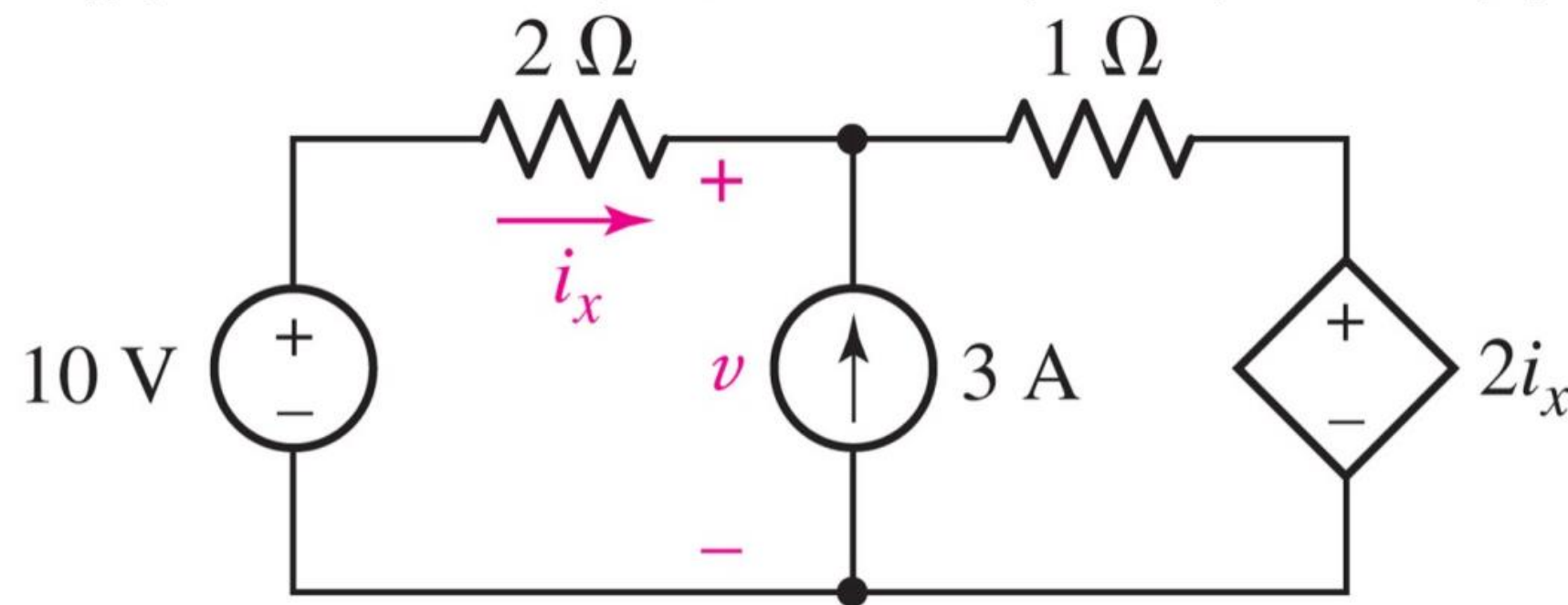
When applying superposition to circuits with *dependent* sources, *these dependent sources are never “turned off.”*




Superposition with a Dependent Source

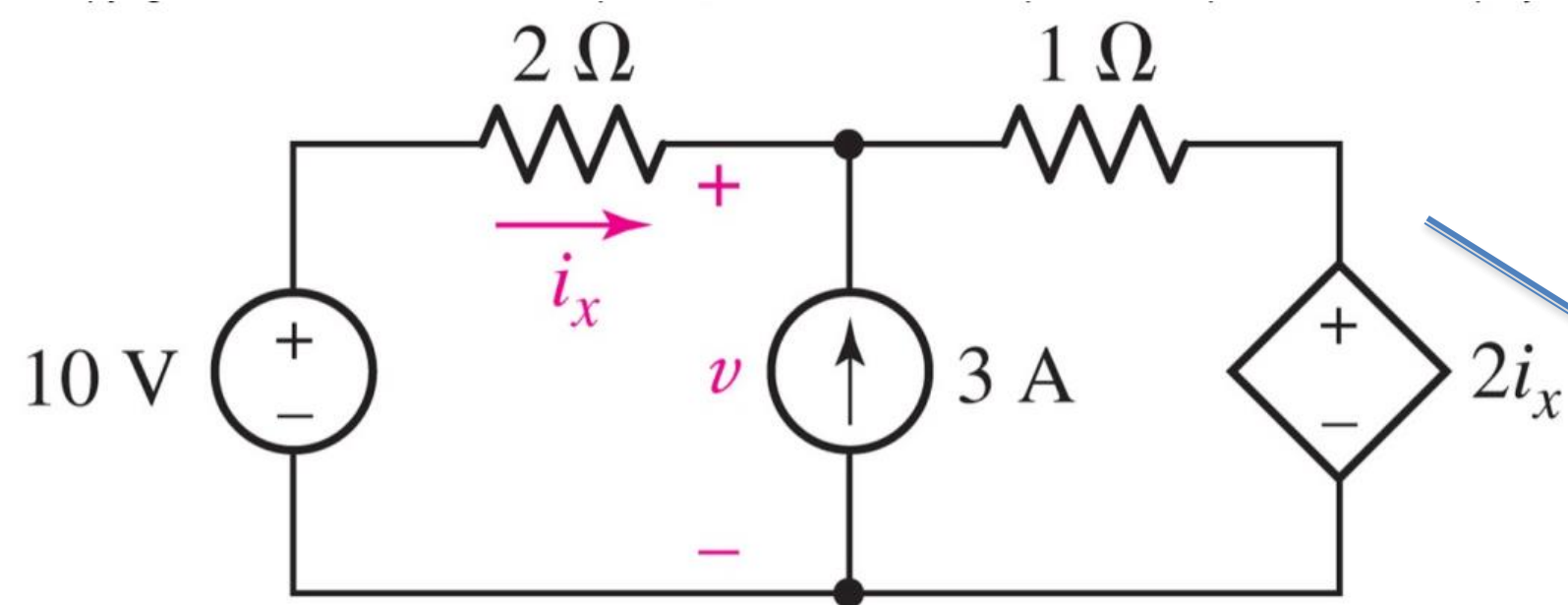

current source off

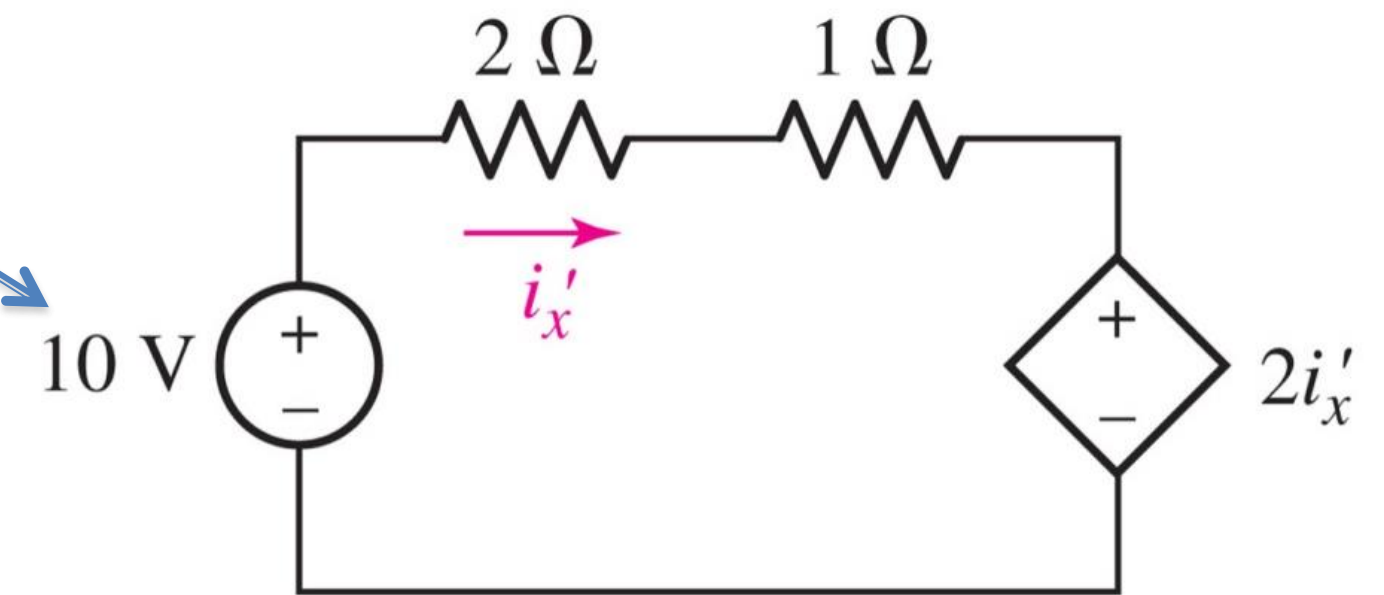


voltage source off

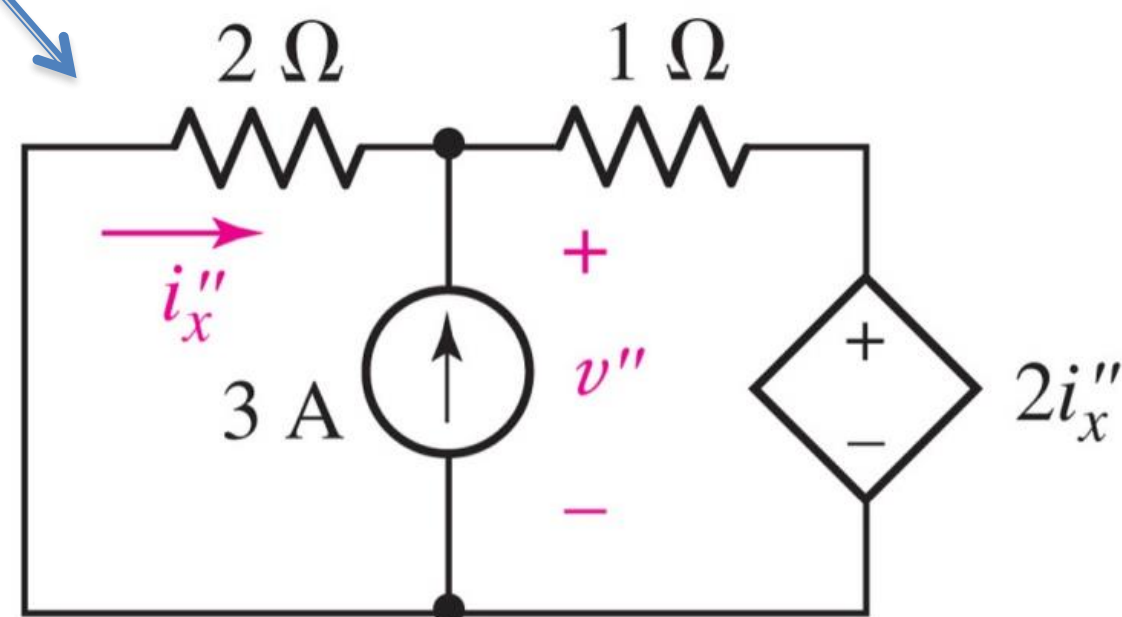


$$i_x = i'_x + i''_x = 2 + (-0.6) = 1.4 \text{ A}$$

Practical Voltage Sources

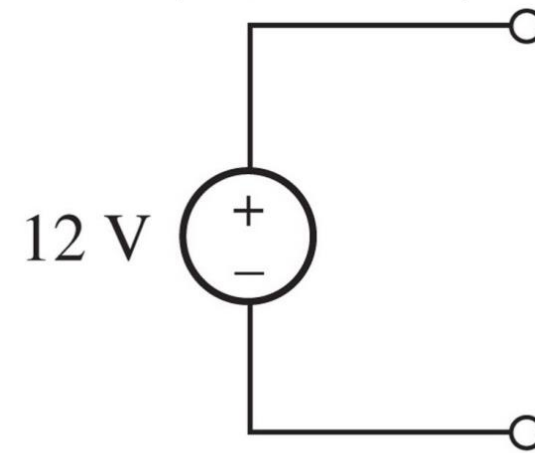- Ideal voltage sources: a first approximation model for a battery.




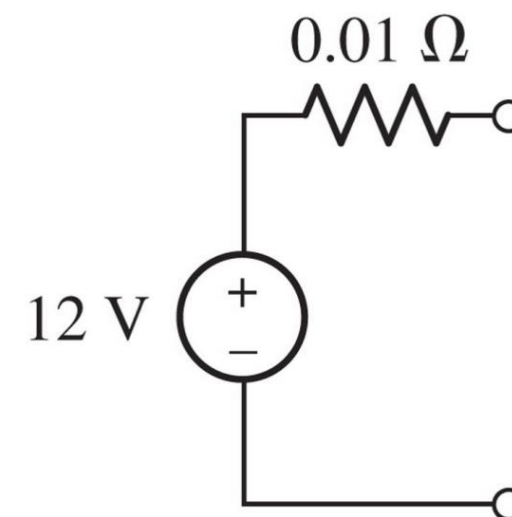
- Why do **real batteries** have a **current limit** and experience **voltage drop** as **current increases**?



Practical Source: Effect of Connecting a Load

For the car battery example:


$$V_L = 12 - 0.01 I_L$$

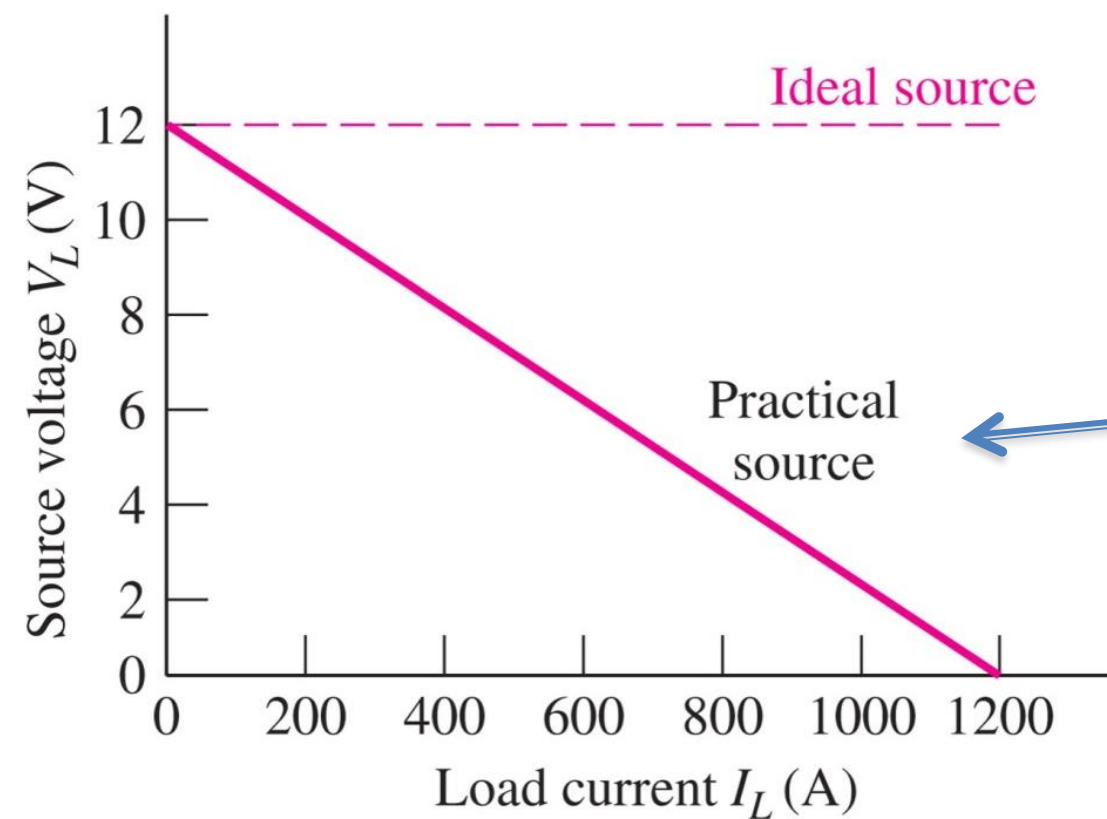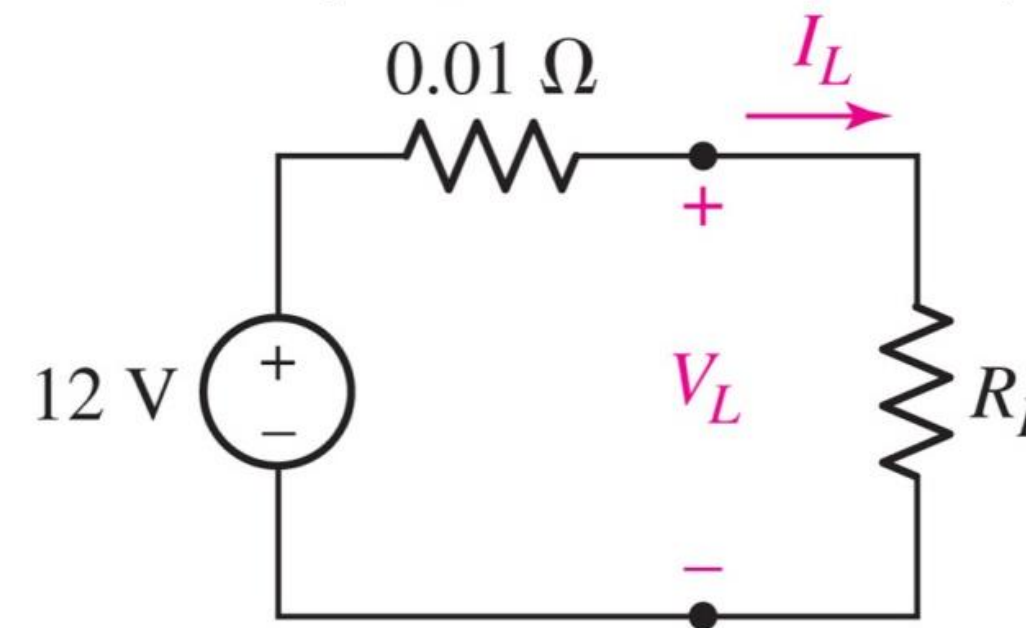


This line represents all possible R_L

Practical Voltage Source

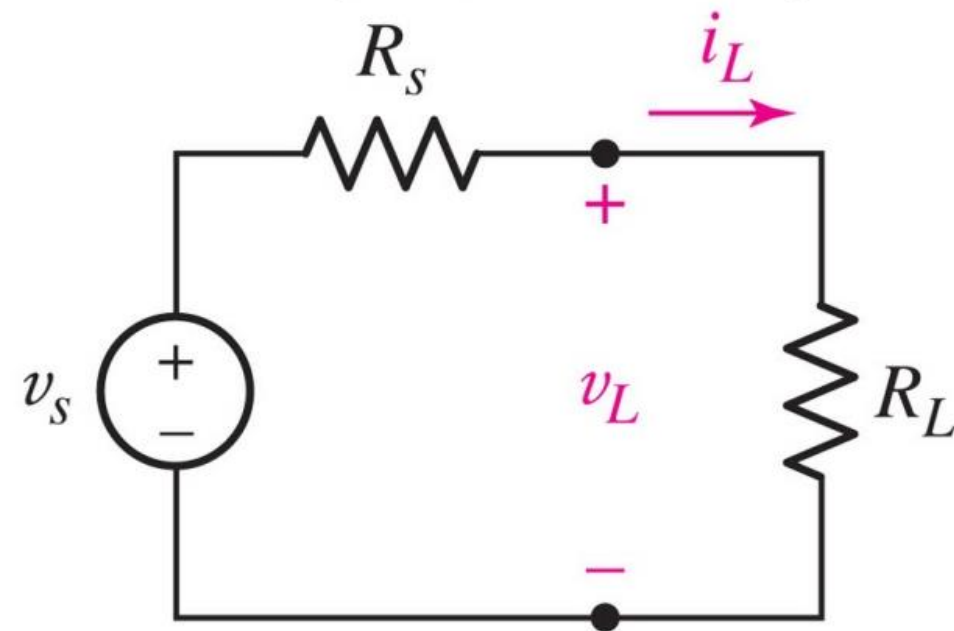The source has an internal resistance or output resistance, which is modeled as R_s




short circuit current (when $R_L=0$)

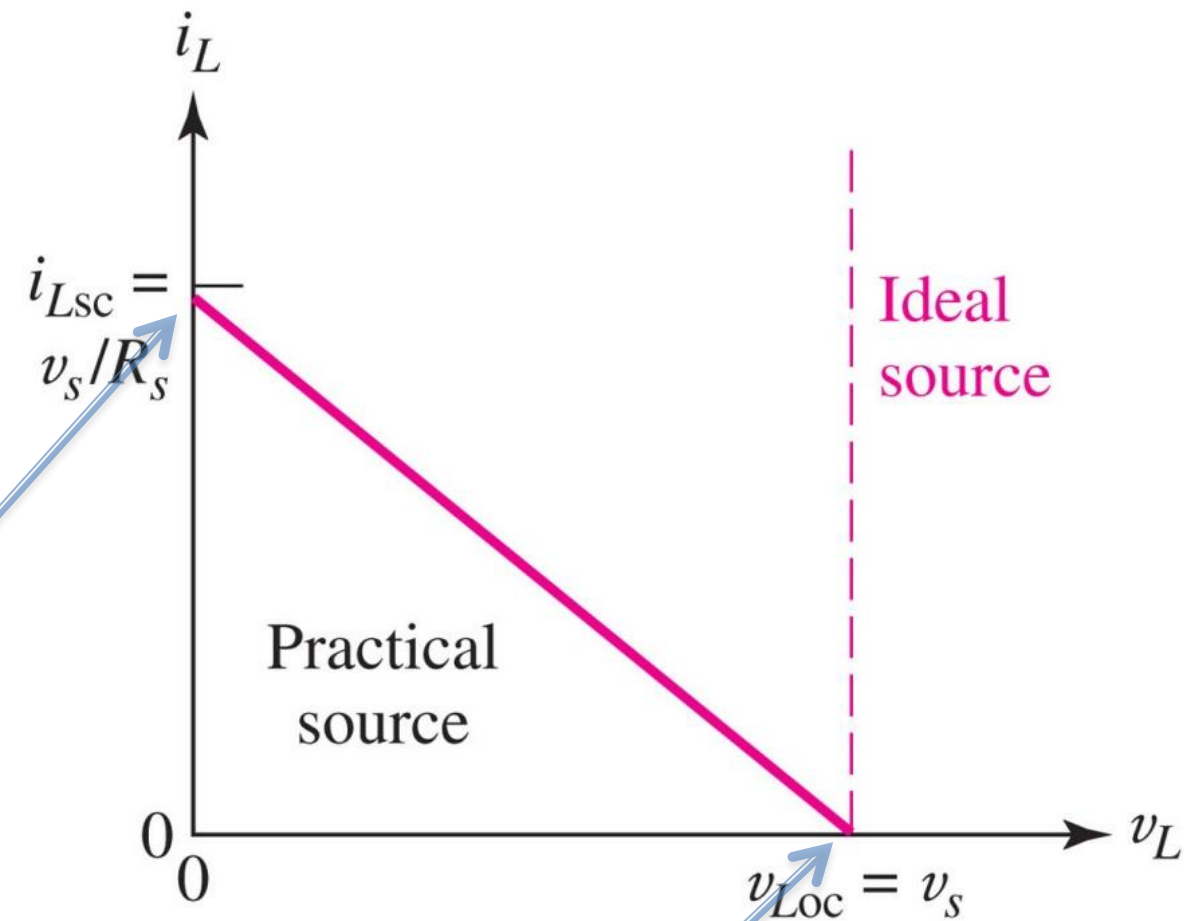


open circuit voltage (when $R_L=\infty$)

Practical Voltage Source

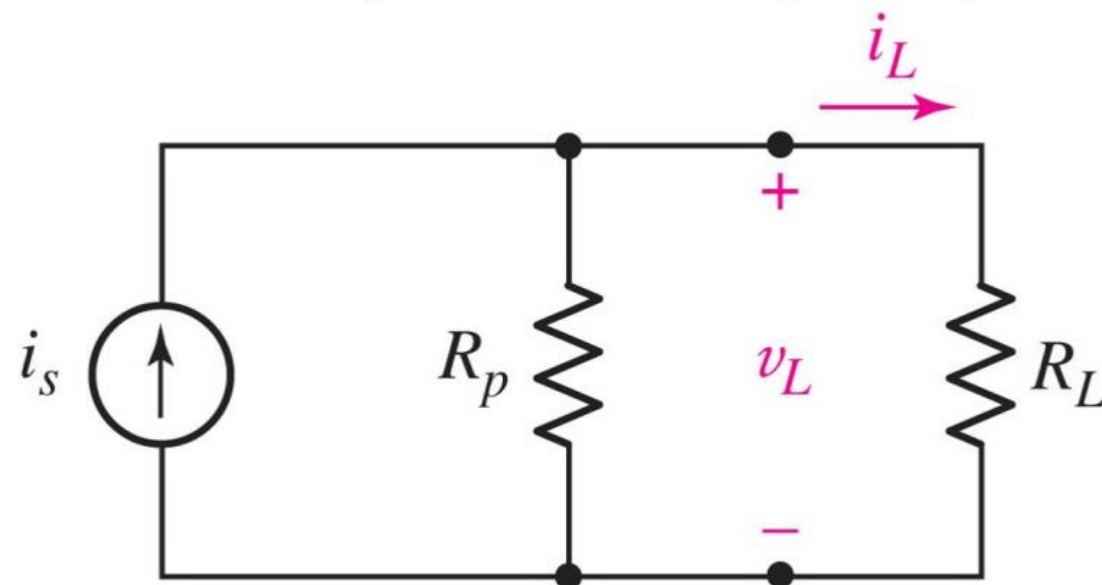The source has an internal *parallel* resistance which is modeled as R_p





short circuit current (when $R_L=0$)

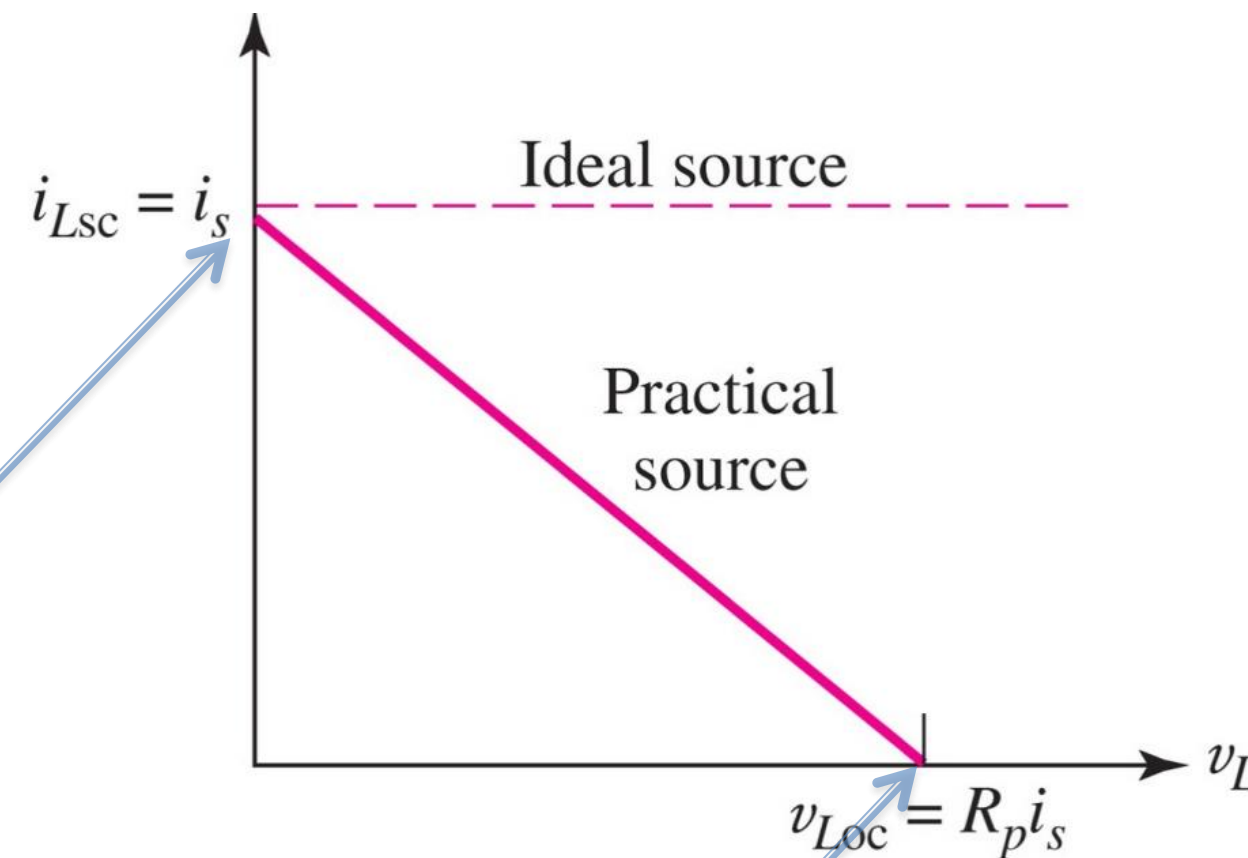

open circuit voltage (when $R_L=\infty$)

The sources are equivalent if



$$R_s = R_p \text{ and } v_s = i_s R_s$$

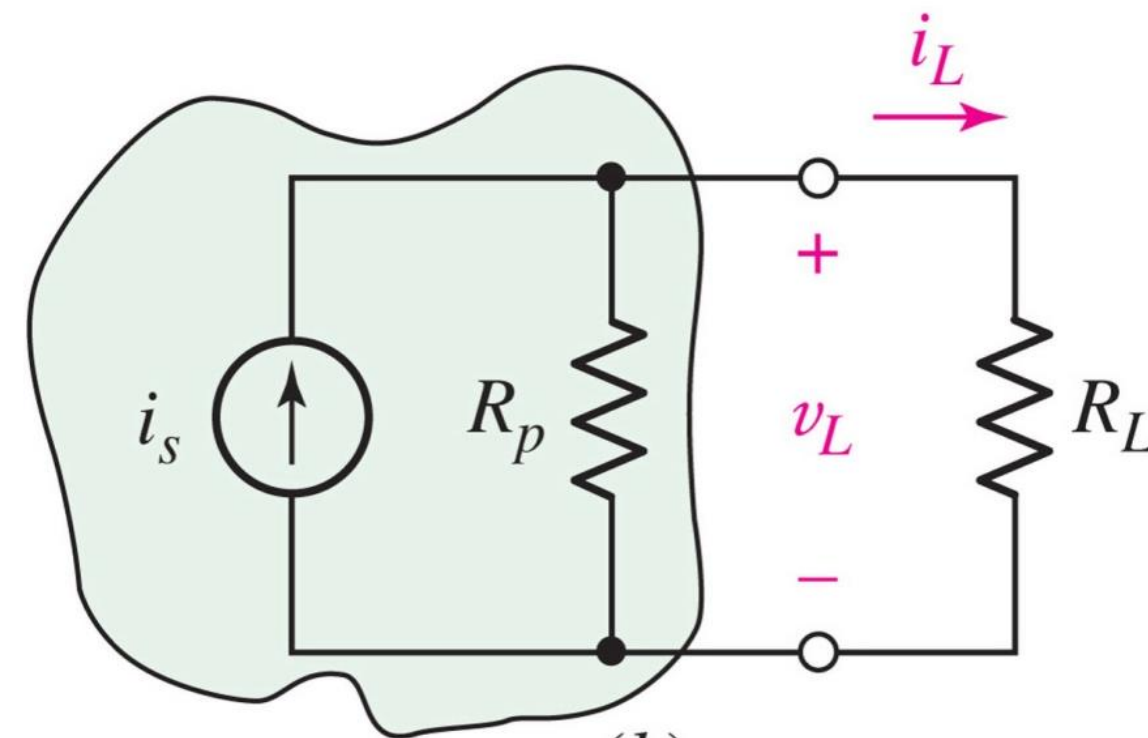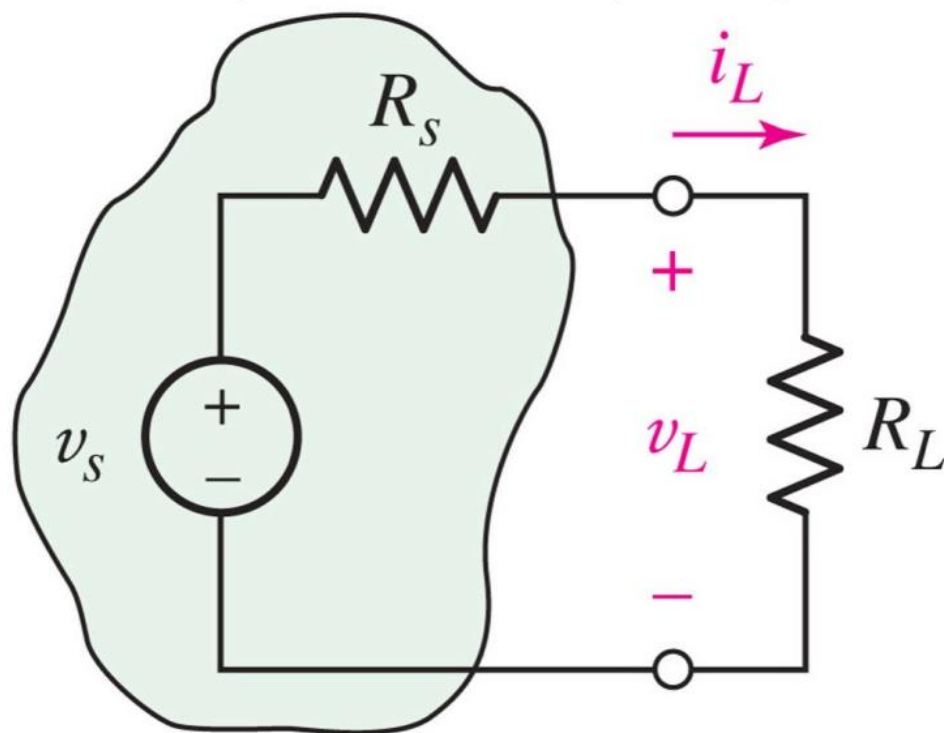

Source Transformation


- The circuits (a) and (b) are equivalent at the terminals.
- If given circuit (a), but circuit (b) is more convenient, switch them!
- This process is called

source transformation.

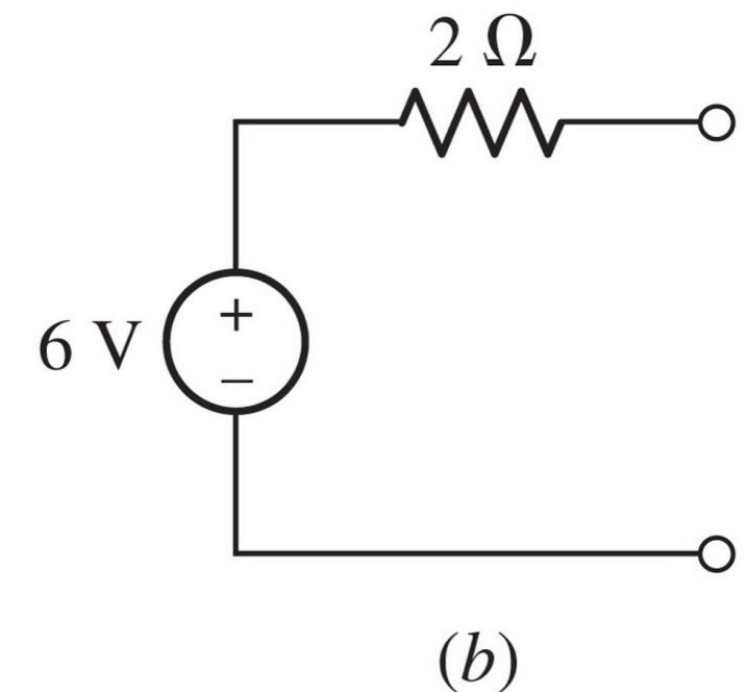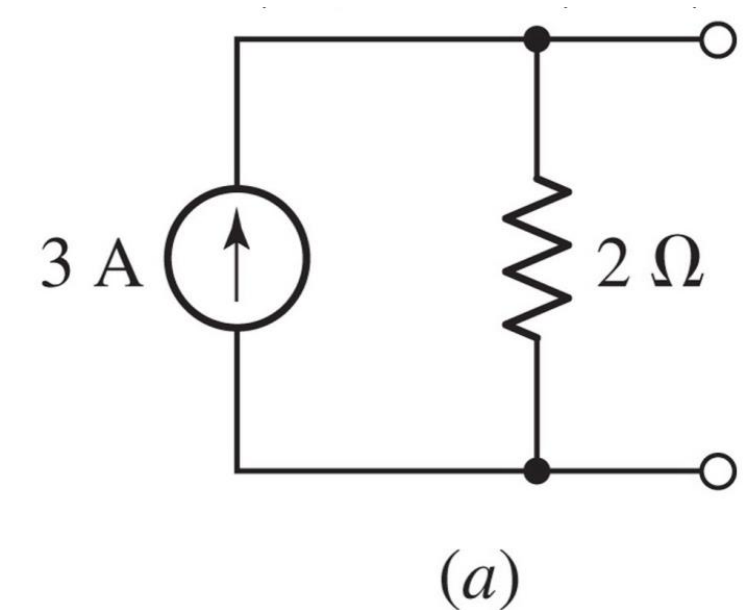

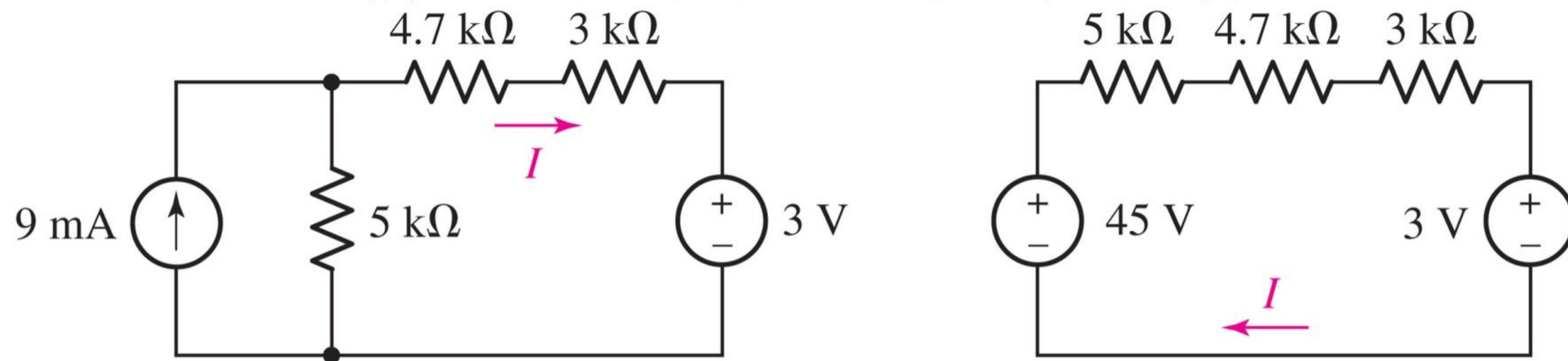Example: Source Transformation


We can find the current I in the circuit below using source transformation, as shown.



$$I = (45 - 3) / (5 + 4.7 + 3) = 3.307 \text{ mA}$$






Thévenin Equivalent Circuits

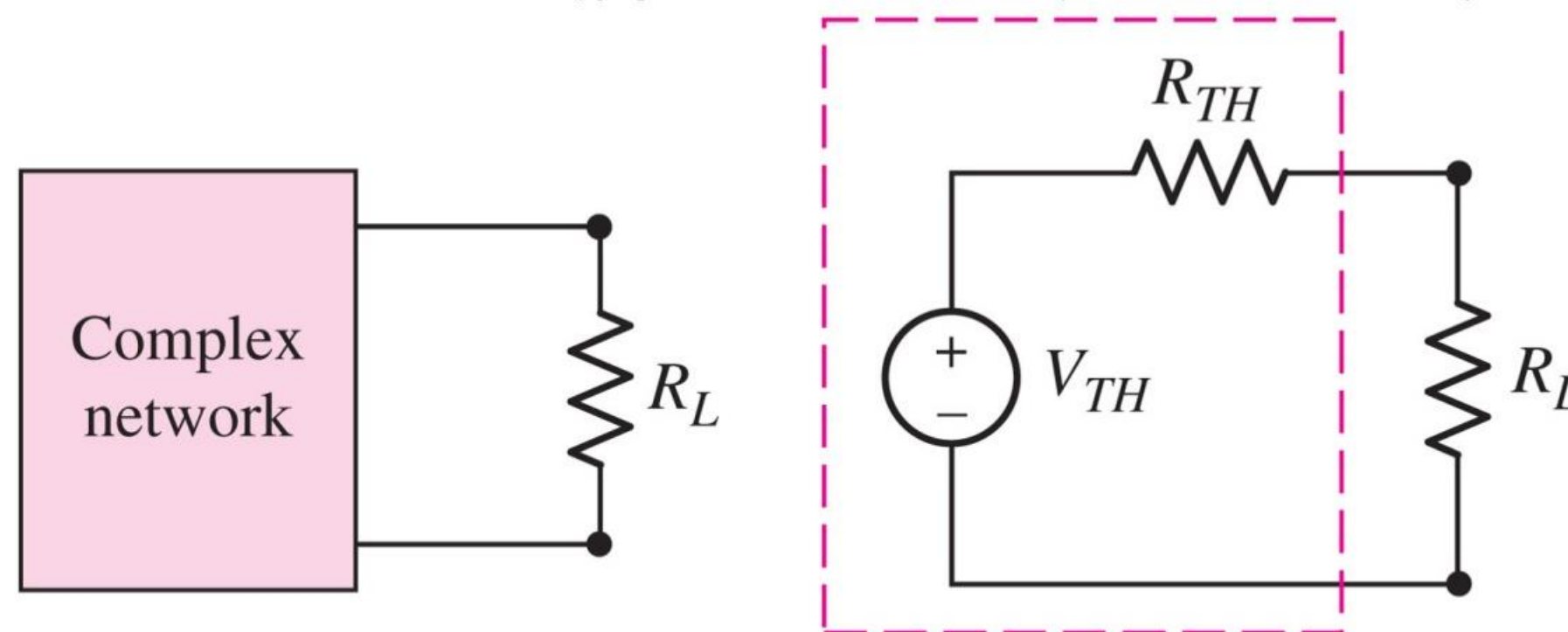- ✓ Thévenin's theorem: a linear network can be replaced by its Thévenin equivalent circuit, In such a way that the current and voltage of the resistor R_L remain unchanged.
- ✓ This new circuit is called the Thevenin equivalent circuit. V_{TH} is referred to as the Thevenin voltage, and R_{TH} as the Thevenin resistance.



Thévenin Equivalent using Source Transformation

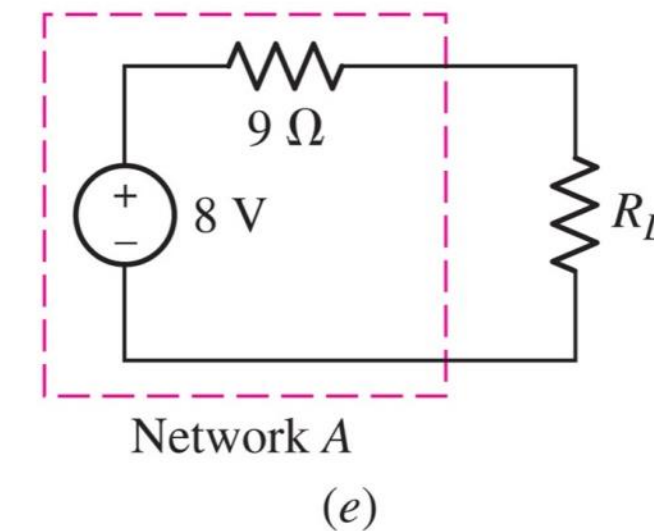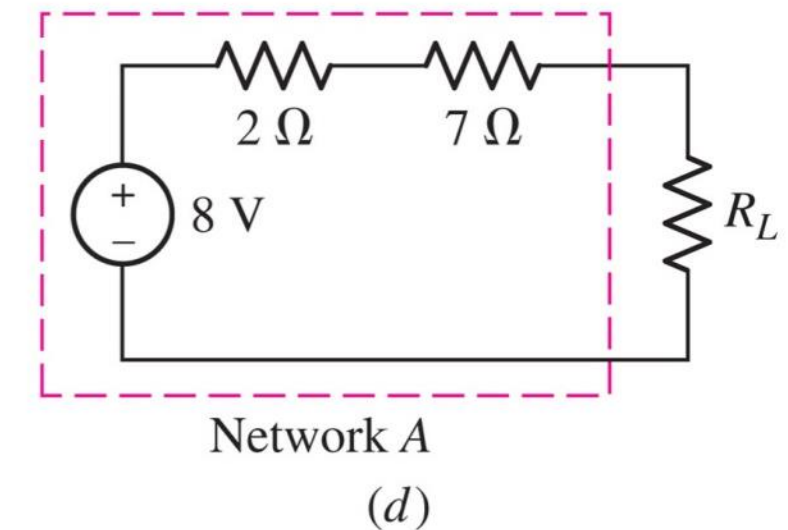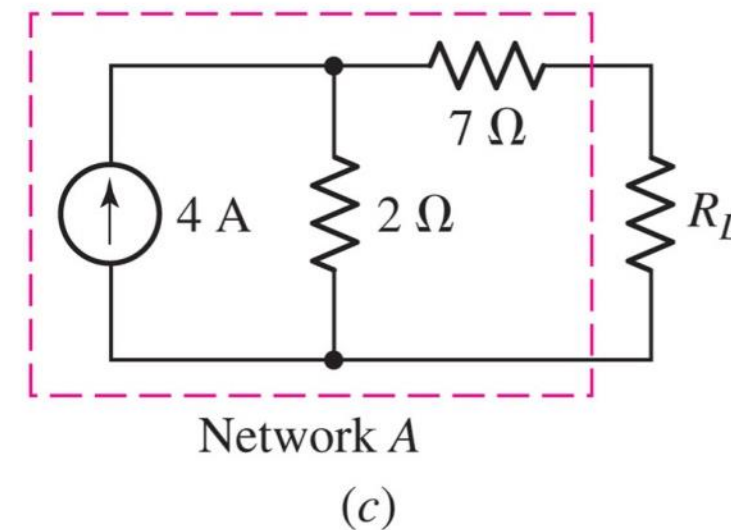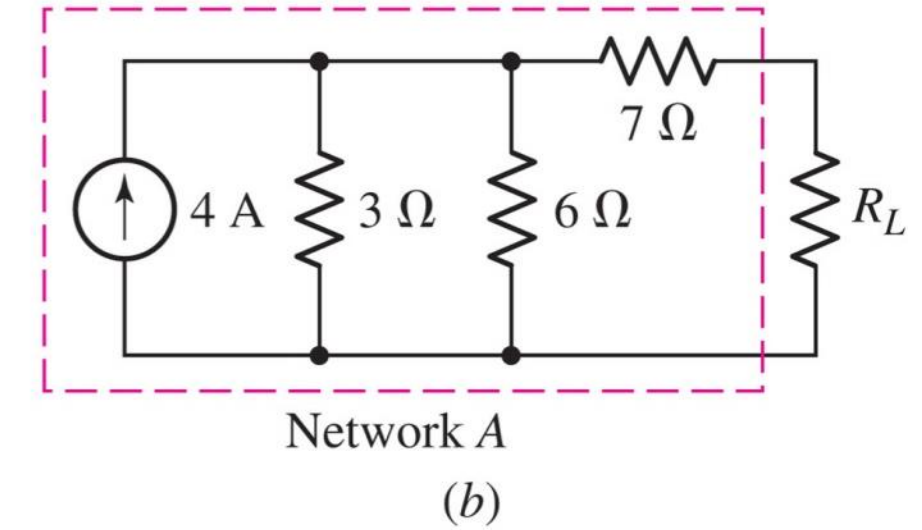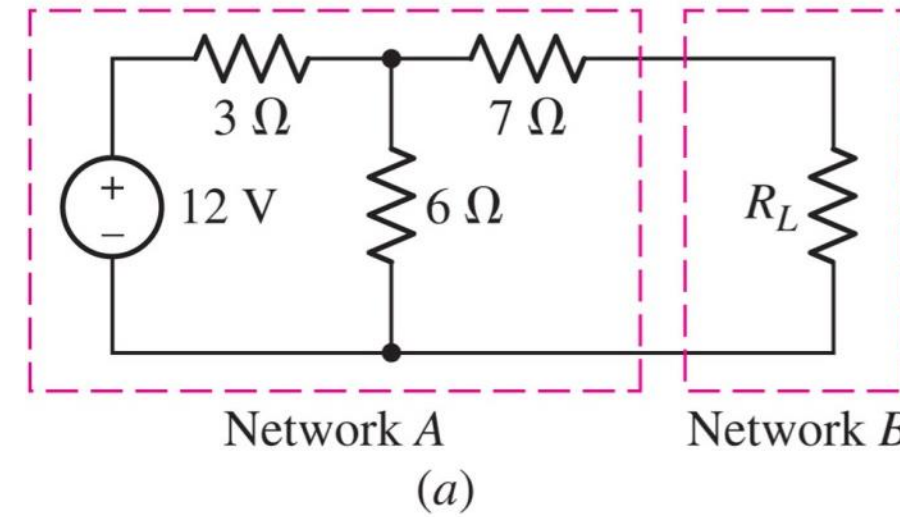- We can repeatedly **apply source transformation** on network A to find its **Thévenin** equivalent circuit.
- This method has **limitations**- not all circuits can be source transformed.




Finding the Thévenin Equivalent

- Disconnect the load.
- Find the open circuit voltage v_{oc}
- Find the equivalent resistance R_{eq} of the network with **all independent sources turned off**.





Then:

$$V_{TH} = v_{oc} \text{ and}$$

$$R_{TH} = R_{eq}$$


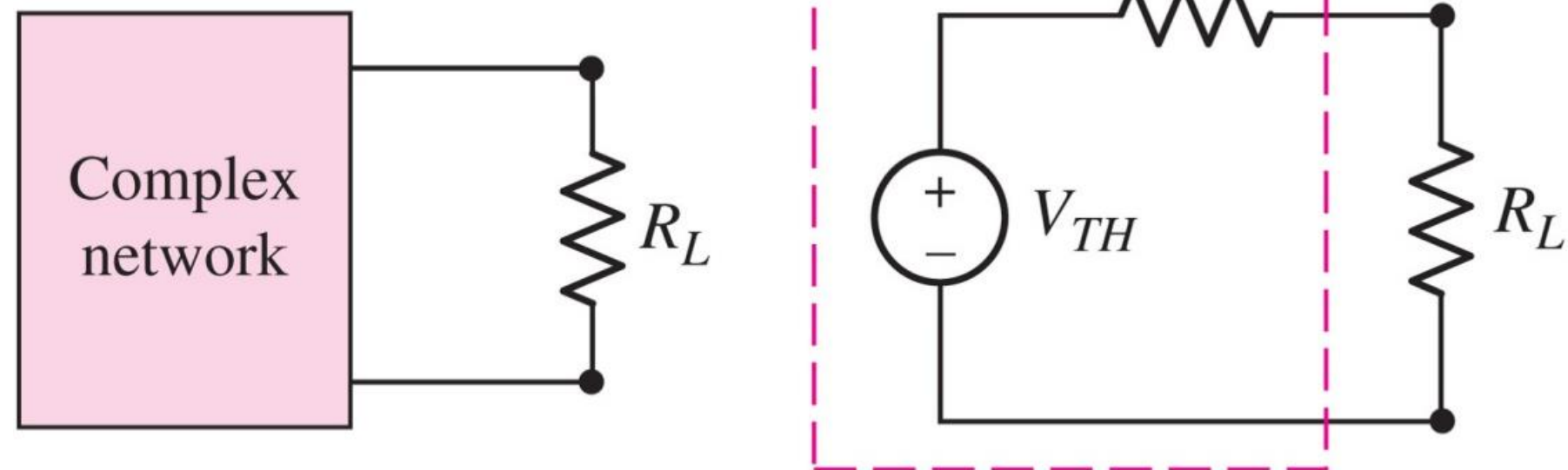


Thévenin Example

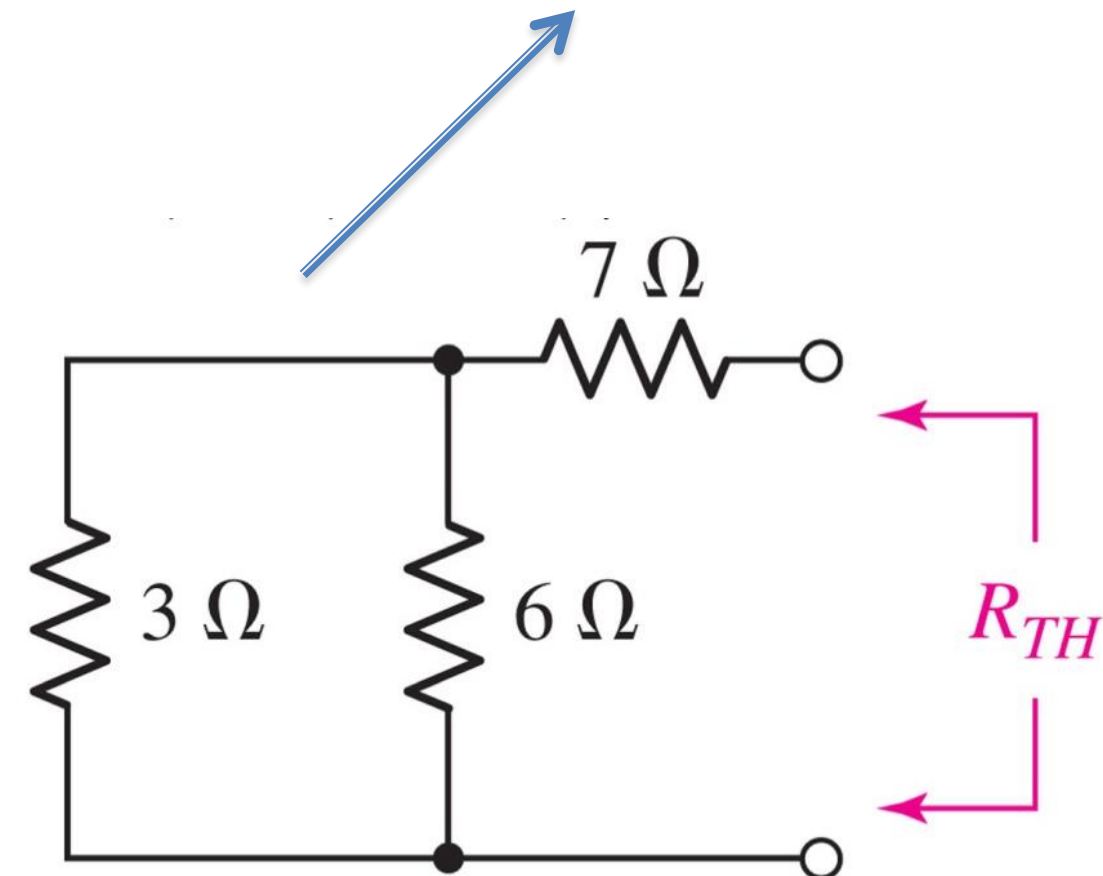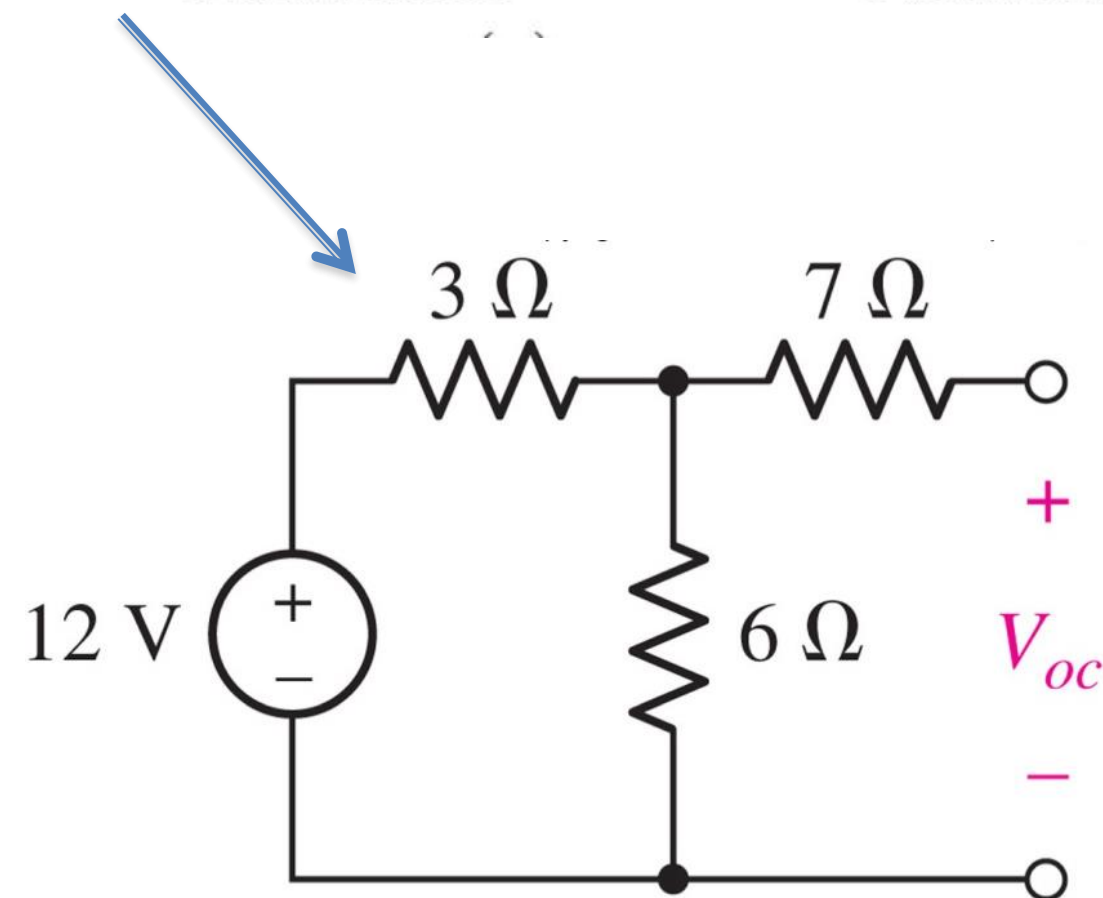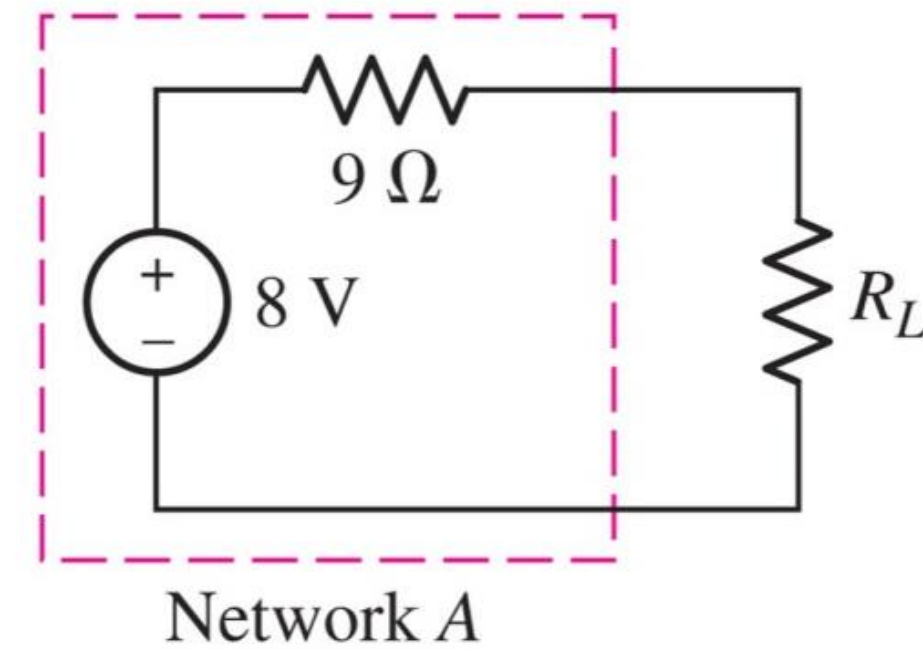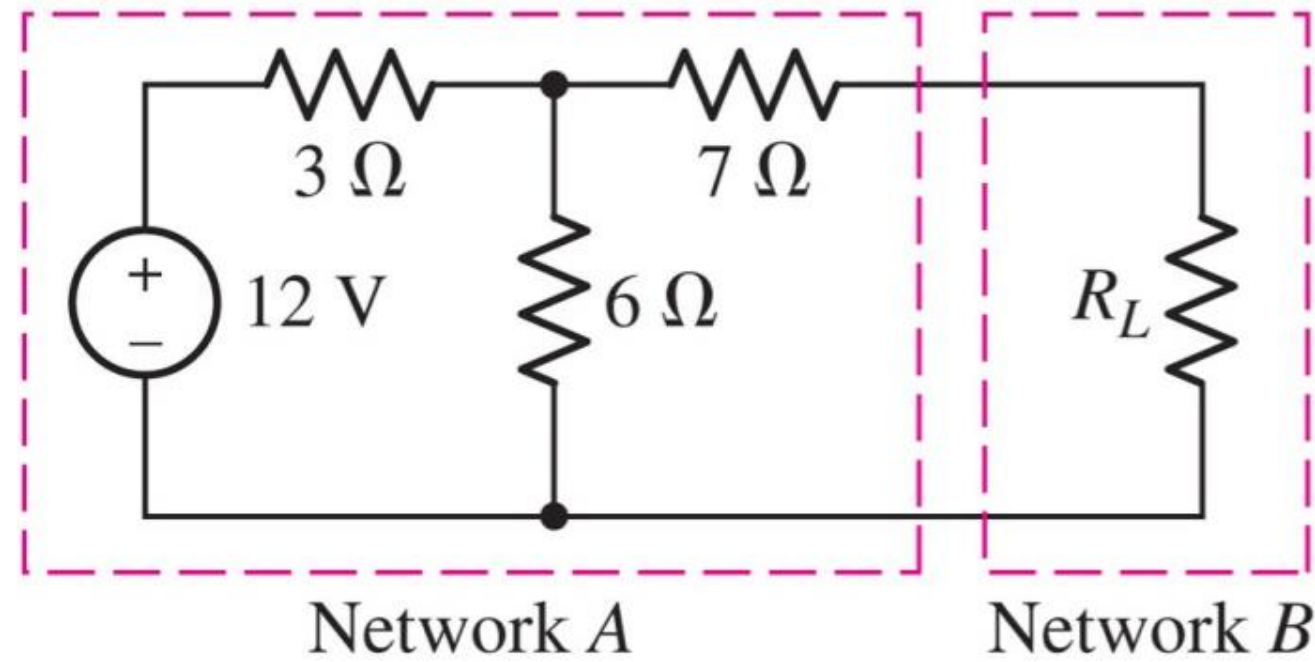

Norton Equivalent Circuits

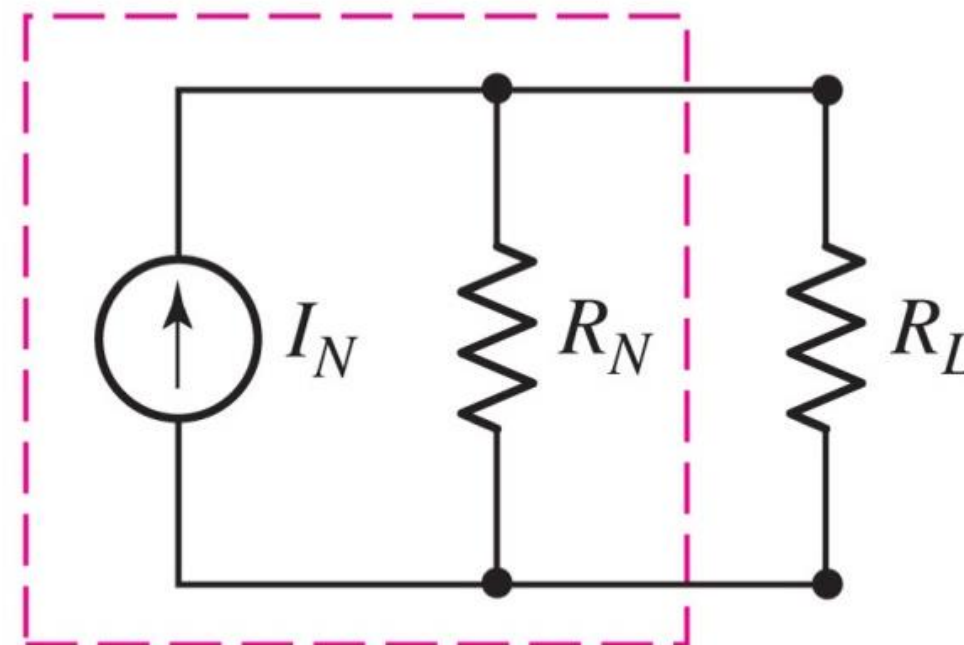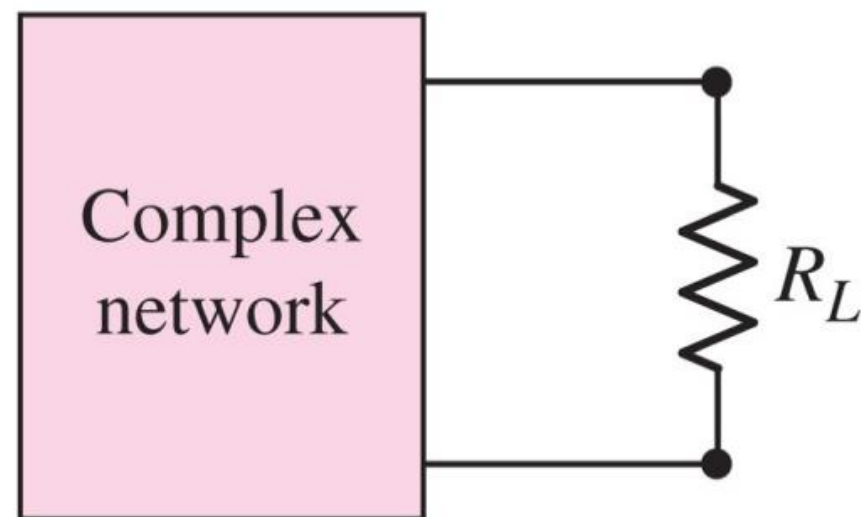- ✓ Norton's theorem: a linear network can be replaced by its Norton equivalent circuit, in such a way that the current and voltage of the resistor R_L remain unchanged.
- ✓ This new circuit is called the Norton equivalent circuit. I_N is referred to as the Norton current, and R_N as the Norton resistance.





Finding the Norton Equivalent


- Replace the load with a **short circuit**.
- Find the **short circuit current** i_{sc}
- Find the equivalent resistance R_{eq} of the network **with all independent sources turned off**.

Then:
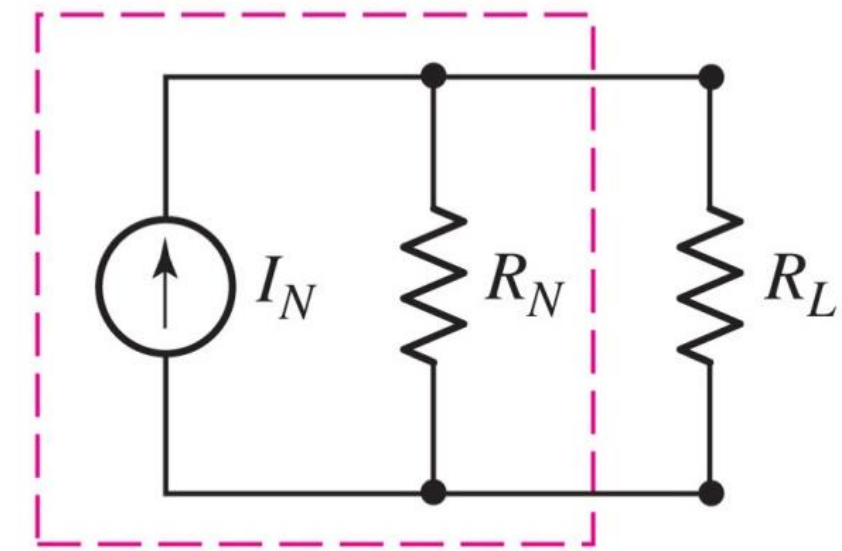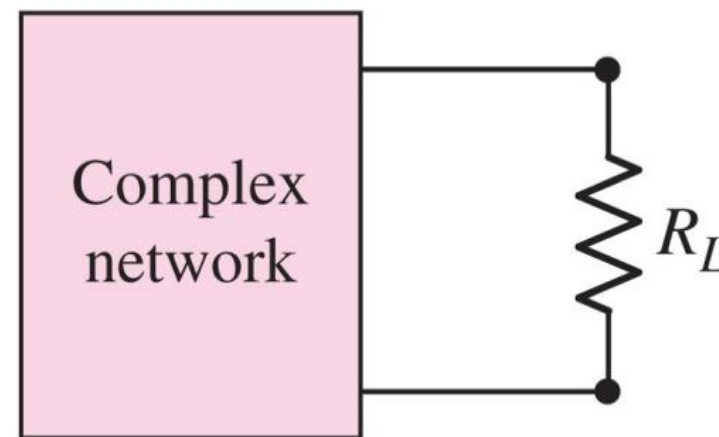
$$I_N = i_{sc} \text{ and } R_N = R_{eq}$$



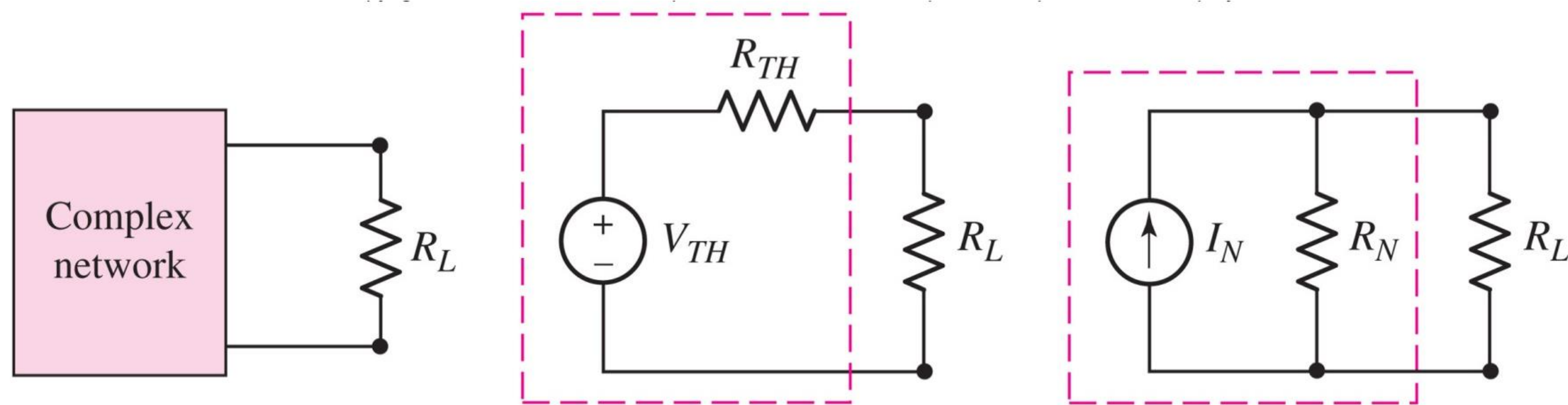
The **Thévenin** and **Norton** equivalents are **source transformations** of each other!




$$R_{TH} = R_N = R_{eq} \text{ and } v_{TH} = i_N R_{eq}$$

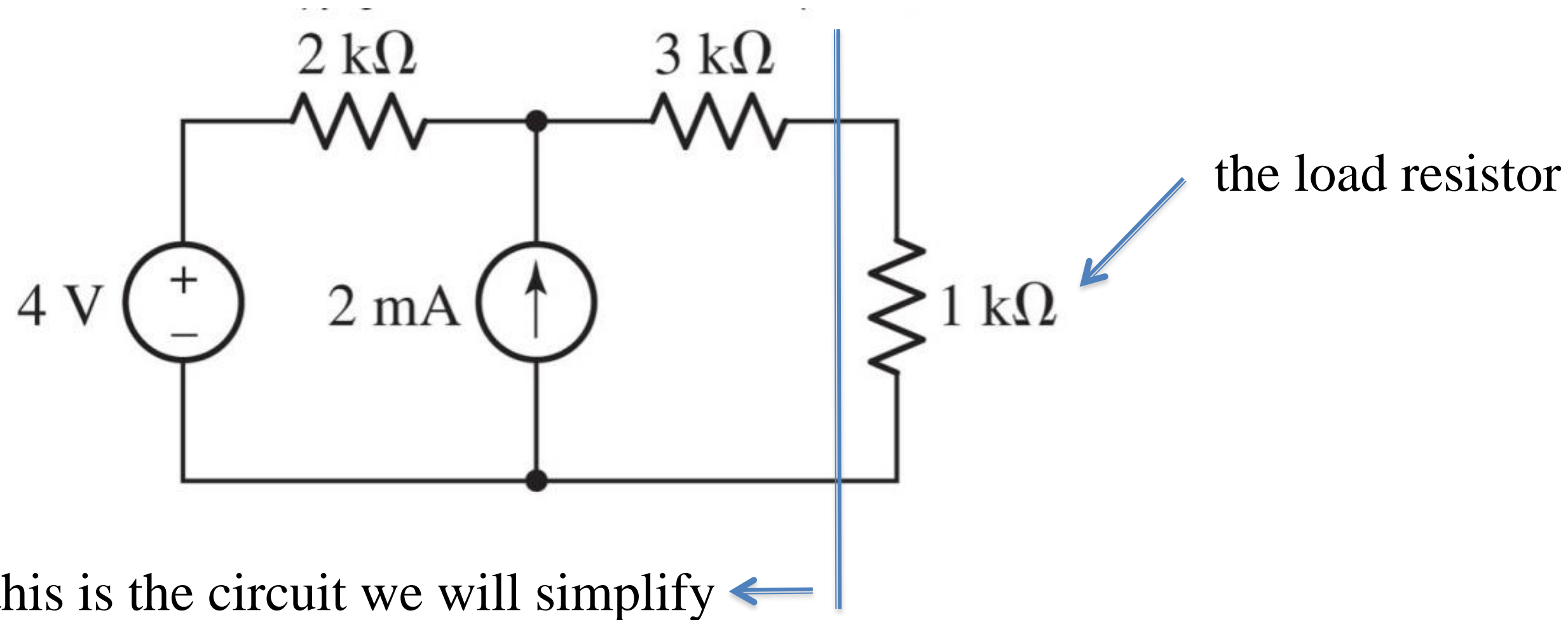Example: Norton and Thévenin

Find the Thévenin and Norton equivalents for the network faced by the 1-k Ω resistor.



Example: Norton and Thévenin

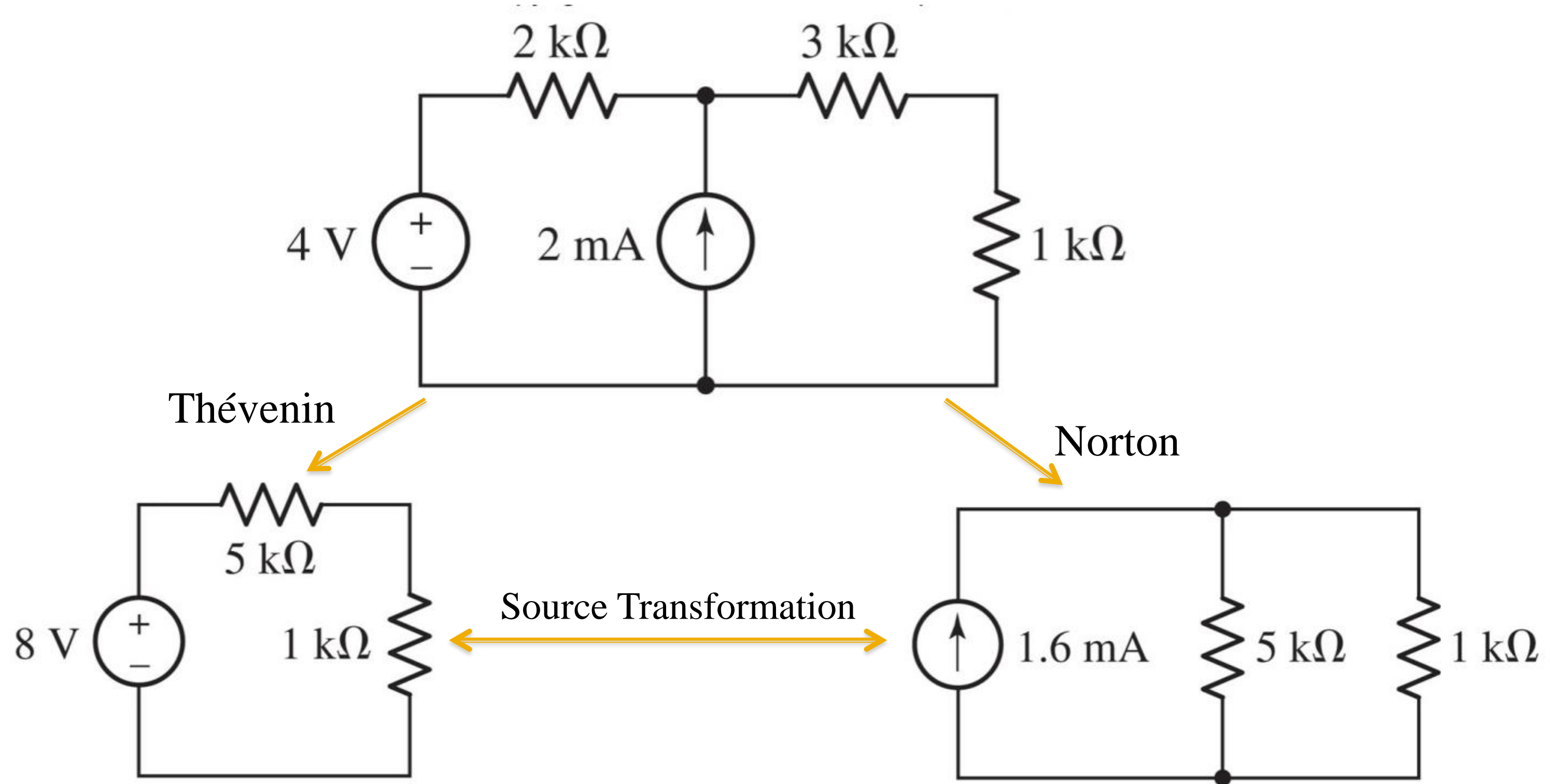


Thévenin Example: Handling Dependent Sources


One method to find the Thévenin equivalent of a circuit with a dependent source: find V_{TH} and I_N and solve for

$$R_{TH} = V_{TH} / I_N$$

Example:

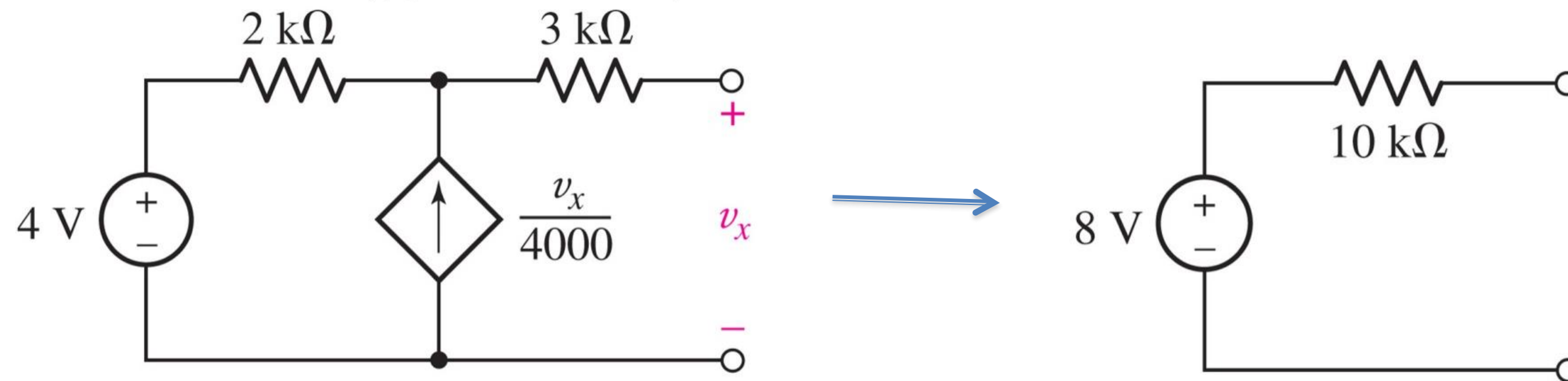

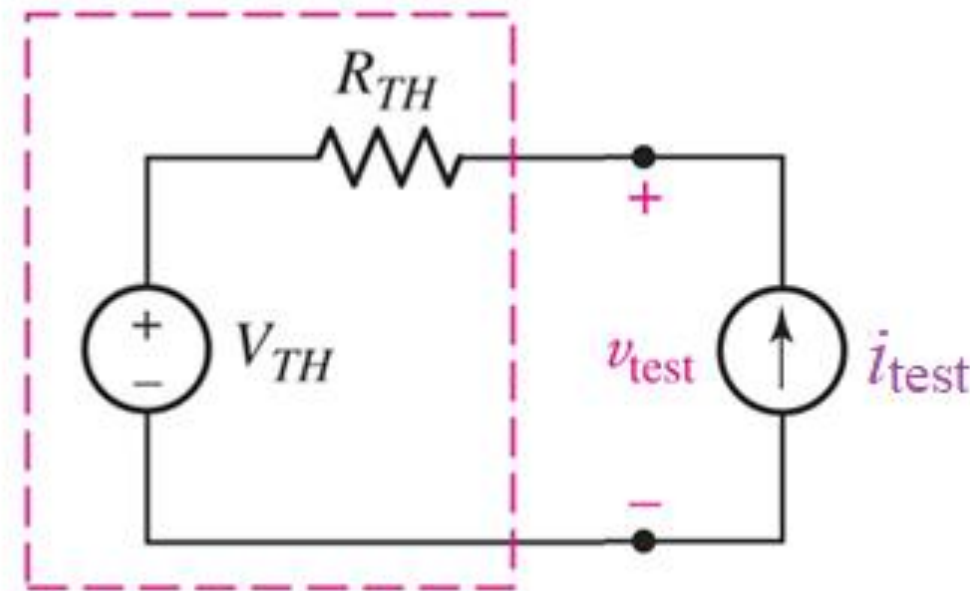
In general, a test source can be used to find the Thevenin and Norton equivalent circuits of any circuit.



$$v_{test} = R_{TH} i_{test} + V_{TH}$$

By placing the test source, an equation is obtained in which the coefficient i_{test} represents the Thevenin resistance, and the accumulated value with it is the Thevenin voltage.

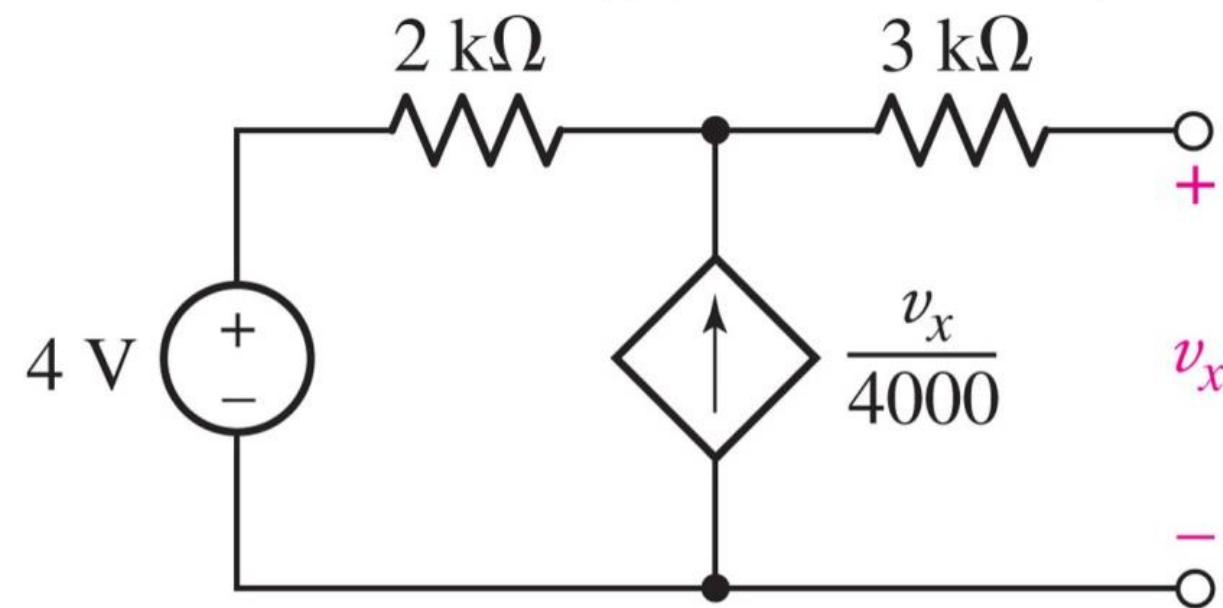
Using a test source to find the equivalent circuit




Thévenin Example: Handling Dependent Sources

Finding the ratio V_{TH}/I_N fails when **both** quantities are **zero**!

Solution: **apply a test source**.

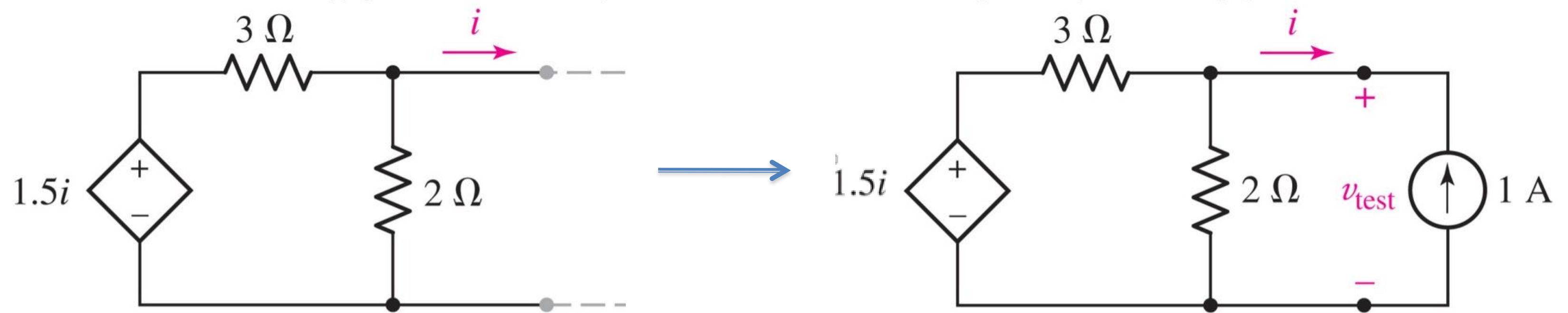


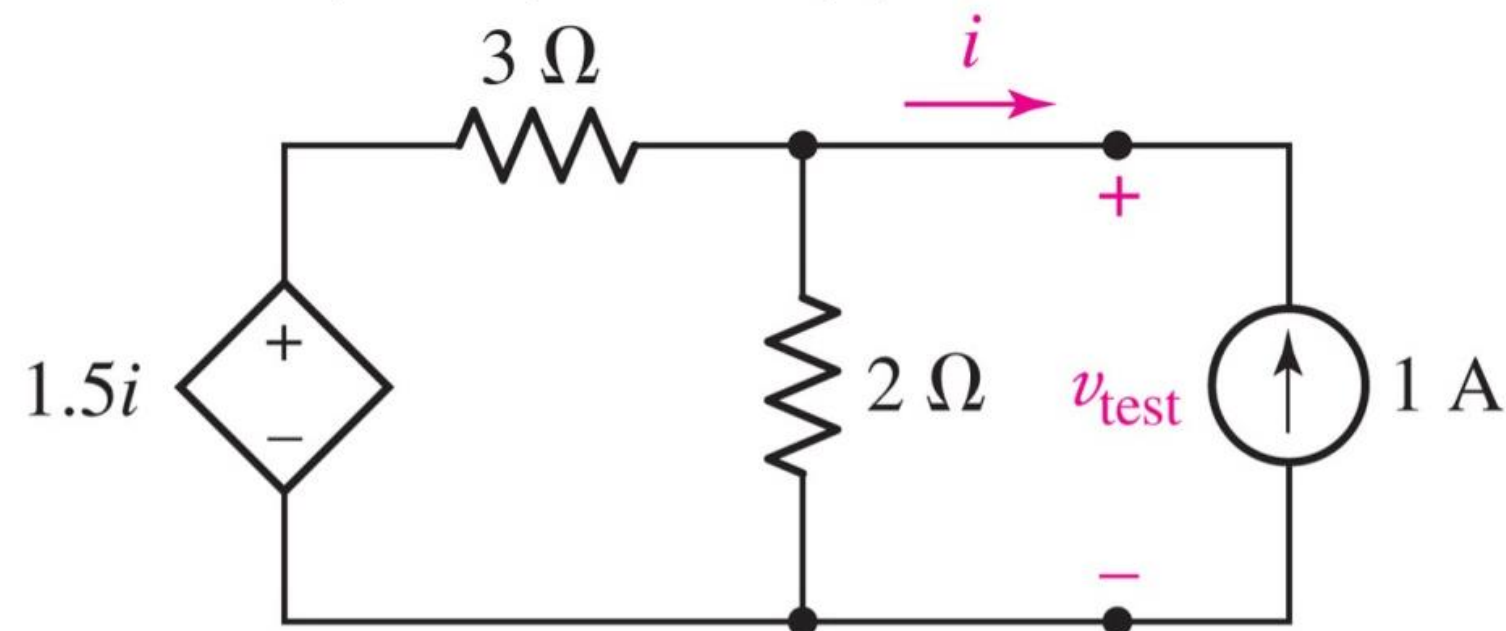
Thévenin Example: Handling Dependent Sources



$$\frac{v_{test}}{2} + \frac{v_{test} - (1.5i)}{3} = 1$$

$$i = -1$$

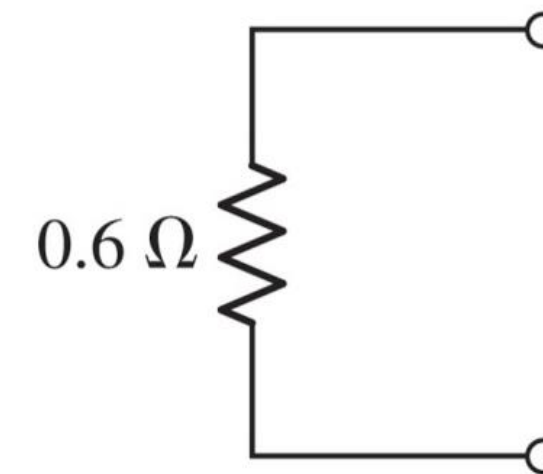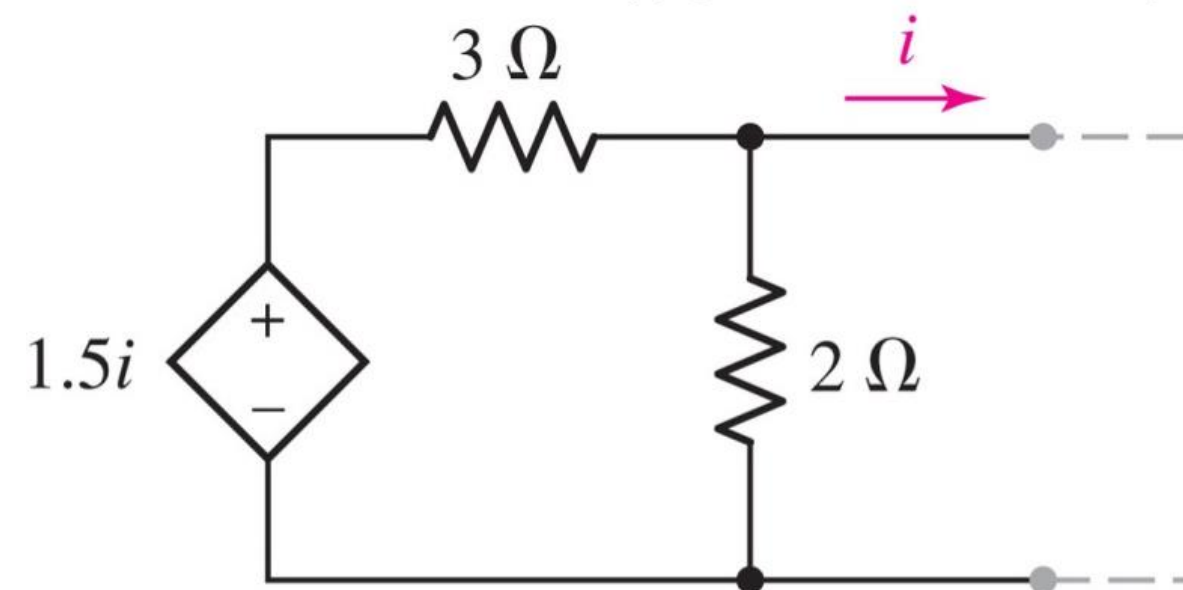Solve: $v_{test} = 0.6 \text{ V}$, and so $R_{TH} = 0.6 \Omega$




Maximum Power Transfer

What load resistor will allow the practical source to deliver the maximum power to the load?

Answer: $R_L = R_s$


[Solve $dp_L/dR_L=0$.]

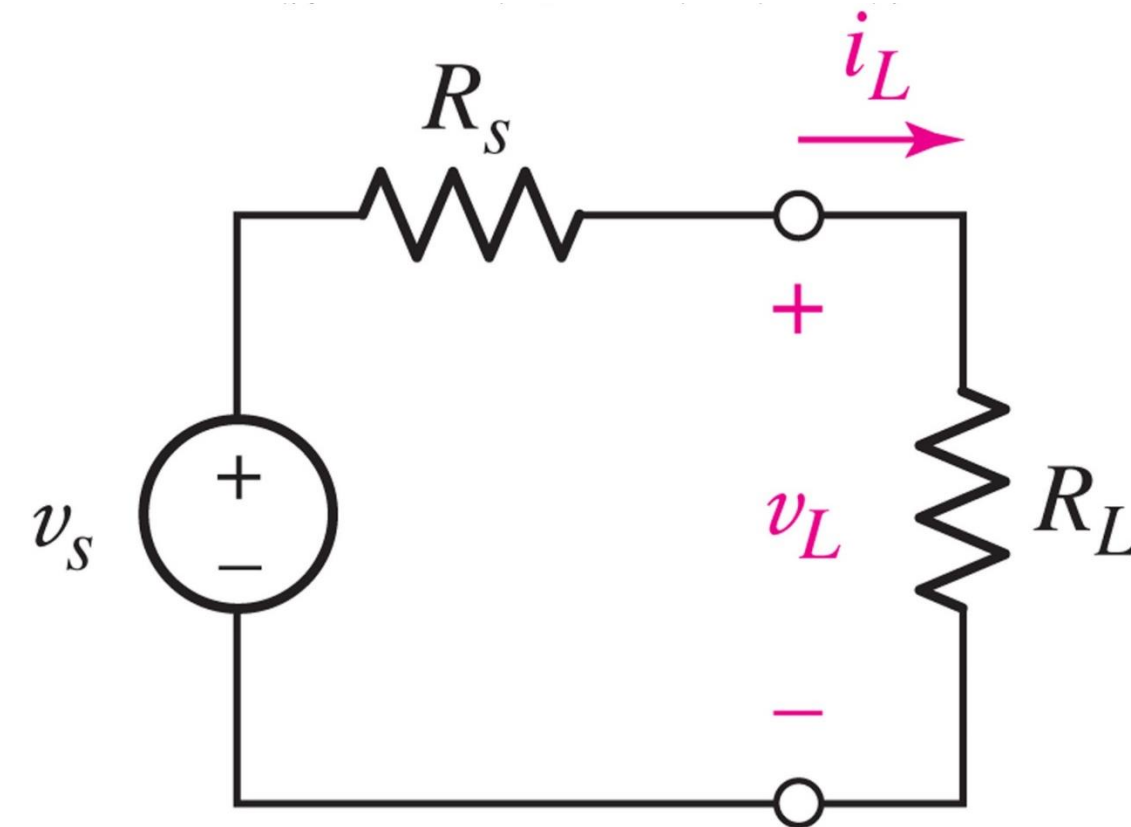[Or: $p_L = i(v_s - iR_s)$, set $dp_L/di=0$ to find $i_{\max} = v_s/2R_s$. Hence $R_L = R_s$]




Δ -Y (delta-wye) Conversion


- The following resistors form a Δ :

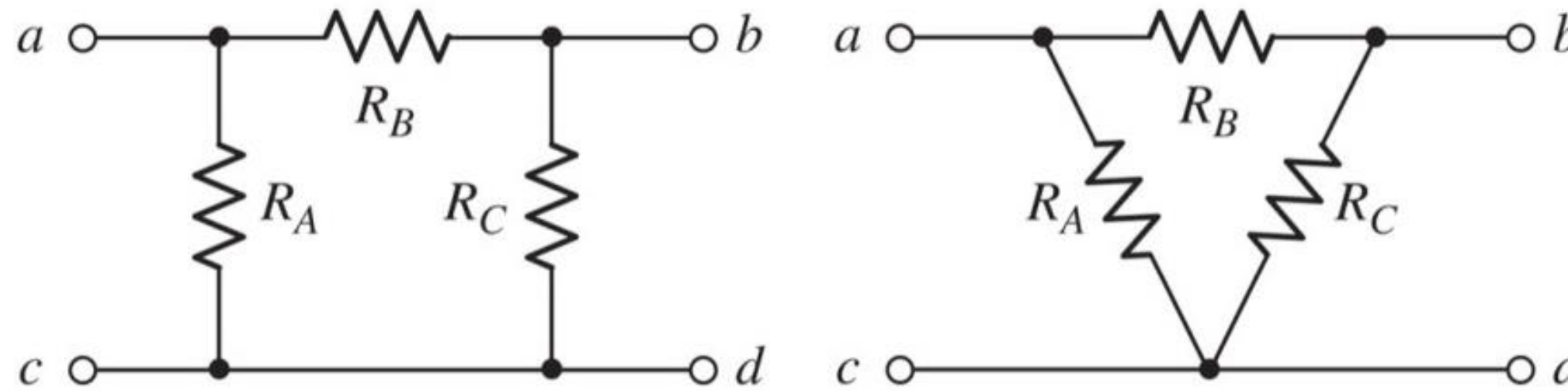

- The following resistors form a Y:

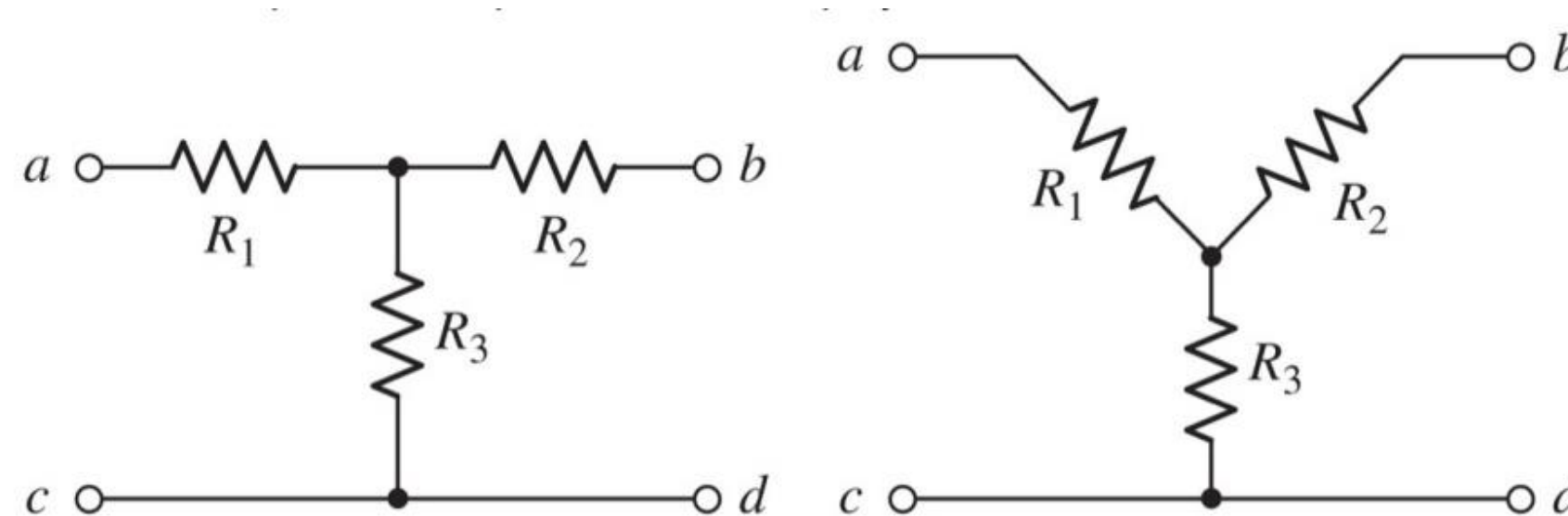

Δ -Y (delta-wye) Conversion

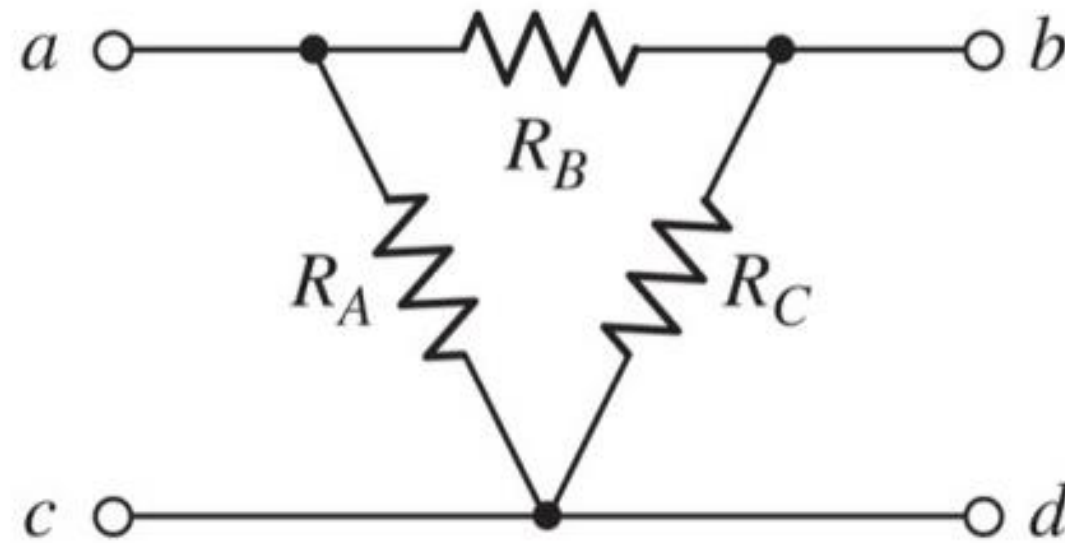


this Δ is equivalent to the Y if

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$
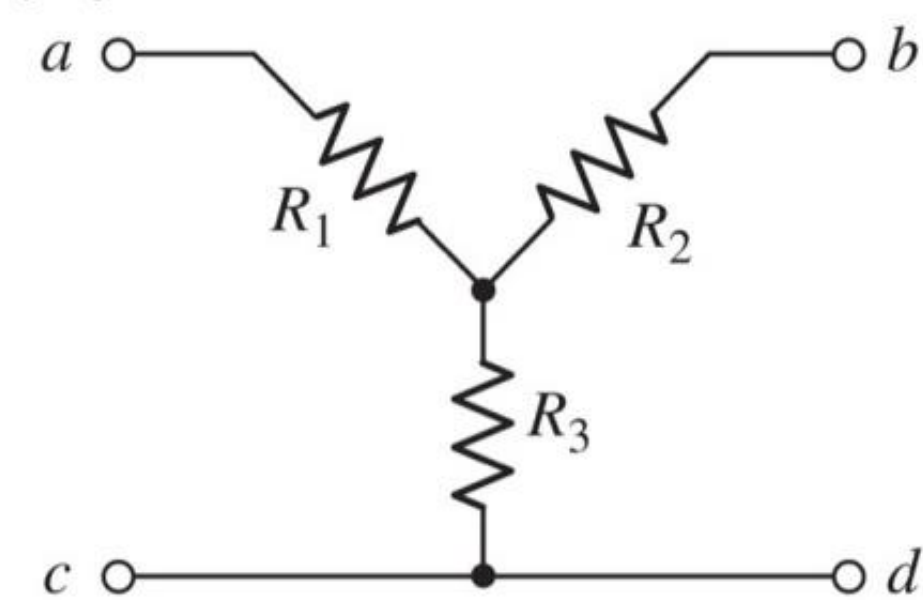
$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



this Y is equivalent to the Δ if


$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$


$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$

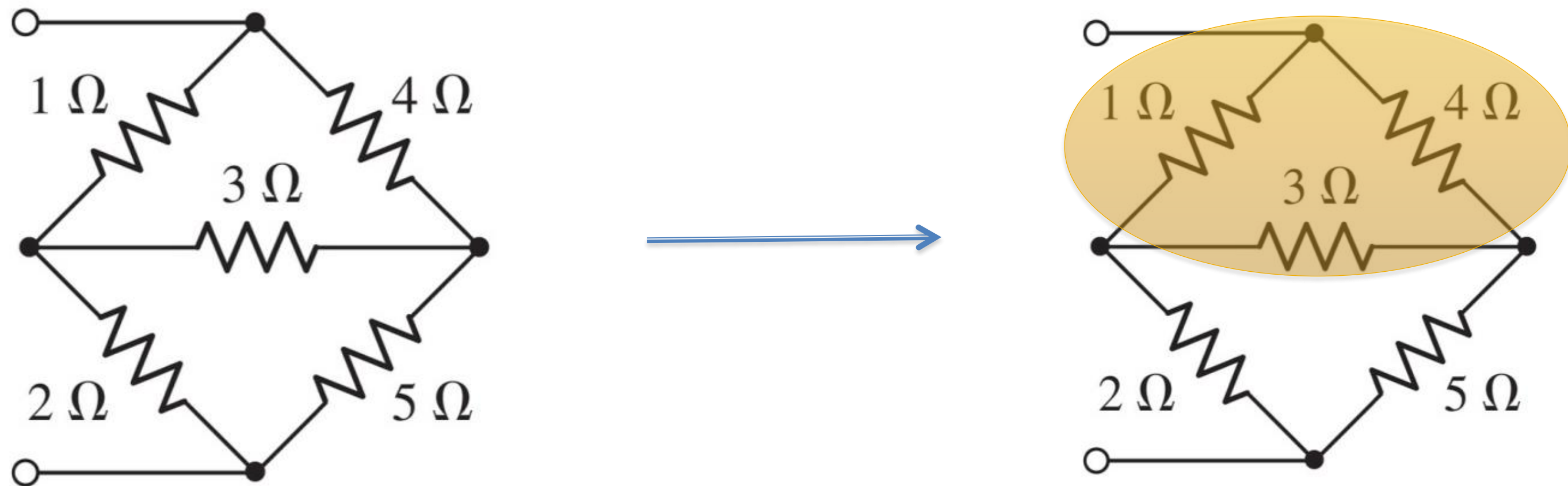Example: Δ -Y Conversion


How do we find the equivalent resistance of the following network? Convert a Δ to a Y




Example: Δ -Y Conversion

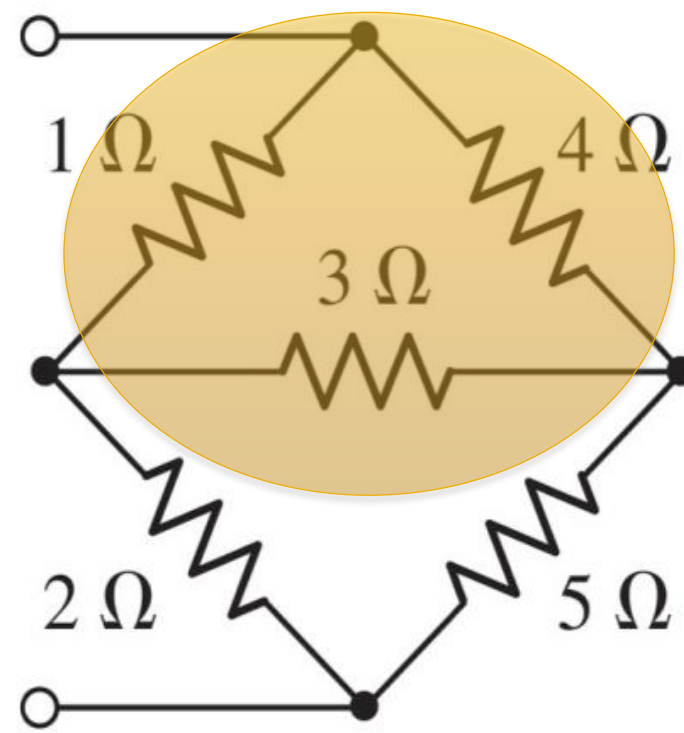

use the Δ to Y equations

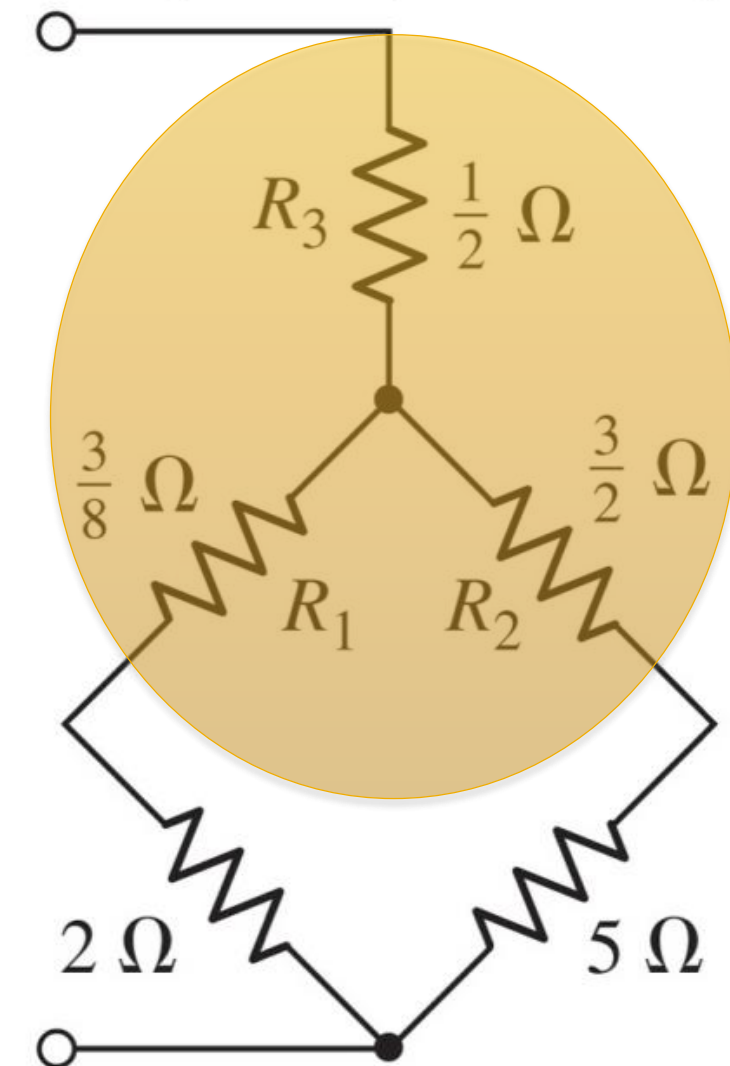

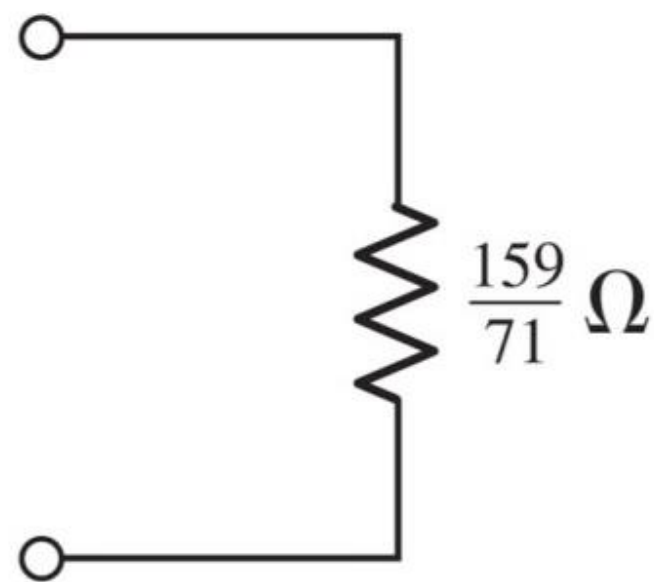use standard serial and parallel combinations




What you learned in this slide:

- The Superposition Theorem and how to use it
- Practical Sources
- Source Transformation and its application in circuit simplification
- Thevenin and Norton Equivalent Circuits and how to calculate them
- Maximum Power Transfer Theorem
- Star-Delta Transformation and its application in circuit simplification

Practice

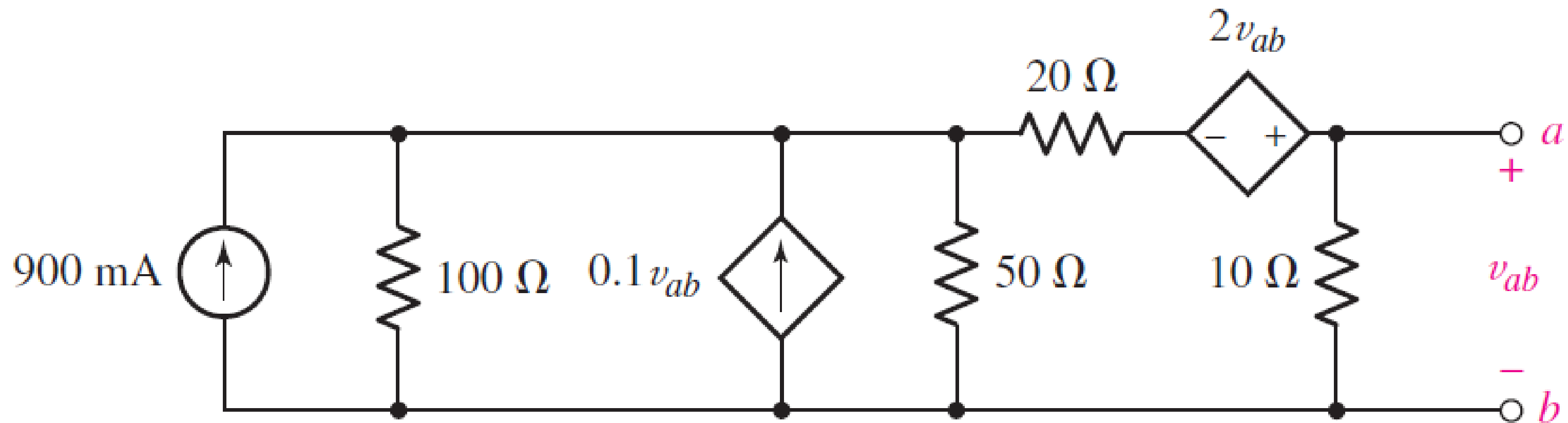If a load R_L is connected across terminals a and b , determine its value for maximum power transfer. Also, calculate the maximum power.





Thanks
