



دانشگاه صنعتی امیر کبیر
(پلی تکنیک تهران)

Electrical and Electronic Circuits

chapter 9. Frequency Response

Afarghadan@aut.ac.ir

عظیم فرقدان 


مهر ۱۴۰۳

Objectives of the Lecture

- Resonance
- Frequency filter
- Describe the sinusoidal steady-state behavior of a circuit as a function of frequency.


- Resonance is a phenomenon in which an external force causes a system to oscillate with a greater amplitude.
- The frequency at which resonance occurs is called the **resonance frequency**.

Tacoma bridge, 1940, US

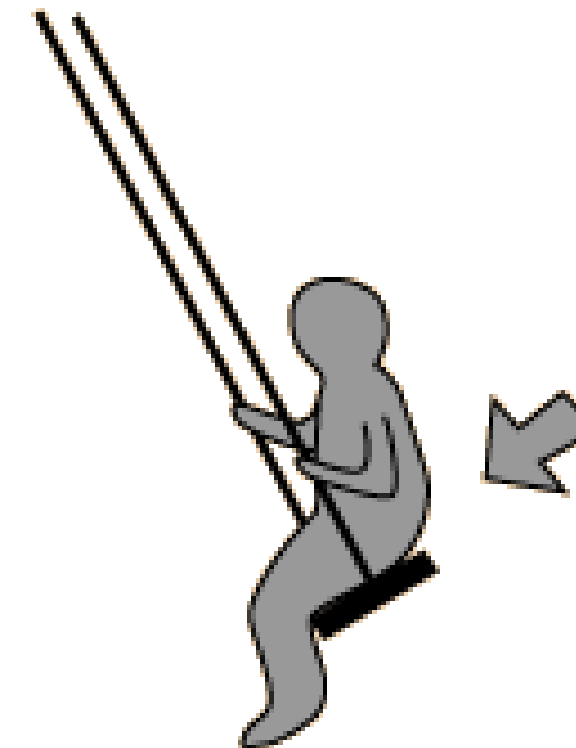

Electrical Resonance

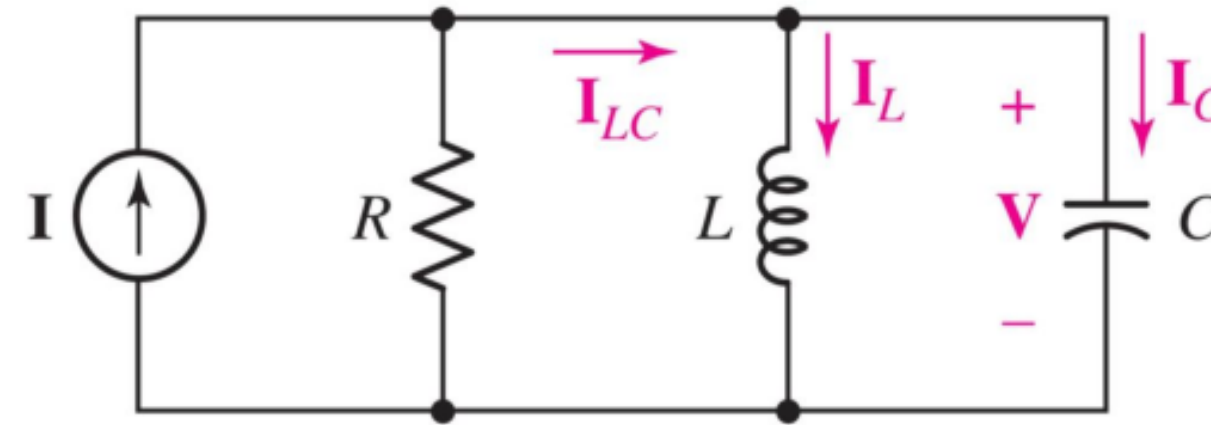In the circuit below, what is the frequency of the sinusoidal source so that the ratio V/I is maximized (Resonance occurs)?



$$\frac{V}{I} = Z_{eq} = \frac{R}{1 + jR(c\omega - \frac{1}{L\omega})} \rightarrow Z_{max} = R$$

The resonance frequency is $\omega_0 = \frac{1}{\sqrt{LC}}$.


Inductor and capacitor begin to exchange energy between themselves and no longer receive energy from the source.

- In the previous example, you observed that when resonance occurs, the imaginary part of the impedance becomes zero.

$$Z_{eq} = \frac{R}{1 + jR\left(C\omega - \frac{1}{L\omega}\right)} \rightarrow Z_{max} = R$$

- This is true for all RLC circuits, meaning resonance occurs when the imaginary part of the impedance or admittance becomes zero.
- In this state, the current and voltage of the circuit become in phase (since the equivalent impedance of the circuit is a real number and behaves like a resistor).

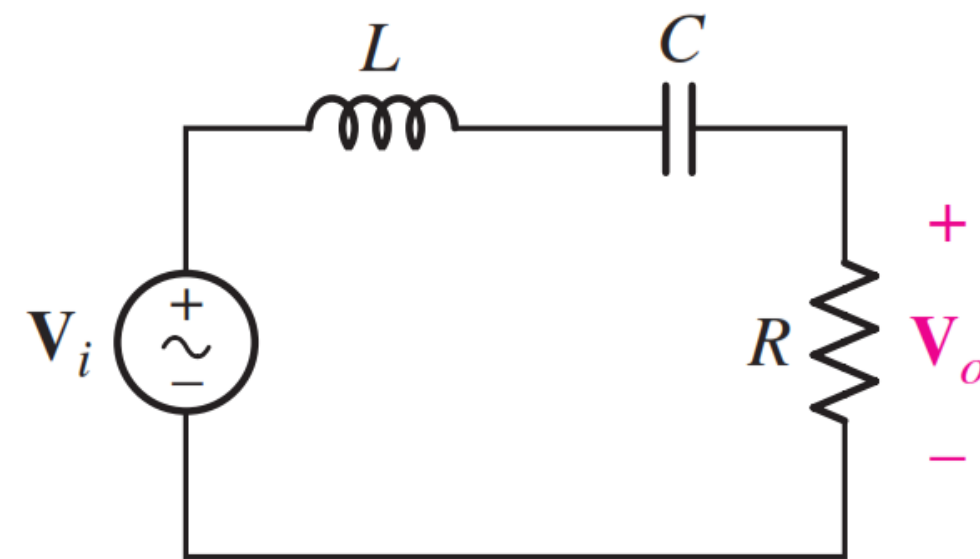What is the resonance frequency in a series RLC circuit?



- $Z_{eq} = R + j\omega L + \frac{1}{j\omega C}$
- $\text{Im}g(Z_{eq}) = 0 \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$


Frequency Response

- If we let the amplitude of the sinusoidal source remain constant and vary the frequency,
 - we obtain the circuit's **frequency response**.
- The **frequency response** of a circuit is the variation in its behavior with change in signal frequency.
- The **frequency response** of a circuit may also be considered as the **variation of the gain and phase with frequency**.

Frequency Response

In an n-order circuit with a sinusoidal input, frequency response analysis involves finding:

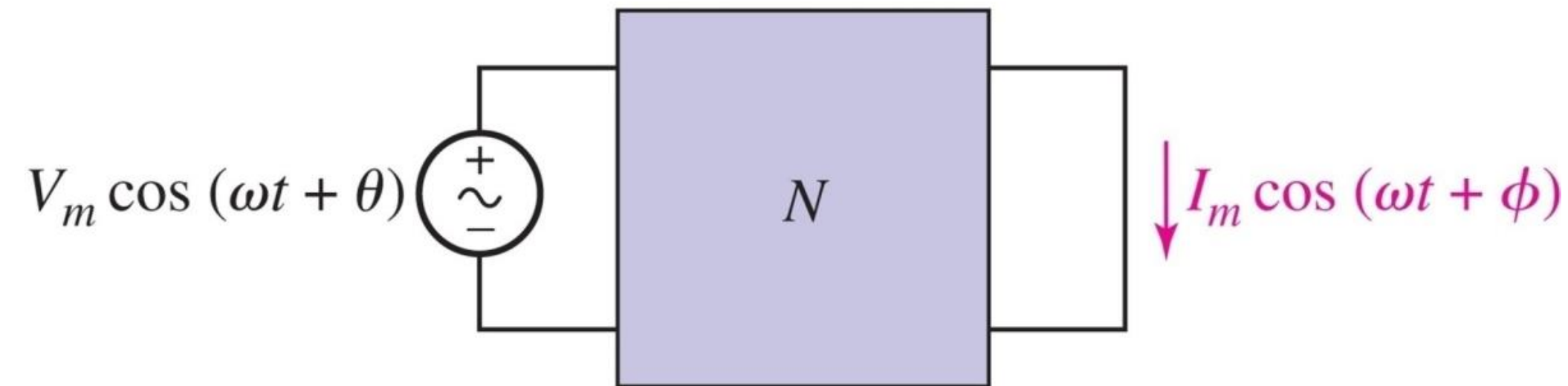
- The ratio of the output amplitude to the input amplitude ($\frac{I_m}{V_m}$), known as the gain A.
- The phase difference between them ($\phi - \theta$) at various frequencies.



To perform this analysis, we use the **transfer function**.

Transfer Function

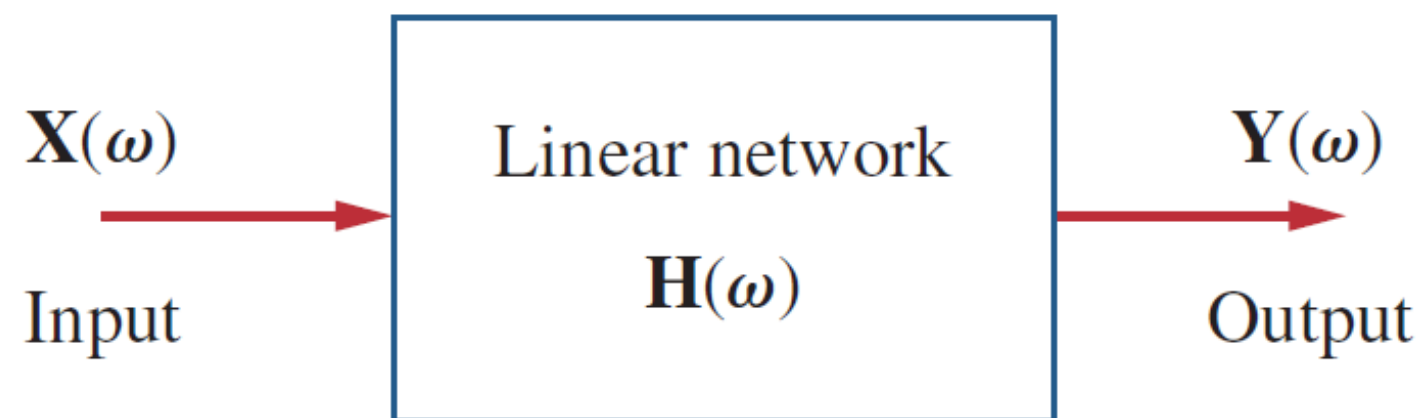
- The **transfer function** $\mathbf{H}(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $\mathbf{Y}(\omega)$ (an element voltage or current) to a phasor input $\mathbf{X}(\omega)$ (source voltage or current).



$$\mathbf{H}(\omega) = \frac{\mathbf{Y}(\omega)}{\mathbf{X}(\omega)}$$

Transfer Function

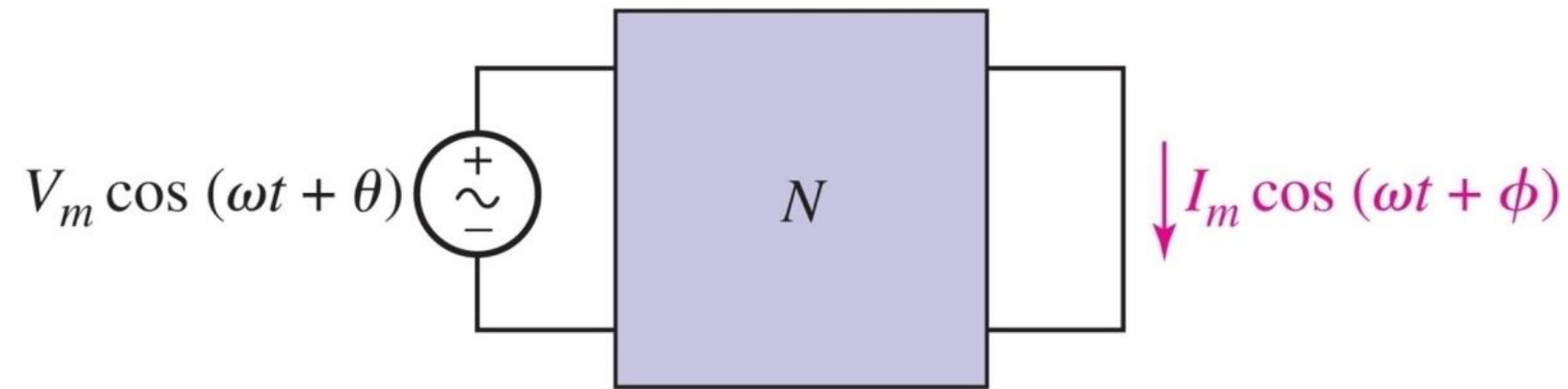The ratio of the output phasor to the input phasor is called the transfer function, $\mathbf{H}(j\omega)$.



- $\mathbf{H}(j\omega) = \frac{I_m e^{j\phi}}{V_m e^{j\theta}}$

- $A = |\mathbf{H}(j\omega)| = \frac{I_m}{V_m}$

- $Phase = \angle \mathbf{H}(j\omega) = \phi - \theta$

All three are functions of frequency.

Transfer Function

- Since the input and output can be either voltage or current at any place in the circuit,
–there are four possible transfer functions:

$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$


$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

A low-pass RC filter
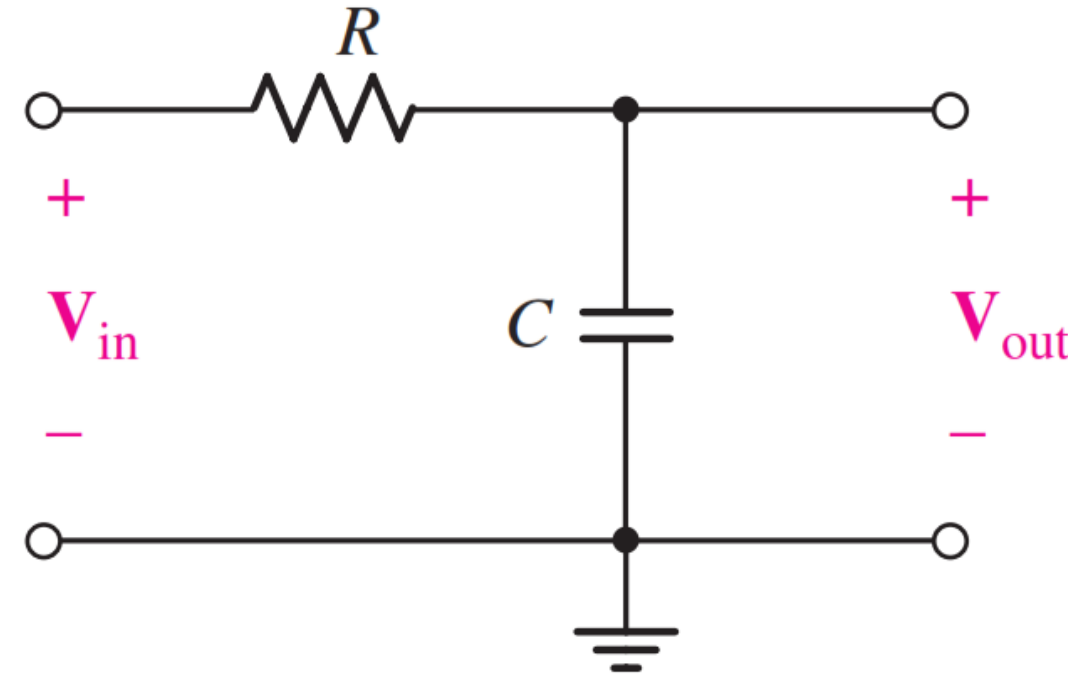
$$V_{out} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} V_{in} = \frac{1}{1 + j\omega RC} V_{in}$$



Assuming the capacitor voltage as the circuit output, the transfer function is given by:

$$\mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

Bode Diagram

A Bode diagram is a plot that shows the magnitude and phase of the transfer function as a function of frequency on a logarithmic scale.

- ✓ The horizontal axis represents frequency, plotted on a logarithmic scale.
- ✓ The vertical axis of the magnitude plot represents the gain in decibels (dB).
- ✓ The vertical axis of the phase plot represents the phase angle on a linear scale.

This diagram is useful for analyzing the frequency response of a system, showing how both the amplitude and phase of the output signal vary with changes in input frequency.


$$H_{dB} = 20 \log |\mathbf{H}(j\omega)|$$

The Bode diagram for an RC low-pass filter

- $\mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1+j\omega RC}$
- $|\mathbf{H}(j\omega)| = \frac{1}{\sqrt{1+\omega^2 R^2 C^2}}$
- $\angle \mathbf{H}(j\omega) = -\tan^{-1} \omega RC$


The **cutoff frequency** is the frequency at which the magnitude of the transfer function drops to $\frac{1}{\sqrt{2}}$ of its maximum value. This corresponds to a -3 dB, point on the magnitude plot.

- $f_c = \frac{1}{2\pi RC}$

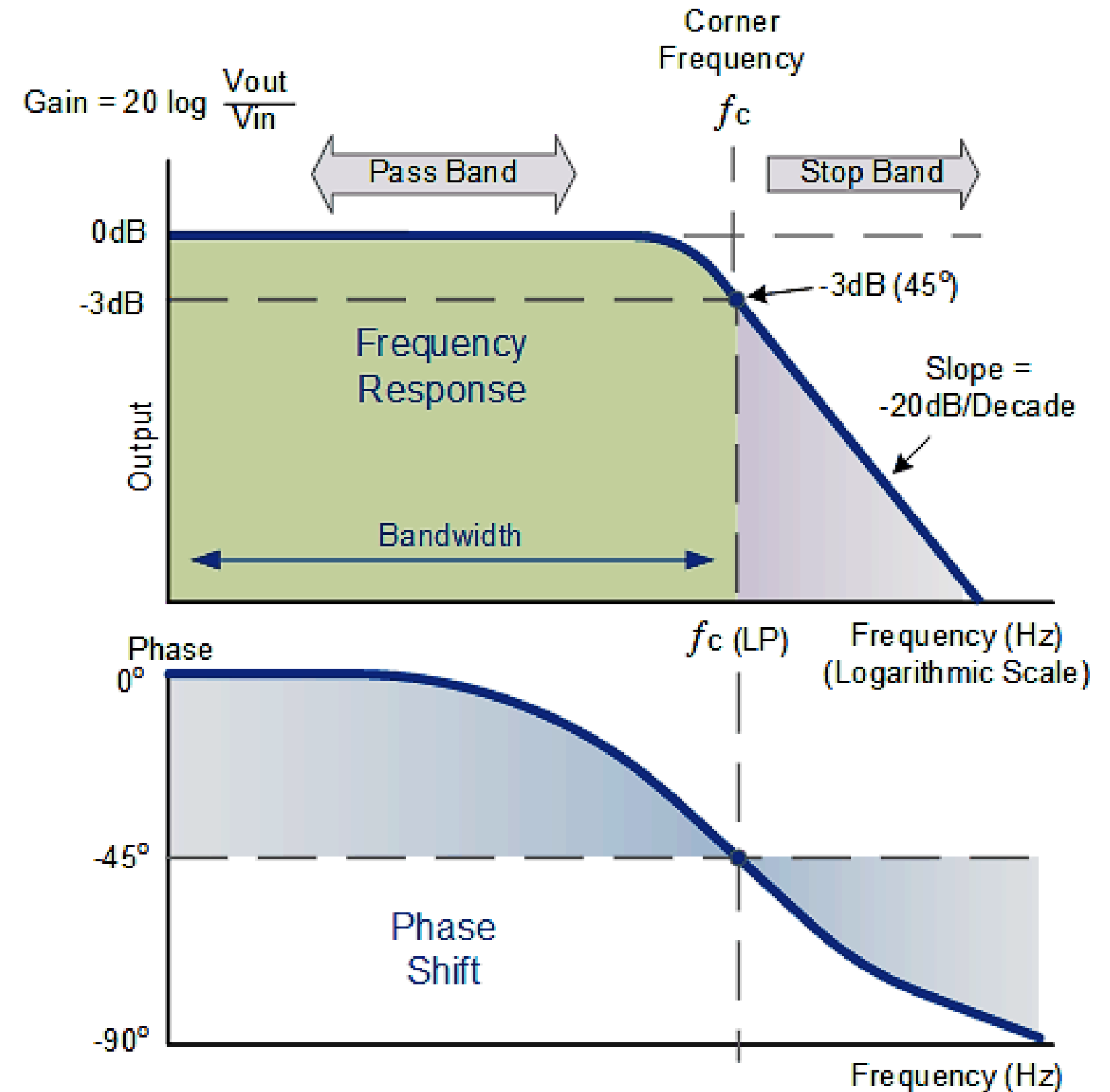

RC high-pass filter
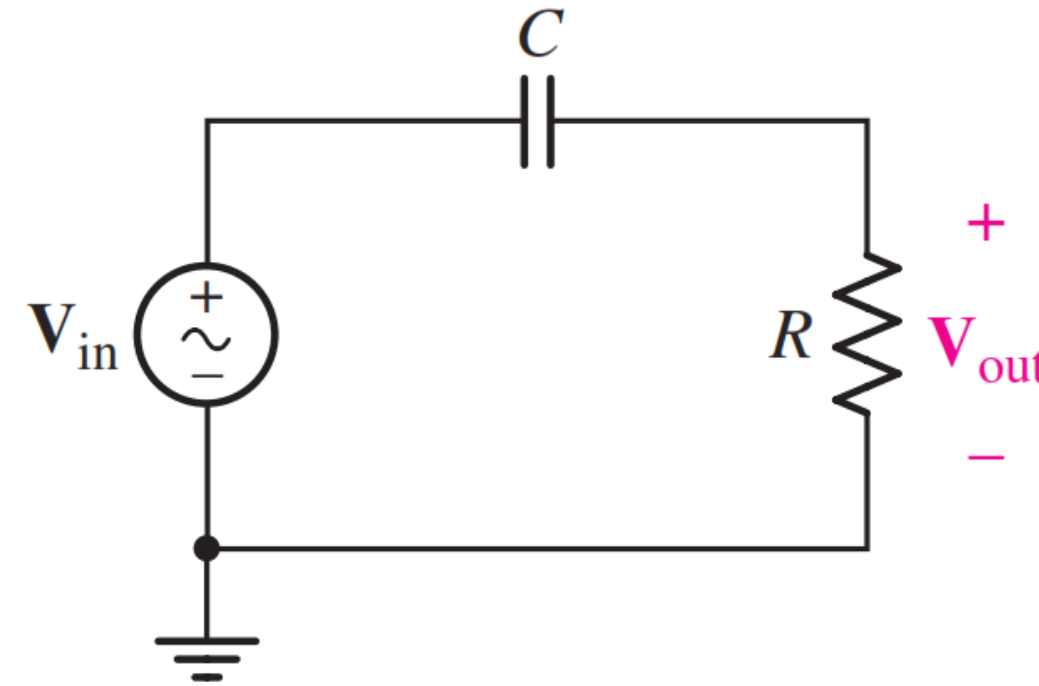
$$V_{out} = \frac{R}{\frac{1}{j\omega C} + R} V_{in} = \frac{j\omega RC}{1 + j\omega RC} V_{in}$$



- Transfer function

$$\mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1 + j\omega RC}$$


The Bode diagram for an RC high-pass filter

$$\square \mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1+j\omega RC}$$


$$\square |\mathbf{H}(j\omega)| = \frac{\omega RC}{\sqrt{1+\omega^2 R^2 C^2}}$$

$$\square \angle \mathbf{H}(j\omega) = \frac{\pi}{2} - \tan^{-1} \omega RC$$

$$\square f_c = \frac{1}{2\pi RC}$$

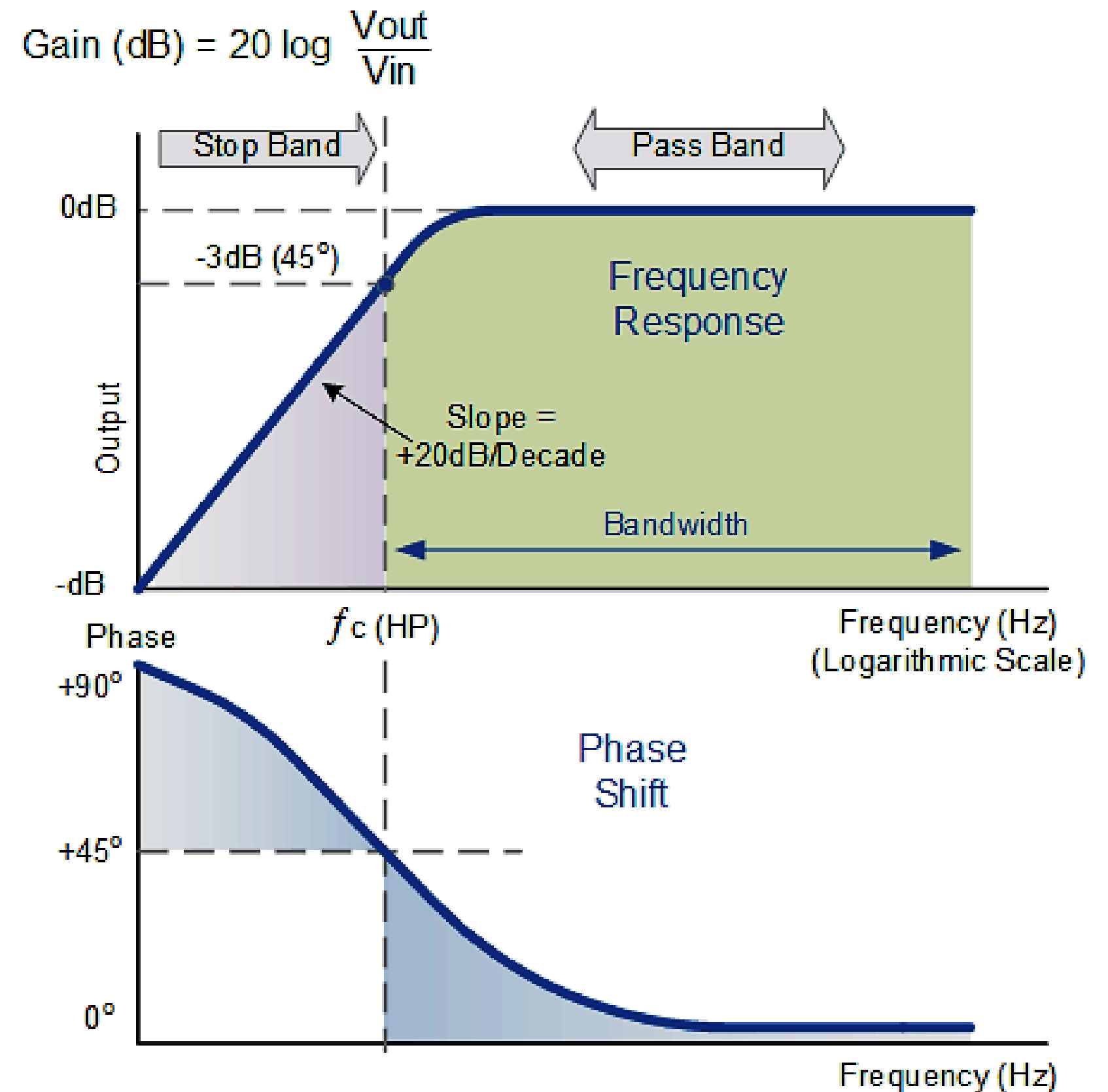
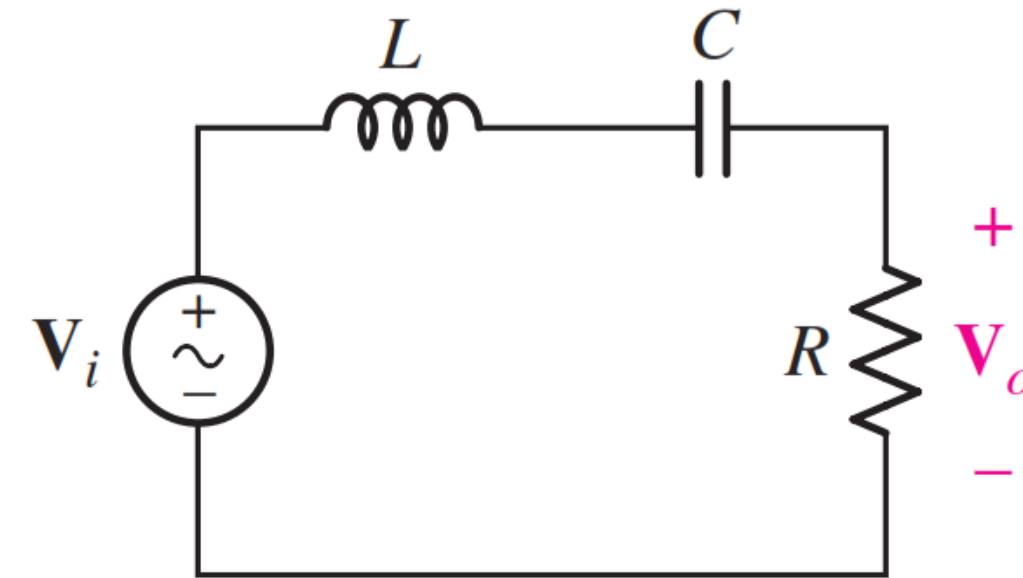
$$V_{out} = \frac{R}{j\omega L + \frac{1}{j\omega C} + R} V_{in}$$



- Transfer function

$$\mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1 + j\omega RC - \omega^2 LC}$$

$$\square \mathbf{H}(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1+j\omega RC-\omega^2 LC}$$


$$\square |\mathbf{H}(j\omega)| = \frac{\omega RC}{\sqrt{(1-\omega^2 LC)^2 + \omega^2 R^2 C^2}}$$

$$\square \angle \mathbf{H}(j\omega) = \frac{\pi}{2} - \tan^{-1} \frac{\omega RC}{1-\omega^2 LC}$$

□ Find the cutoff frequencies f_L and f_H .

□ Bandwidth: the distance between the two frequencies.

$$\square BW = 2\pi(f_H - f_L)$$

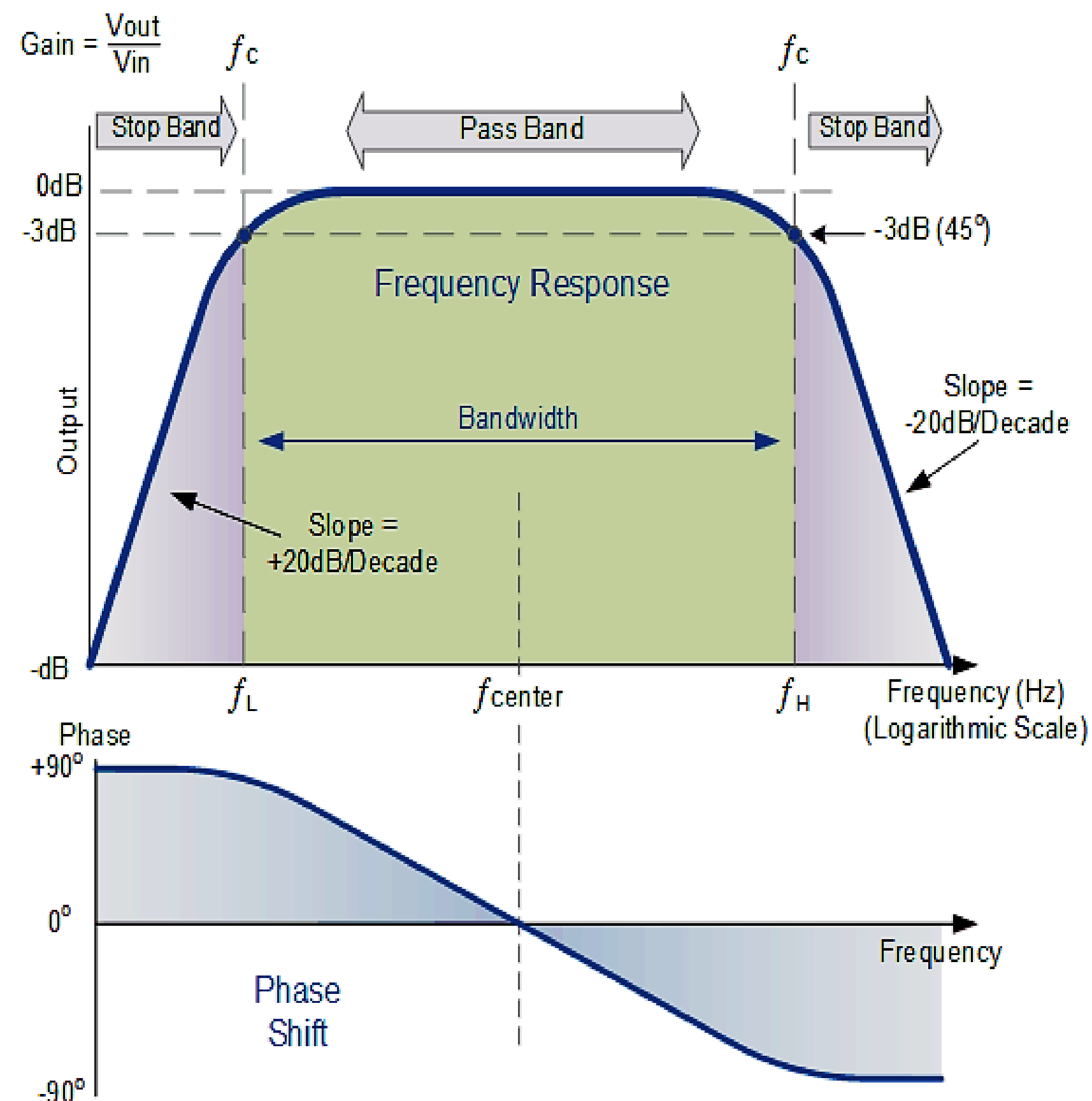



Thanks
