



دانشگاه صنعتی امیر کبیر  
( پلی تکنیک تهران )

# Electrical and Electronic Circuits

## Chapter 1

## Introduction and Basic Components and Electric Circuits

Afarghadan@aut.ac.ir


عظیم فرقدان 

مهر ۱۴۰۳

Method	Quantity	(%)	(%)
Quiz	-	5	-
Homework/Problem Solving	7	15	-
Laboratory	-	-	100
Midterm Exam	1	35	-
Final Exam	1	45	-
Attendance & participation	-	extra	-
Final Grade		75	25

# Reference Books

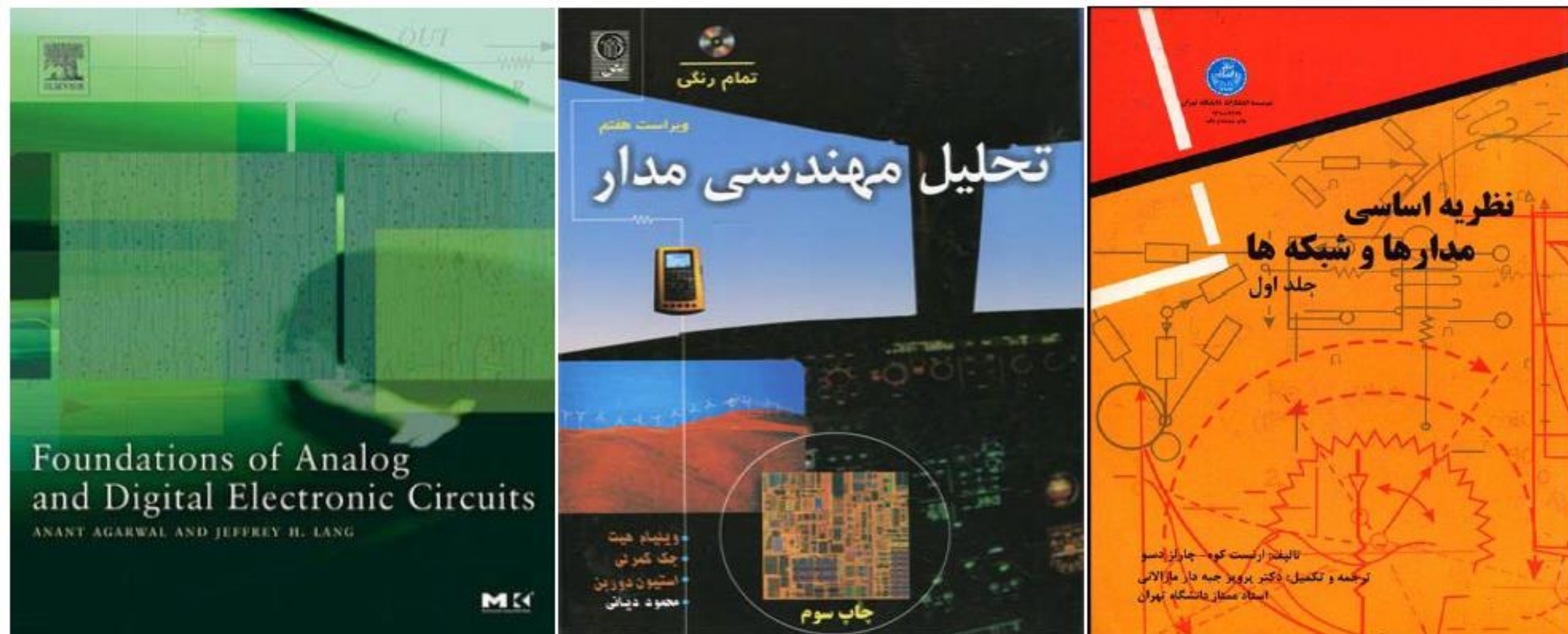1. C. Desoer, Basic Circuit Theory, 2nd Edition
2. W. Hayt, Engineering Circuit Analysis, 8th Edition
3. A. Agarwal, Foundations of Analog and Digital Electronic Circuits



# The SI System

- Base units:
  - meter (m), kilogram (kg), second (s), ampere (A)
- Derived units:
  - work or energy: joule (J)
  - power (rate of doing work): watt (W)
  - $1 \text{ W} = 1 \text{ J/s}$

□ Any measurement can be expressed in terms of a unit, or a unit with a “prefix” modifier.


FACTOR	NAME	SYMBOL
$10^{-9}$	nano	n
$10^{-6}$	micro	$\mu$
$10^{-3}$	milli	m
$10^3$	kilo	k
$10^6$	mega	M

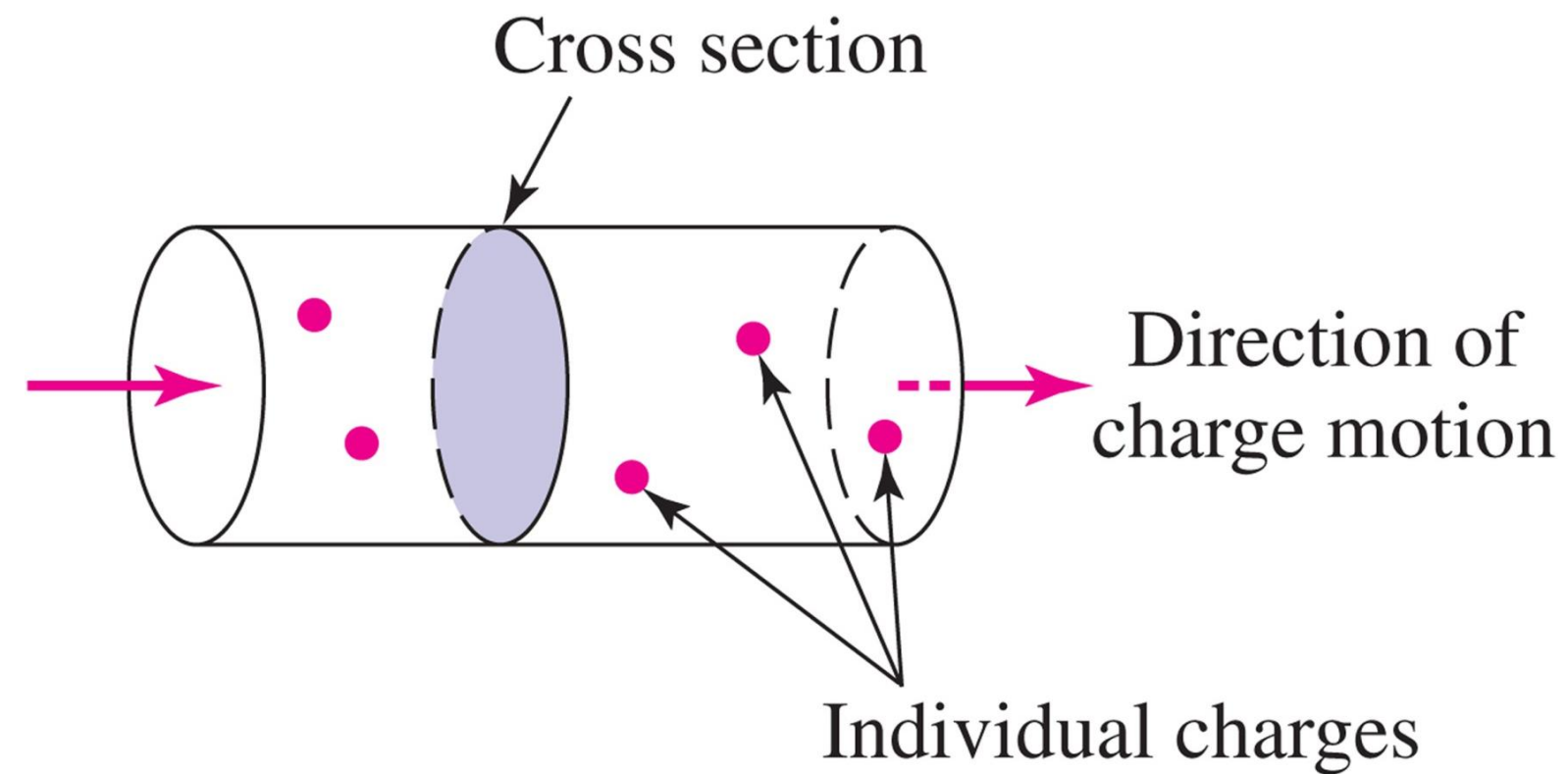Example:  $12.3 \text{ mW} = 0.0123 \text{ W} = 1.23 \times 10^{-2} \text{ W}$

- charge is *conserved*: it is neither created nor destroyed
- symbol: **Q** or *q*; units are coulomb (**C**).
- the smallest charge, the *electronic charge*, is carried by an **electron**  
( $-1.602 \times 10^{-19}$  C) or a **proton** ( $+1.602 \times 10^{-19}$  C).
- in most circuits, the charges in motion are **electrons**.



- Current is the rate of charge flow:
- 1 ampere = 1 coulomb/second (or  $1 \text{ A} = 1 \text{ C/s}$ )





- ❑ Current (designated by  $I$  or  $i$ ) is **the rate of flow of charge**
- ❑ Current must be designated with both a **direction** and a **magnitude**
- ❑ These two currents are the **same**:


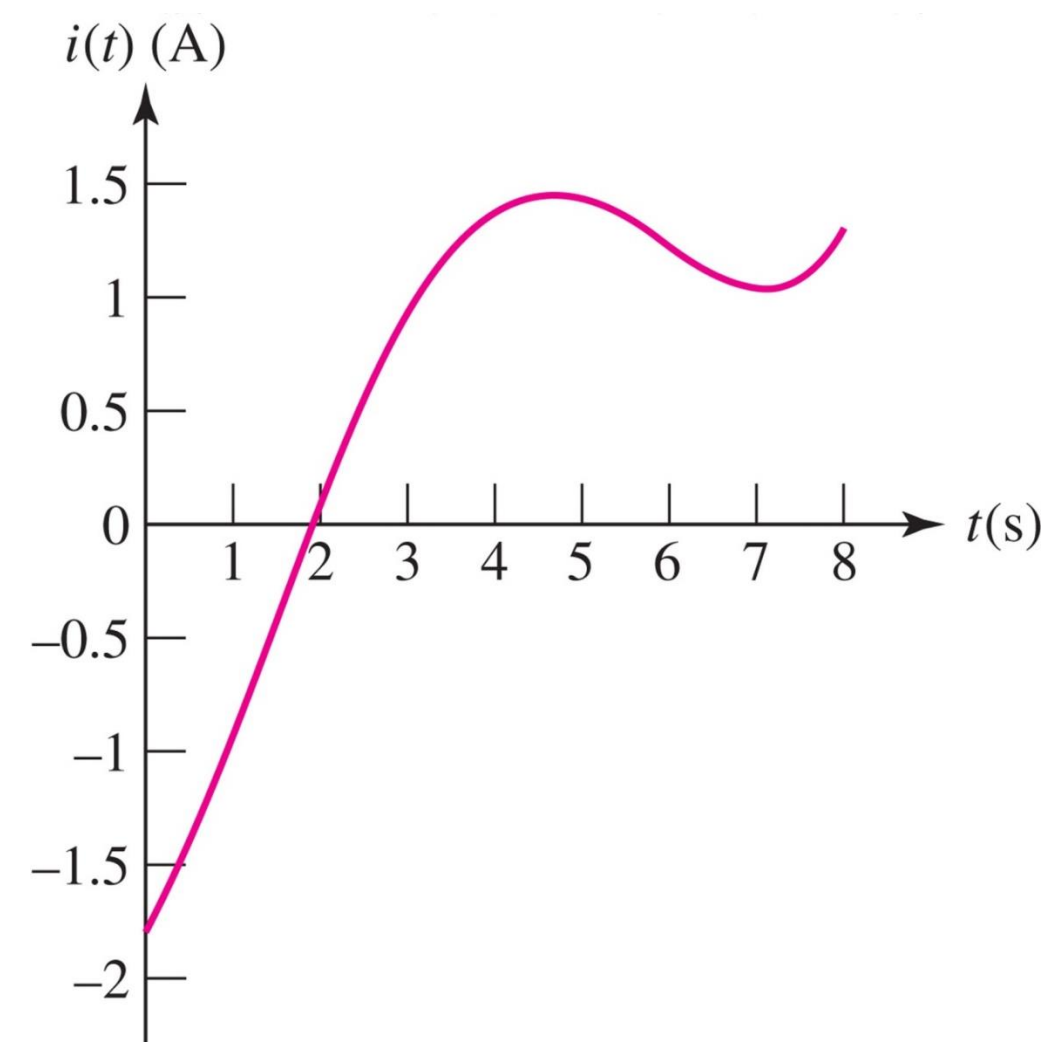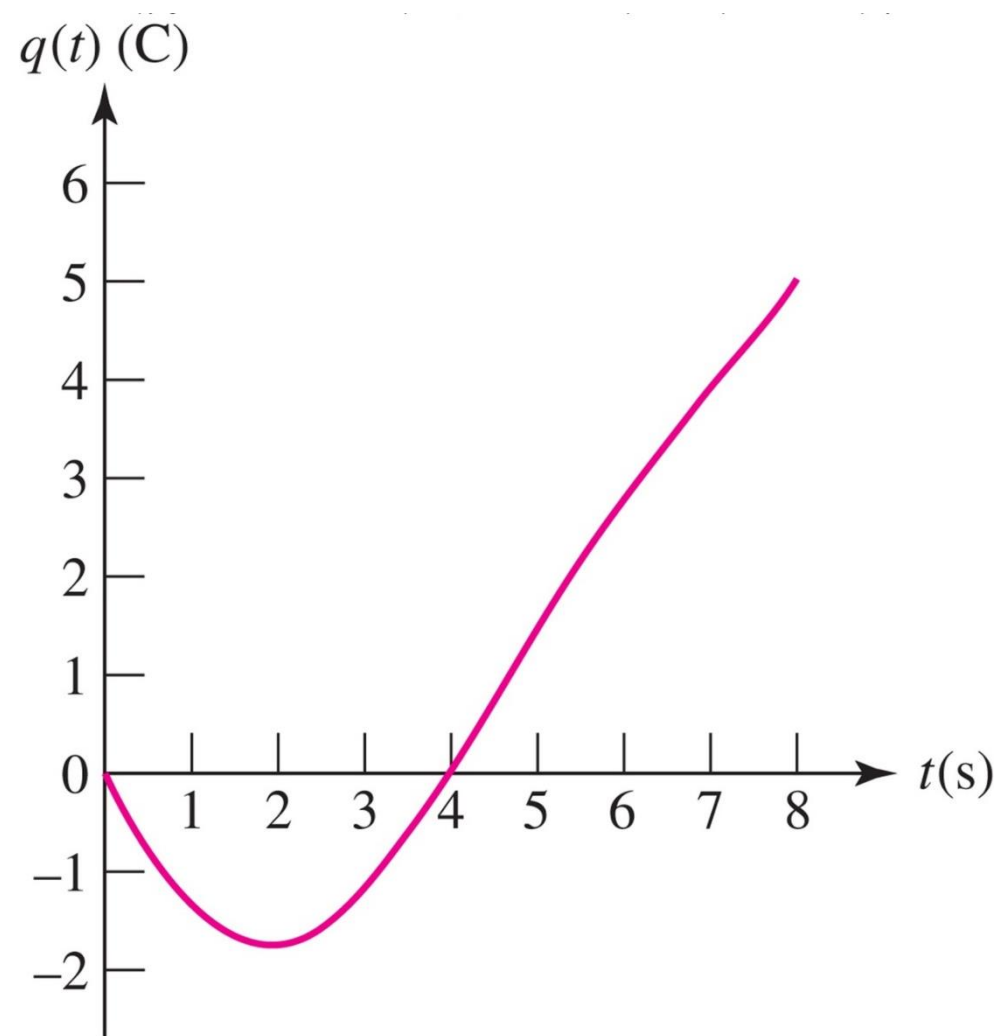
# Current and Charge: $i = dq/dt$


□ Current is **the rate of flow of charge**:  $i = dq/dt$





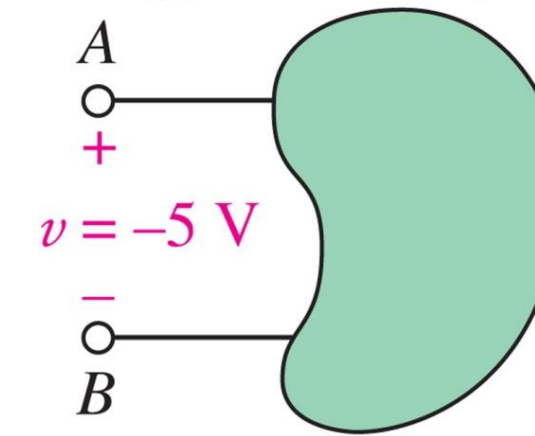
# Voltage


- When  $1 \text{ J}$  of work is required to move  $1 \text{ C}$  of charge from A to B, there is a voltage of 1 volt between A and B.
- Voltage ( $V$  or  $v$ ) across an element requires both a magnitude and a polarity.
- $V = dW/dq$
- Example: (a)=(b), (c)=(d)




(a)

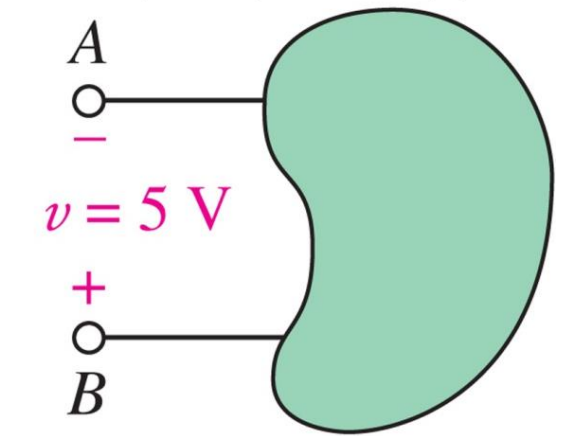

(b)

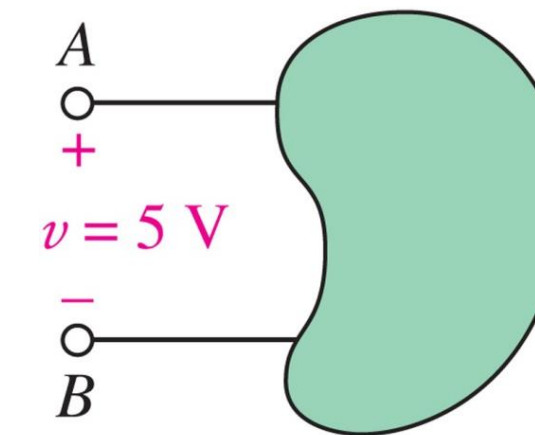

(c)

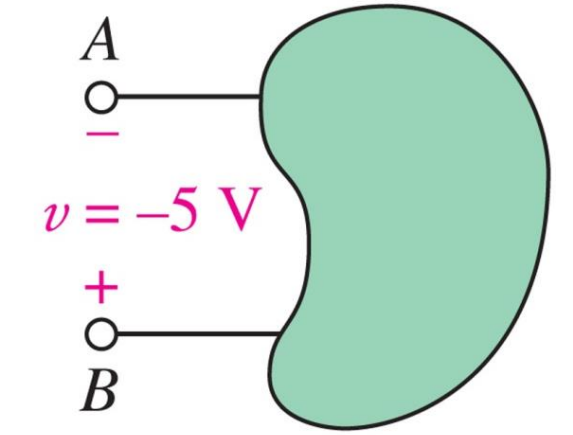

(d)

$$\text{Power: } p = v i$$


- The power required to push a current  $i$  (C/s) into a voltage  $v$  (J/C) is  $p = vi$  (J/s = W).

➤  $P = dE/dt$


- When power is positive, the element is *absorbing* energy.
- When power is negative, the element is *supplying* energy.

- The direction of current and voltage shown in this figure is referred to as **the conventional direction**.

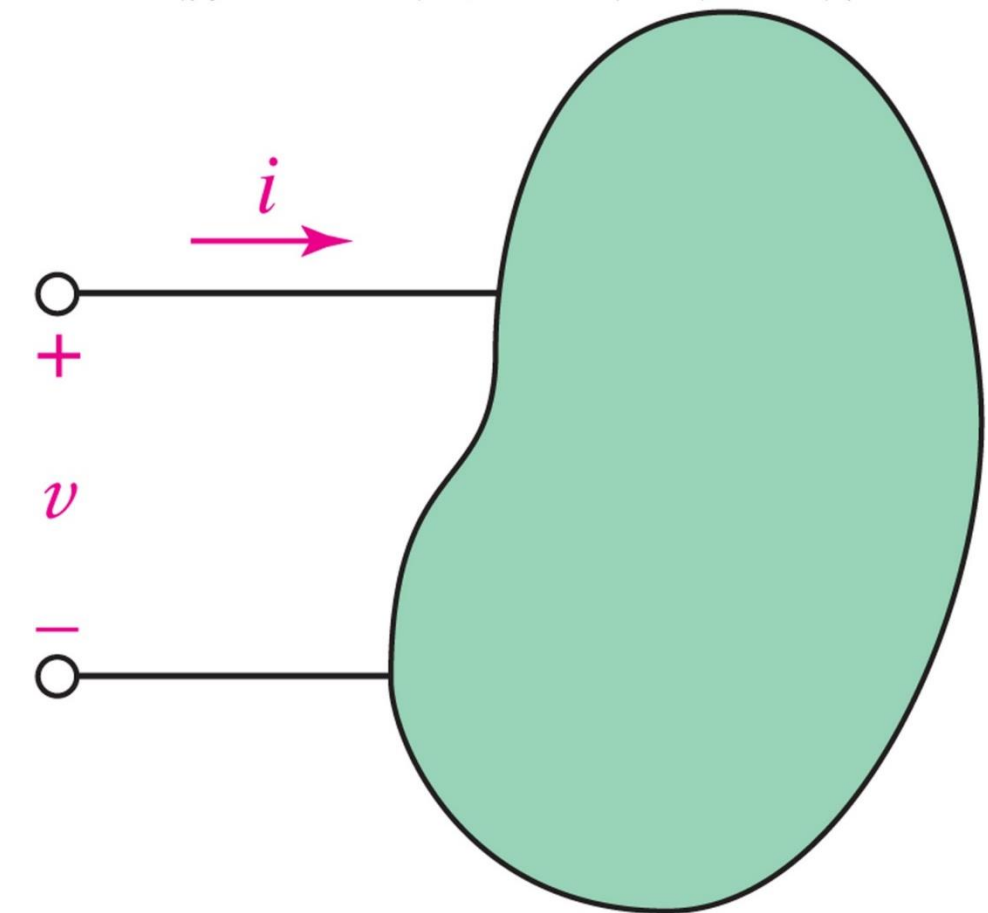➤ The *current enters* the element from the *positive terminal* of the voltage.




## Example: Power

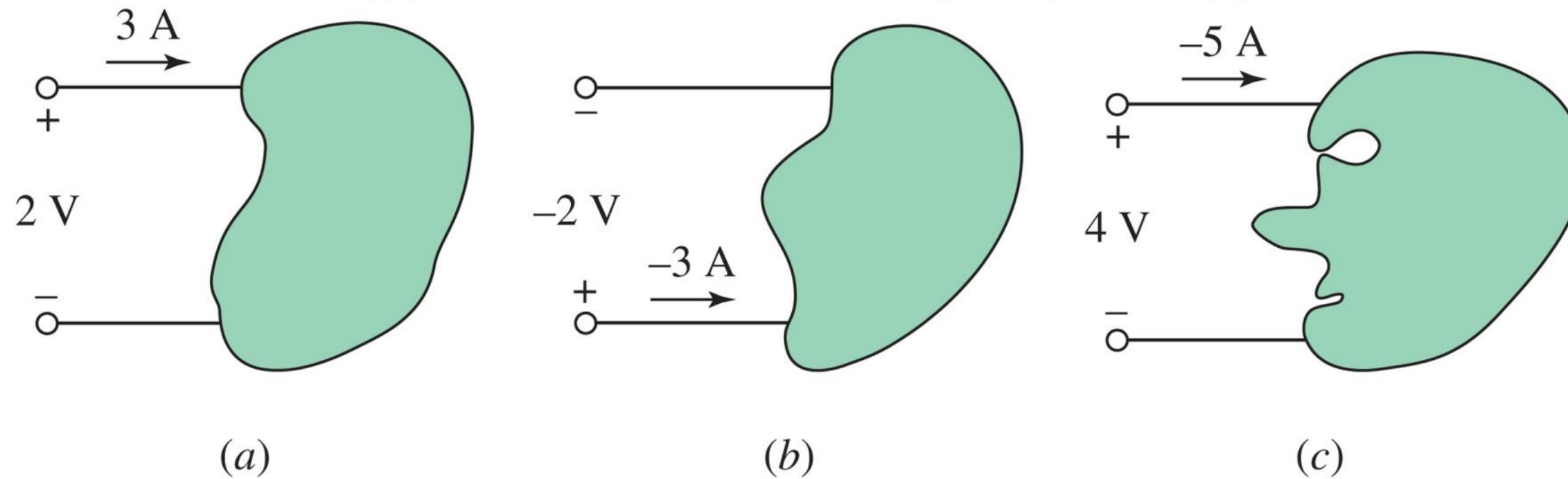


- How much power is absorbed by the three elements above?
- $P_a = +6\text{ W}$ ,  $P_b = +6\text{ W}$ ,  $P_c = -20\text{ W}$ .
- (Note: (c) is actually supplying power)

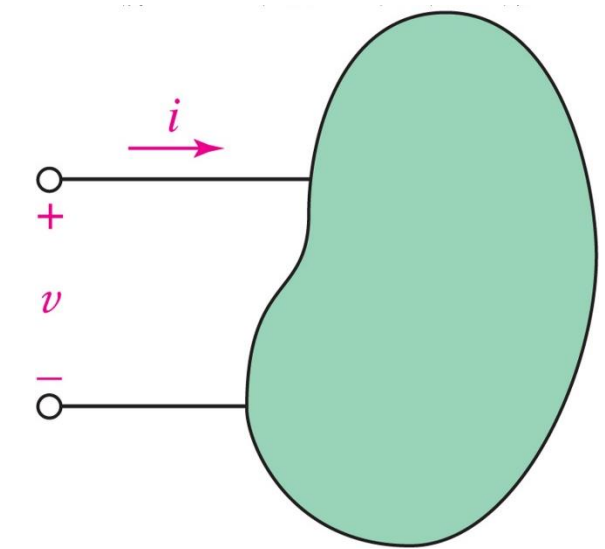- A circuit element usually has two terminals (sometimes three or more).
- The relationship between **the voltage  $v$**  across the terminals and the **current  $i$**  through the device defines **the circuit element model**.




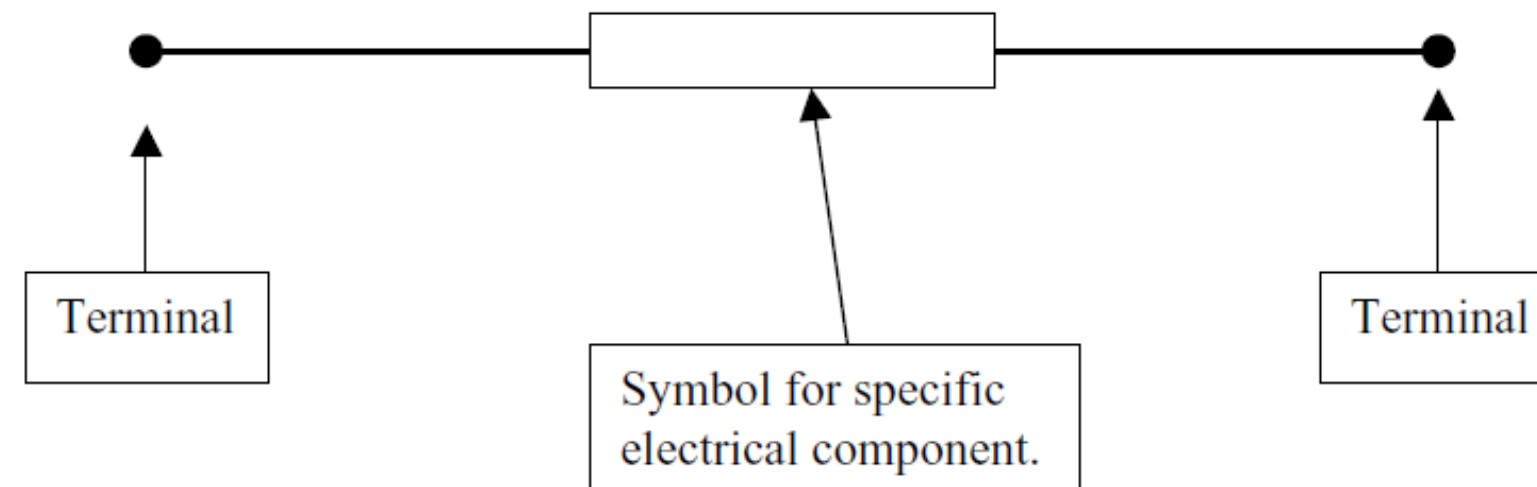- An arrangement into a network of several connected **two-terminal** electrical components.
- Each type of component will have its own symbol.



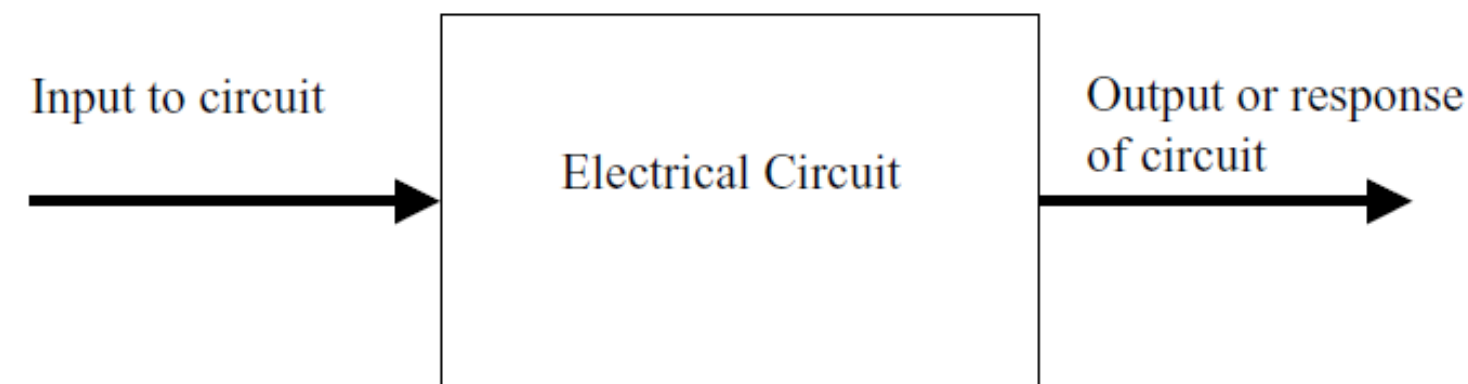
# What Is Circuit Analysis?

- Art of finding out how the unique circuit we are given responds to a particular input.
  - The input could be a **voltage** or a **current**, or maybe some **combination of voltages and currents**.
- The response of the circuit is the output.






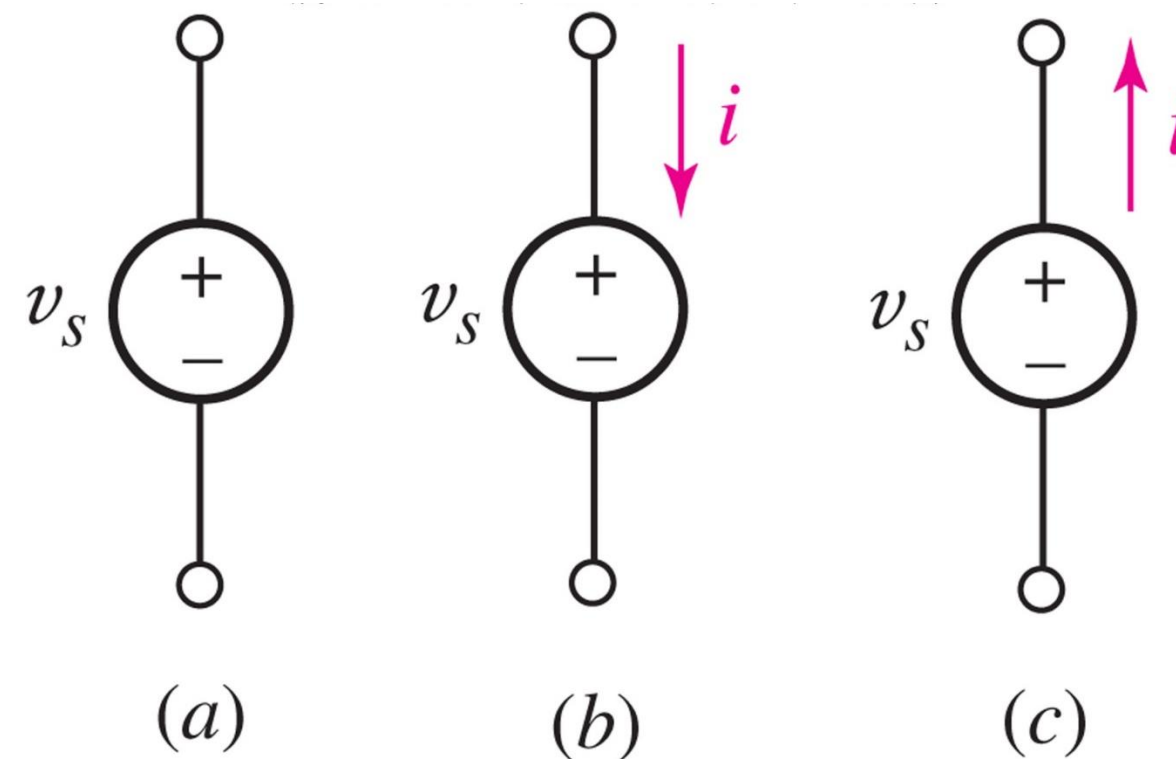
- An ideal voltage source is a circuit element that will **maintain the specified voltage  $v_s$**  across its terminals.
- The **current** will be determined by other circuit elements.



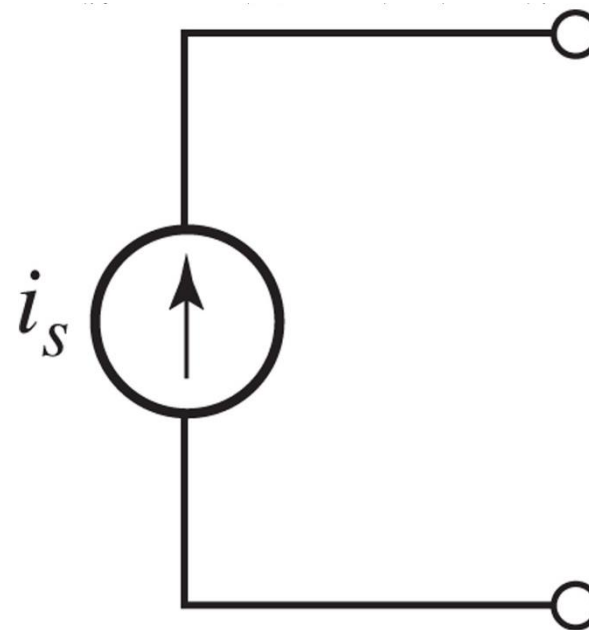- An ideal current source is a circuit element that **maintains the specified current flow  $i_s$**  through its terminals.
- The **voltage** is determined by other circuit elements.




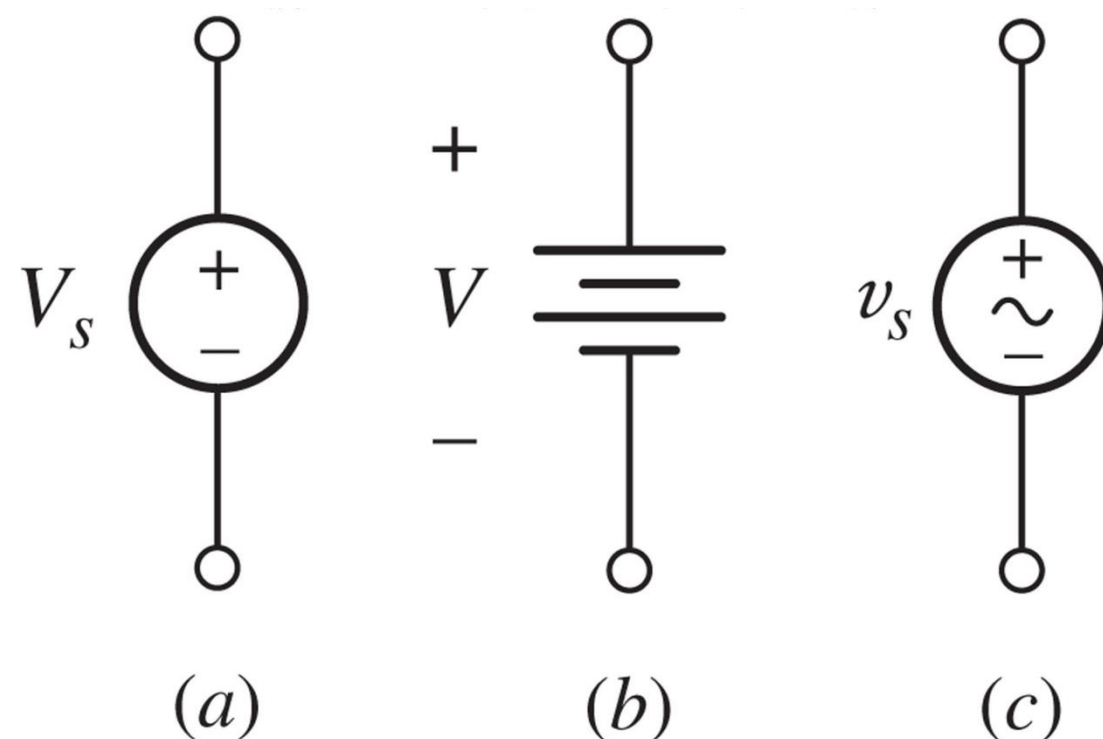- A voltage source is an *idealization* (no limit on current) and *generalization* (voltage can be time-varying) of a battery.
- A battery supplies a constant “dc” voltage  $V$  but in practice a battery has a maximum power.



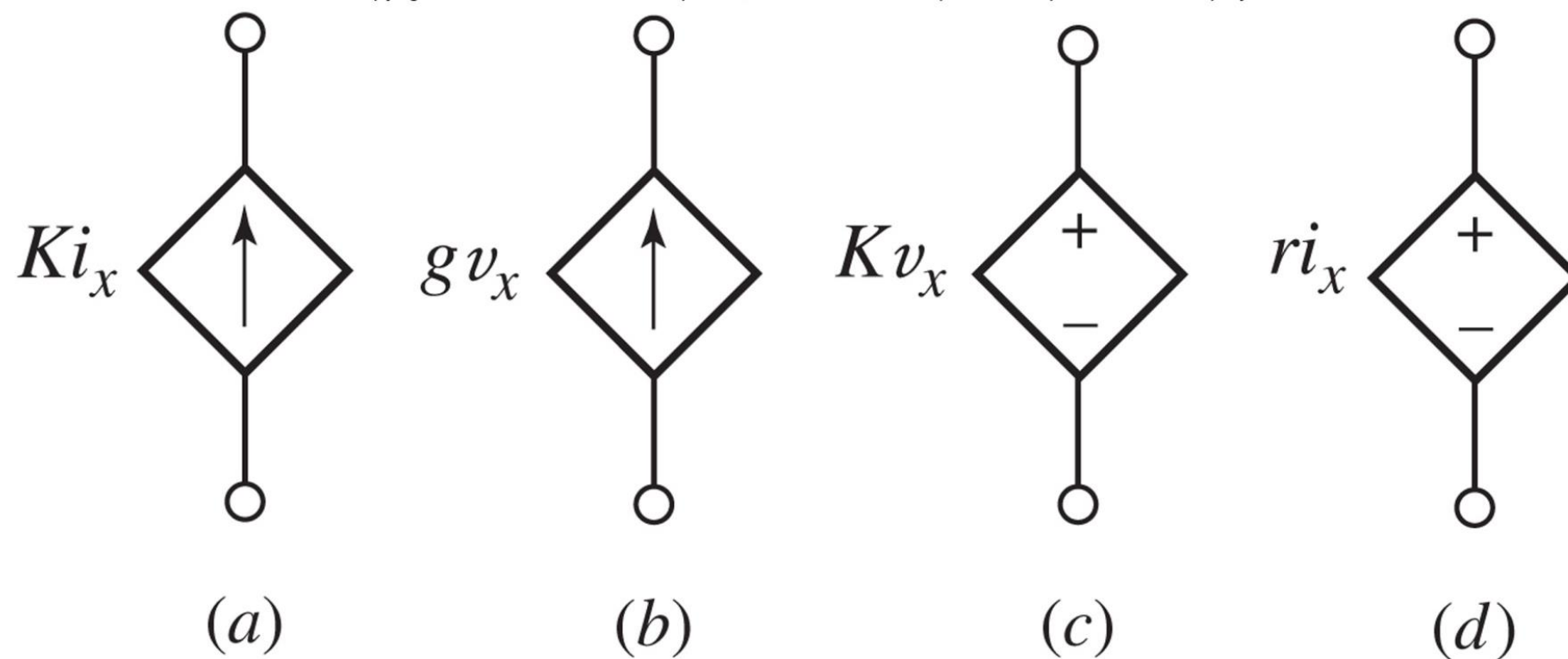
# Dependent Sources

- Dependent current sources (a) and (b) maintain a *current* specified by another circuit variable.
- Dependent voltage sources (c) and (d) maintain a *voltage* specified by another circuit variable.


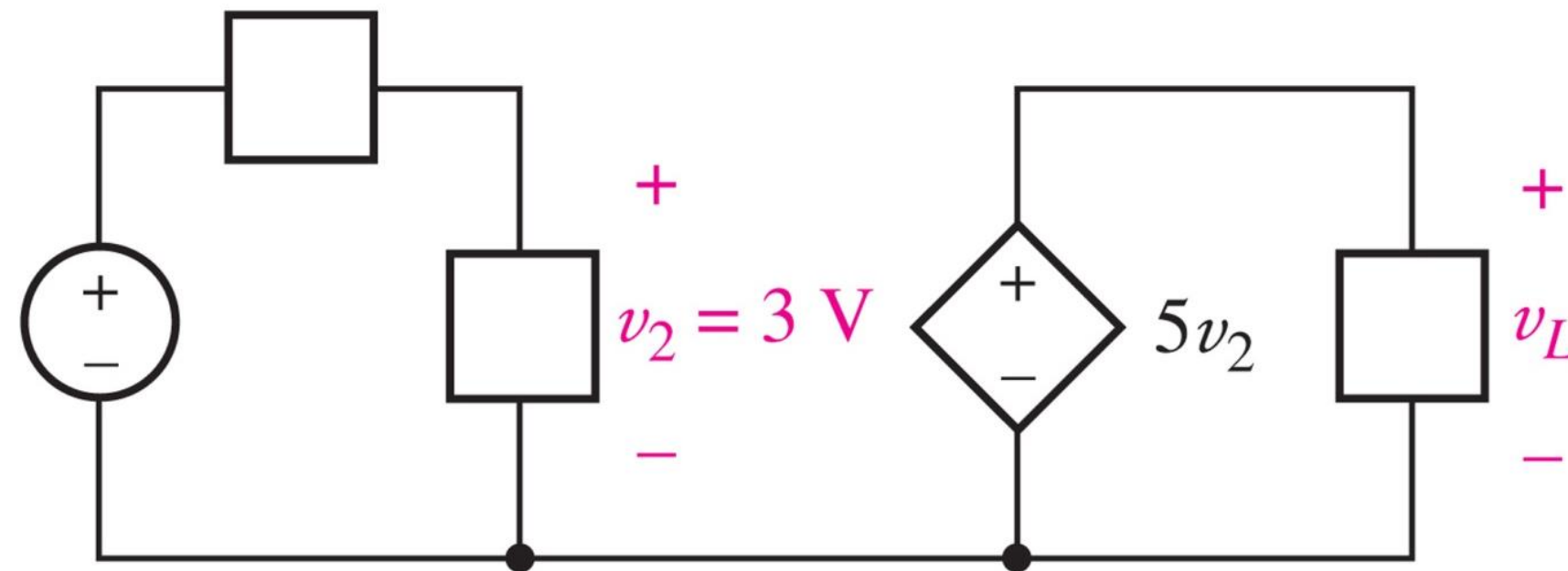
## Example: Dependent Sources

- Find the voltage  $v_L$  in the circuit below.




# Ohm's Law: Resistance

- A (linear) resistor is an element for which

$$v=iR$$

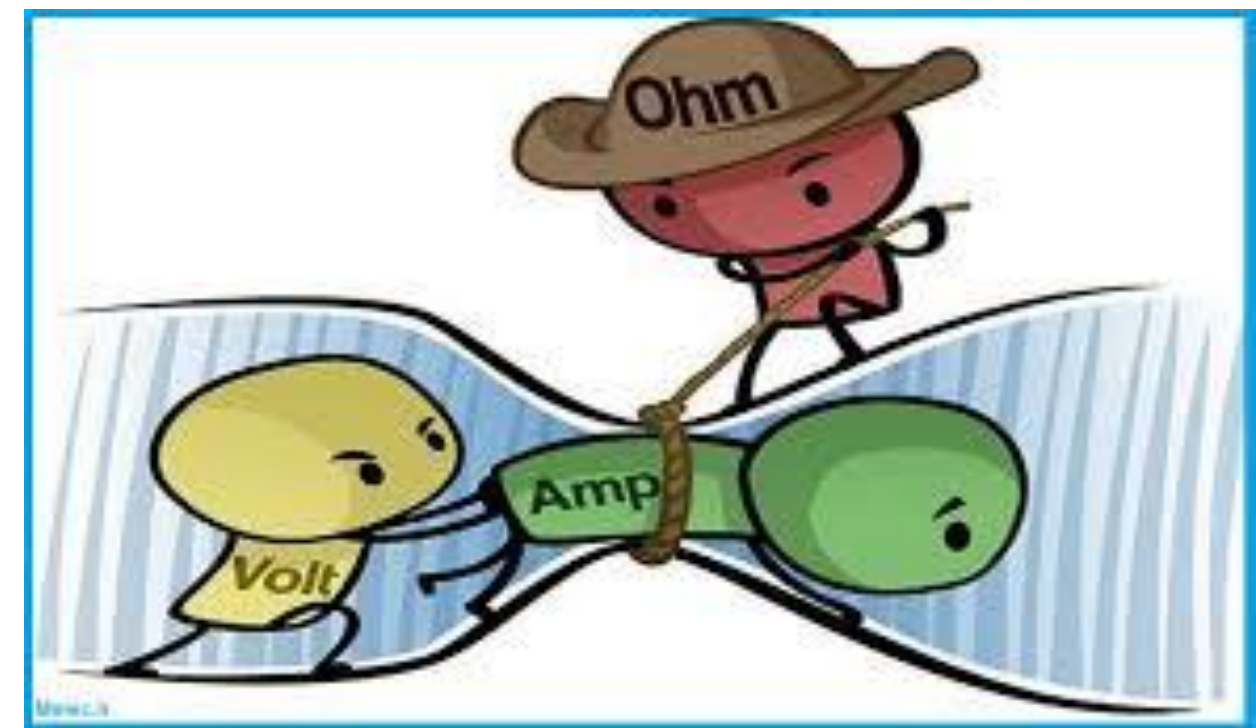
- where the constant  $R$  is a resistance.
- The equation is known as “**Ohm's Law.**”
- The unit of resistance is **ohm ( $\Omega$ )**.





# Resistors

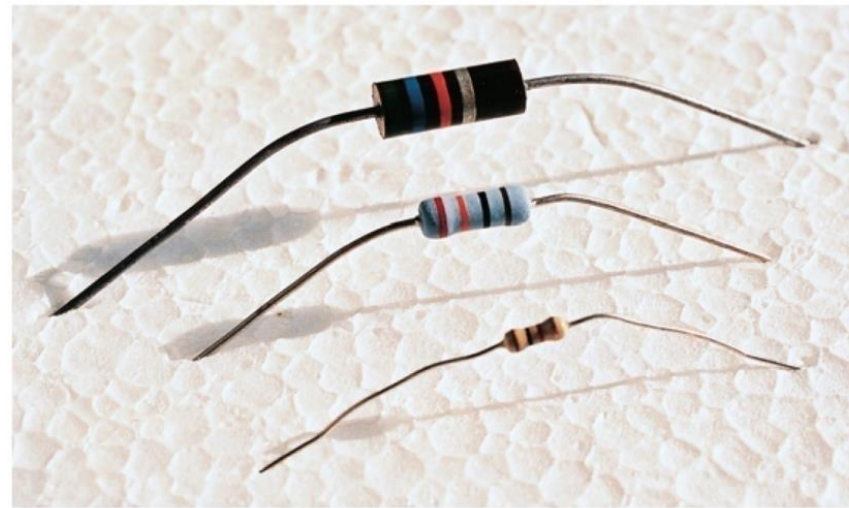
(a) typical resistors (b) power resistor  
(c) a 10 T $\Omega$  resistor (d) circuit symbol



(a)



(b)

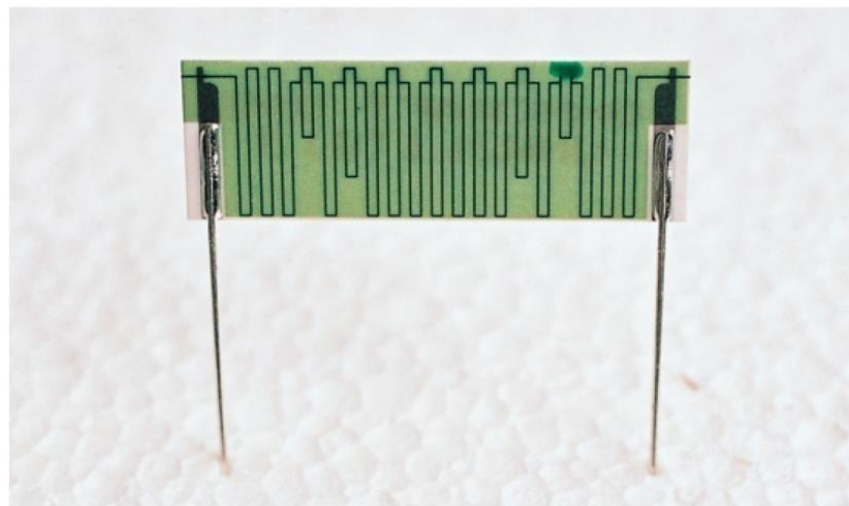


(c)



(d)
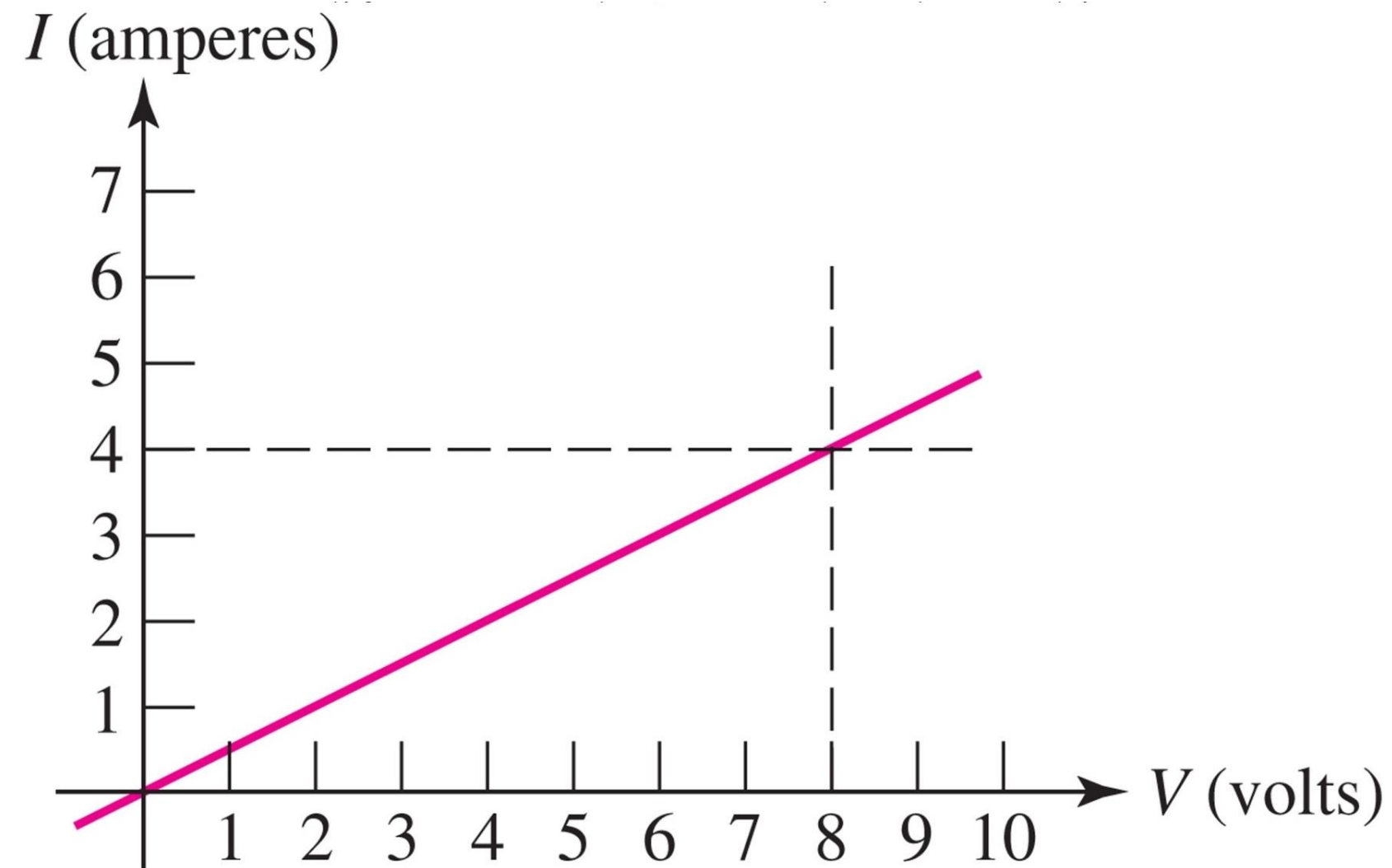
# The i-v Graph for a Resistor

- For a resistor, the plot of current versus voltage is a straight line:




- In this example, the slope is  $4 \text{ A} / 8 \text{ V}$  or  $0.5 \text{ } \Omega^{-1}$ .
- This is the graph for a **2 ohm** resistor.

- Resistors absorb power:
  - since  $v=iR$

$$p=vi = v^2/R = i^2R$$

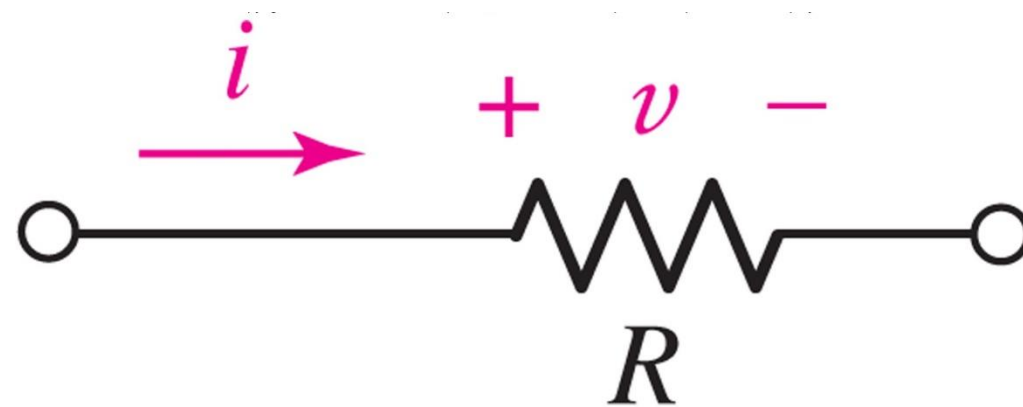- Positive power means the device is absorbing energy.
- Power is always positive for a resistor!



## Example: Resistor Power


- A  $560\ \Omega$  resistor is connected to a circuit which causes a current of  $42.4\ \text{mA}$  to flow through it.
- ✓ Calculate the voltage across the resistor and the power it is dissipating.

$$v = iR = (0.0424)(560) = 23.7\ \text{V}$$

$$p = i^2 R = (0.0424)^2(560) = 1.007\ \text{W}$$

- The resistance of a wire is determined by the resistivity of the conductor as well as the geometry:

$$R = \rho l / A$$

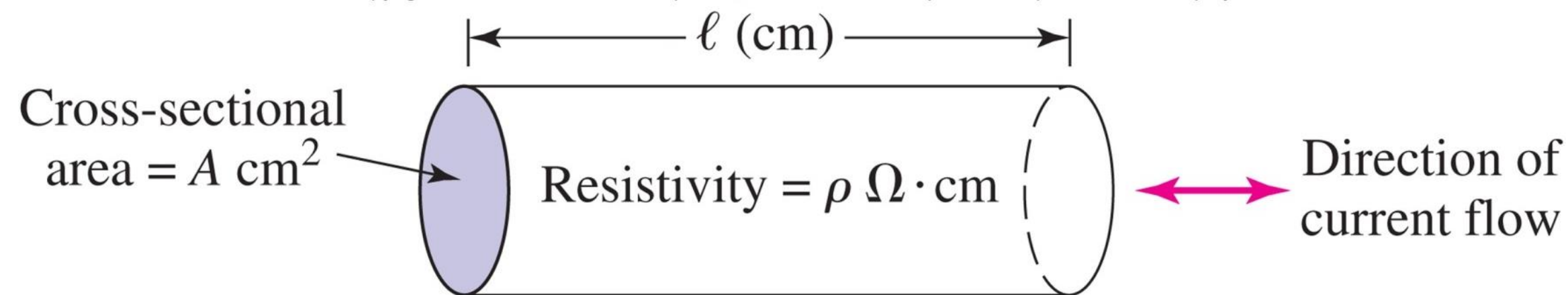

[In most cases, the resistance of wires can be assumed to be 0 ohms.]



- We sometimes prefer to work with *the reciprocal of resistance* ( $1/R$ ), which is called conductance (symbol  $G$ , unit siemens (S)).
- A resistor  $R$  has conductance  $G=1/R$ .
- The  $i$ - $v$  equation (i.e. Ohm's law) can be written as


$$i=Gv$$


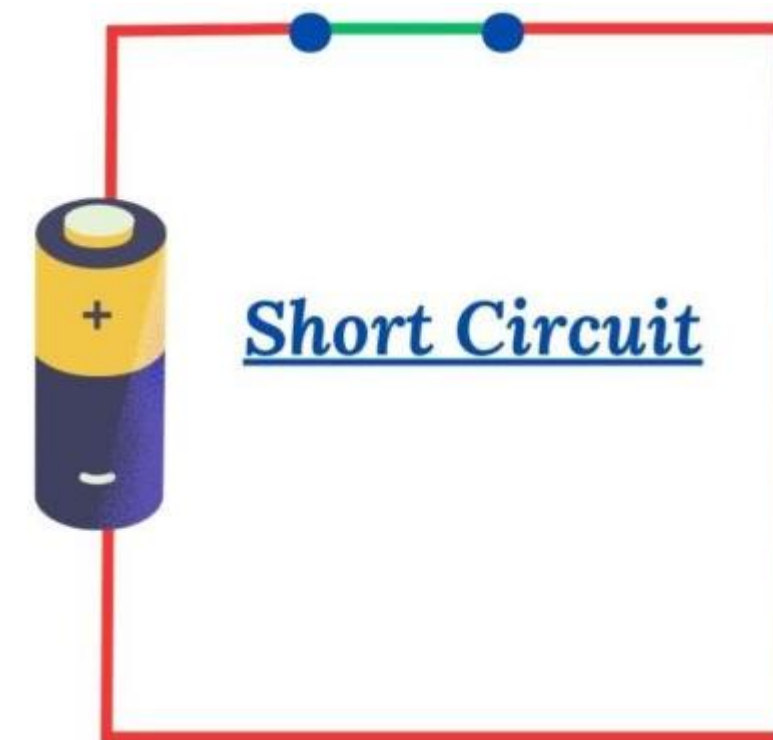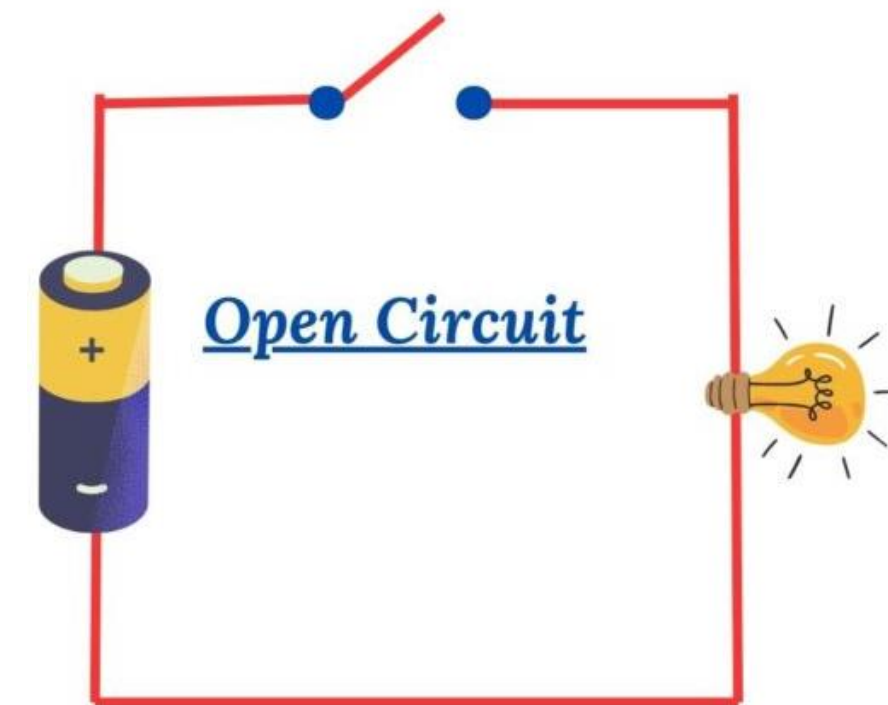
# Open and Short Circuits

- An **open circuit** between A and B means  $i=0$ .
- *Voltage across* an open circuit: **any value**.
- An open circuit is equivalent to  $R = \infty \Omega$ .
- A **short circuit** between A and B means  $v=0$ .
- *Current through* a short circuit: **any value**.
- A short circuit is equivalent to  $R = 0 \Omega$ .



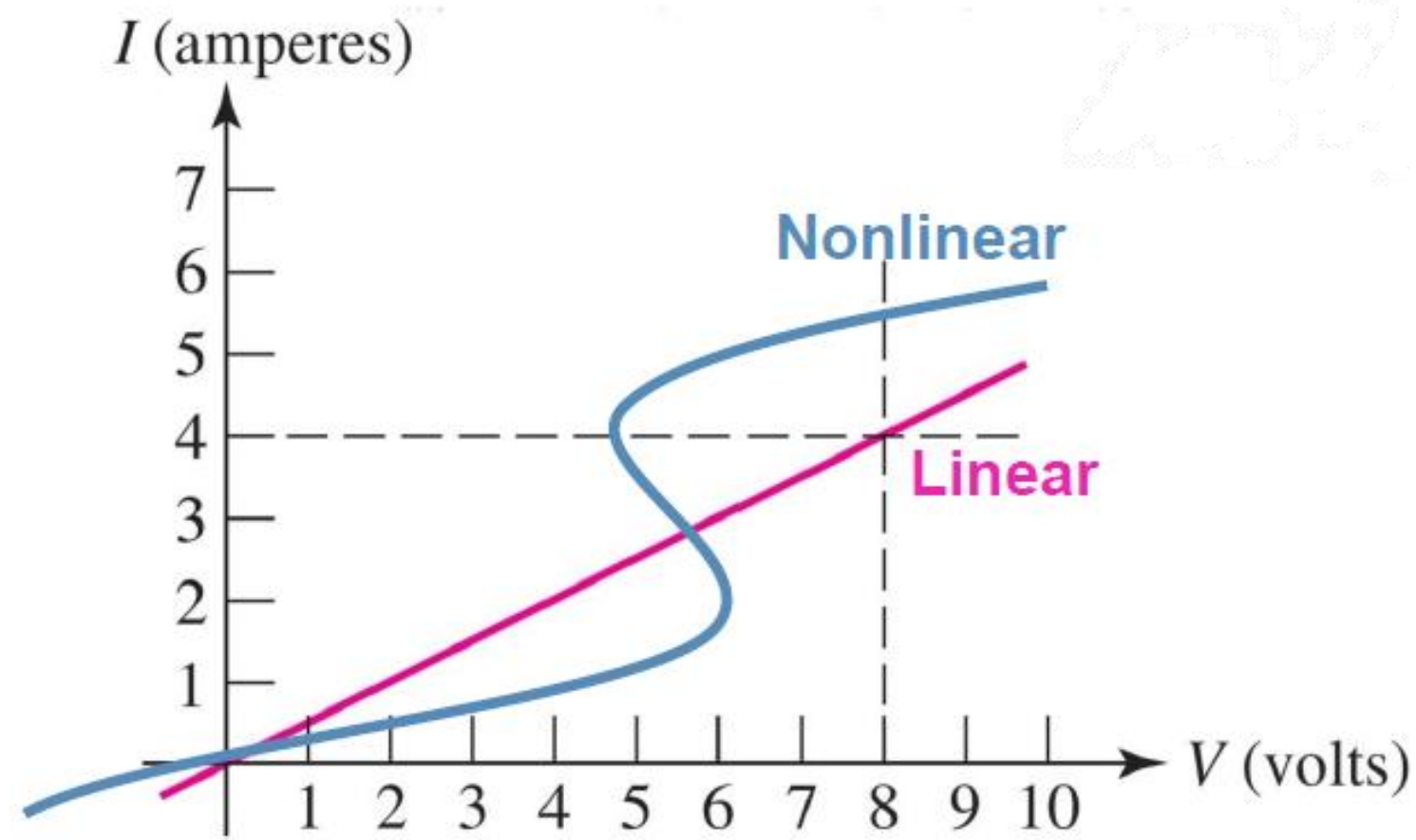

Linear function:

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

$$f(ax) = af(x)$$

Linear resistance:


$$v = f(i) = 2i$$

Nonlinear resistance:

$$v = f(i) = 50i + 0.5i^3$$
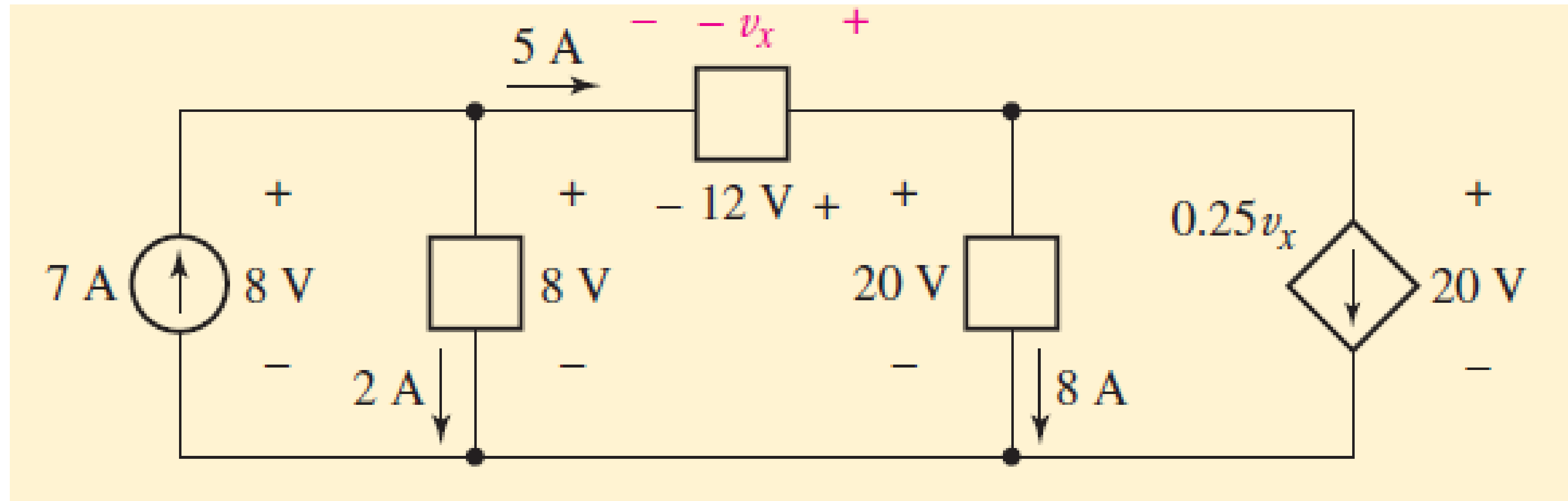
# Practice1





Find the power *absorbed* by each element in the circuit



Ans: (left to right)  $-56\text{ W}$ ;  $16\text{ W}$ ;  $-60\text{ W}$ ;  $160\text{ W}$ ;  $-60\text{ W}$ .
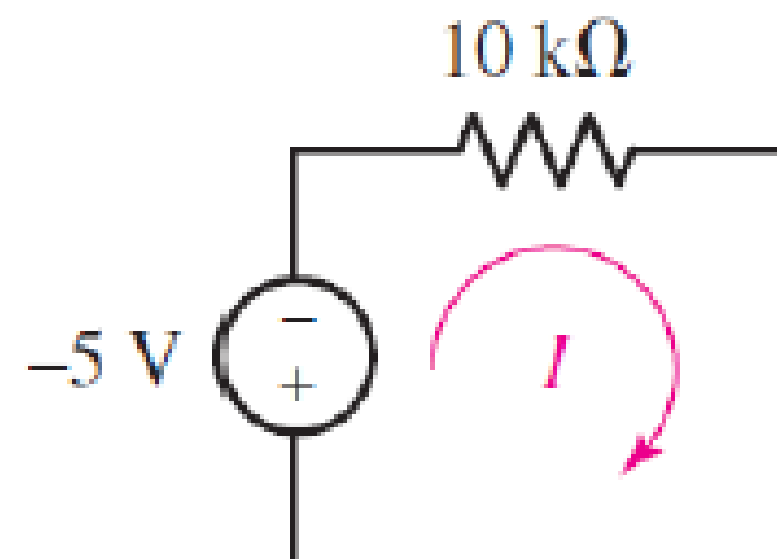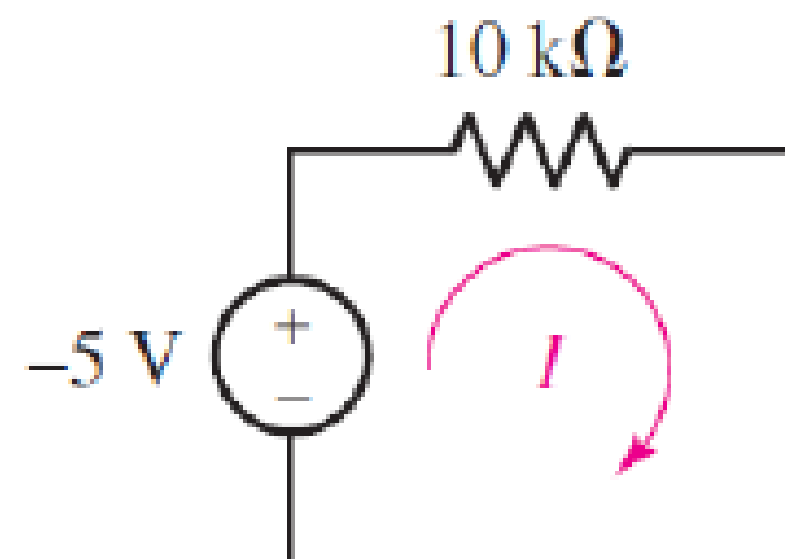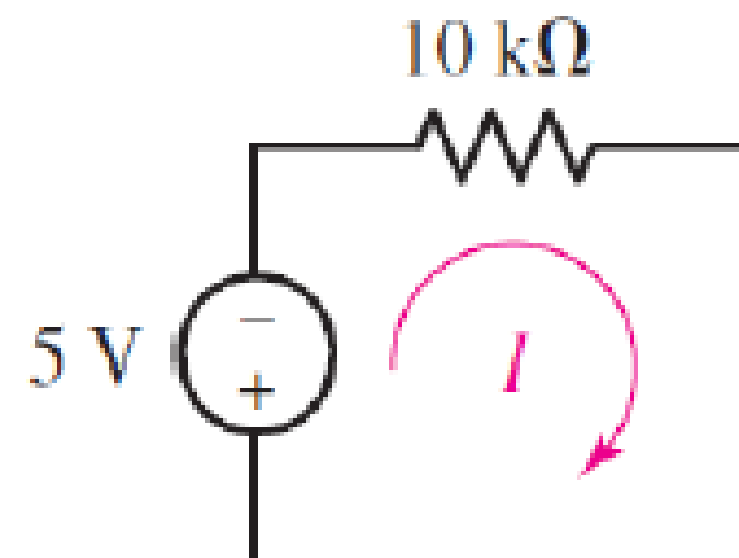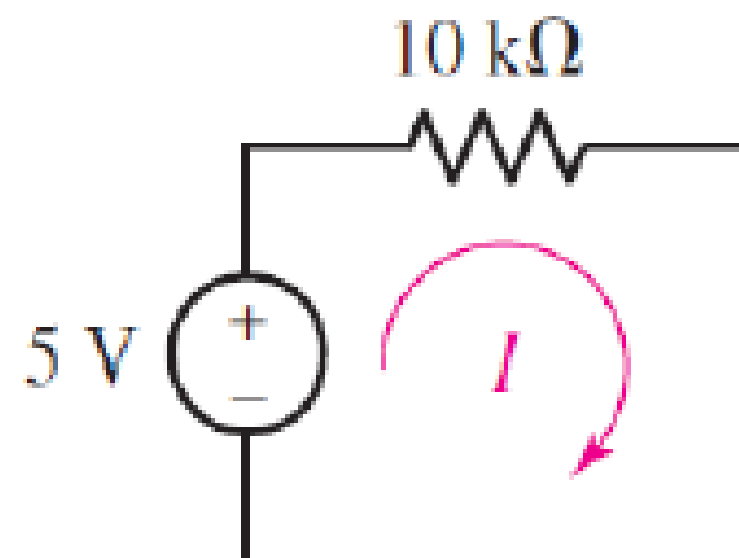
## Practice 2


For each of the circuits, find the current  $I$  and compute the power absorbed by the resistor.



show that:

$$V_{R2} = V_S \cdot \frac{R_2}{R_1 + R_2}$$

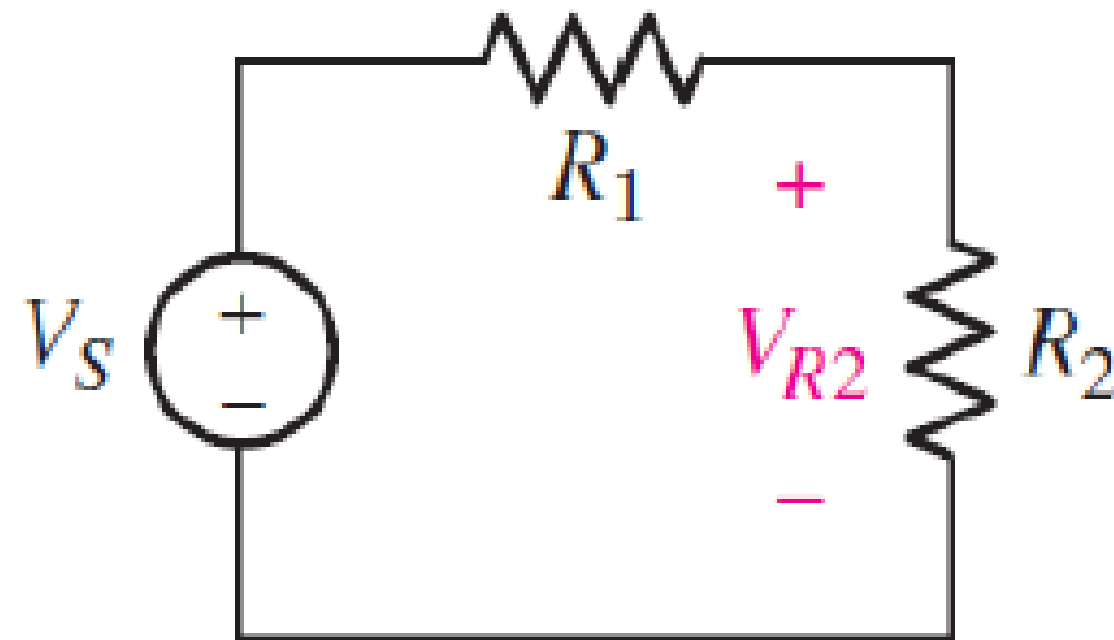You may assume the same current flows through each element (a requirement of charge conservation).





# Thanks

---