



دانشگاه صنعتی امیر کبیر  
( پلی تکنیک تهران )

# Electrical and Electronic Circuits

## chapter 2 : Voltage and Current Laws

Afarghadan@aut.ac.ir

عظیم فرقدان 

مهر ۱۴۰۳

# Objectives of the Lecture

- Present Kirchhoff's Current and Voltage Laws.
- Demonstrate how these laws can be used to find currents and voltages in a circuit.
- Explain how these laws can be used in conjunction with Ohm's Law.

# Nodes, Paths, Loops, Branches

- these two networks are **equivalent**
- there are **three nodes** and **five branches**

- **Node**

- point at which 2+ elements have a common connection
  - e.g., node 1, node 2, node 3

- **Branch**



- a single path in a network; contains one element and the nodes at the 2 ends
  - e.g.,  $1 \rightarrow 2$ ,  $1 \rightarrow 3$ ,  $3 \rightarrow 2$

- **Path**


- a route through a network, through nodes that never repeat
  - e.g.,  $1 \rightarrow 3 \rightarrow 2$ ,  $1 \rightarrow 2 \rightarrow 3$

- **Loop**

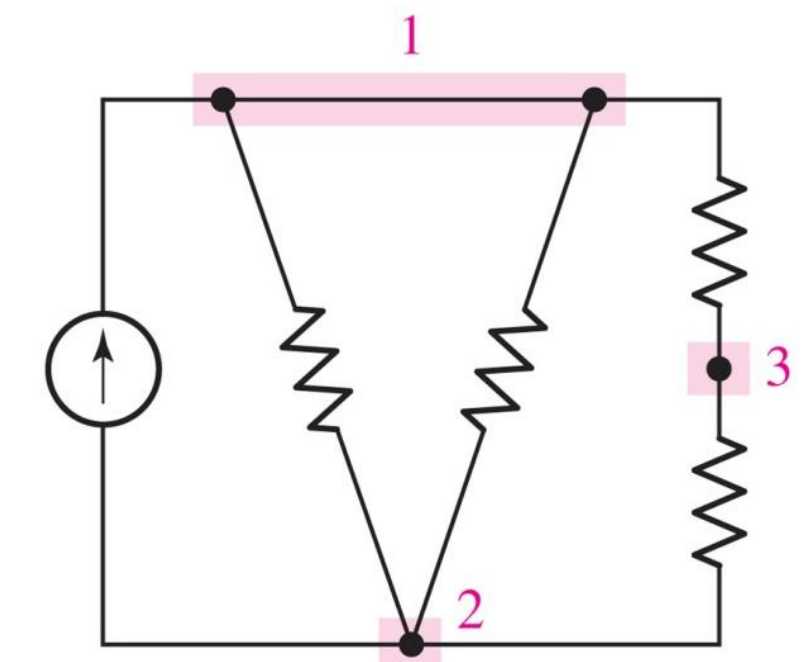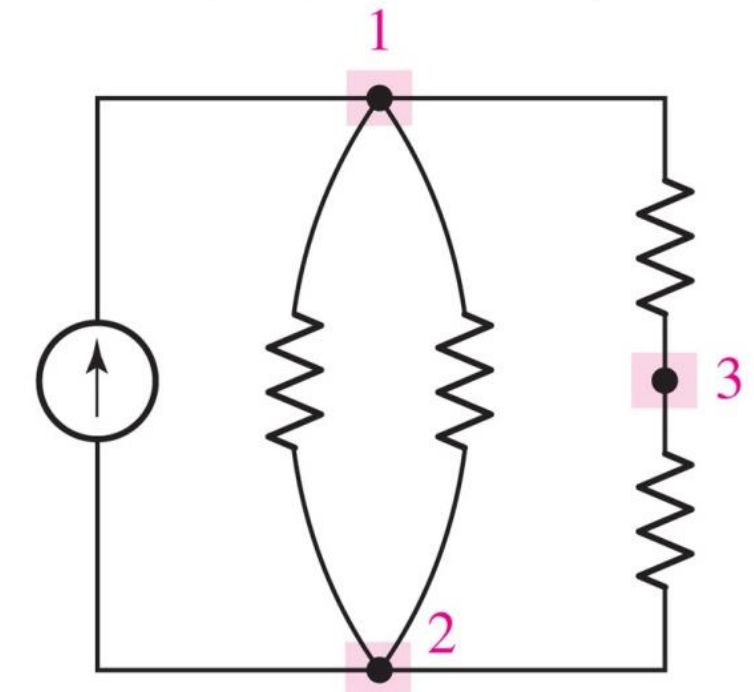- a path that starts & ends on the same node
  - e.g.,  $3 \rightarrow 1 \rightarrow 2 \rightarrow 3$



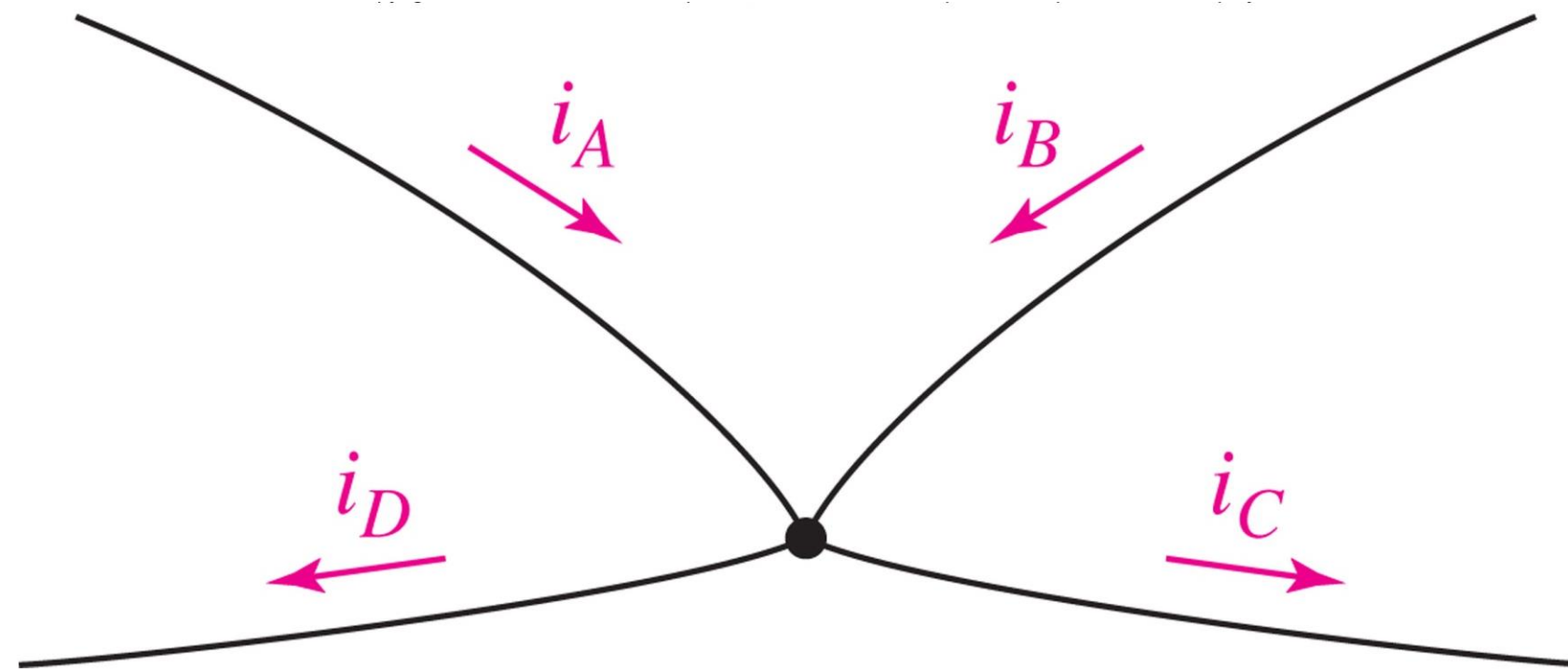KCL: The algebraic sum of the currents entering any node is zero.



$$i_A + i_B + (-i_C) + (-i_D) = 0$$

- Current *IN* is zero:


$$i_A + i_B + (-i_C) + (-i_D) = 0$$

- Current *OUT* is zero:

$$(-i_A) + (-i_B) + i_C + i_D = 0$$


- Current *IN*=*OUT*:

$$i_A + i_B = i_C + i_D$$

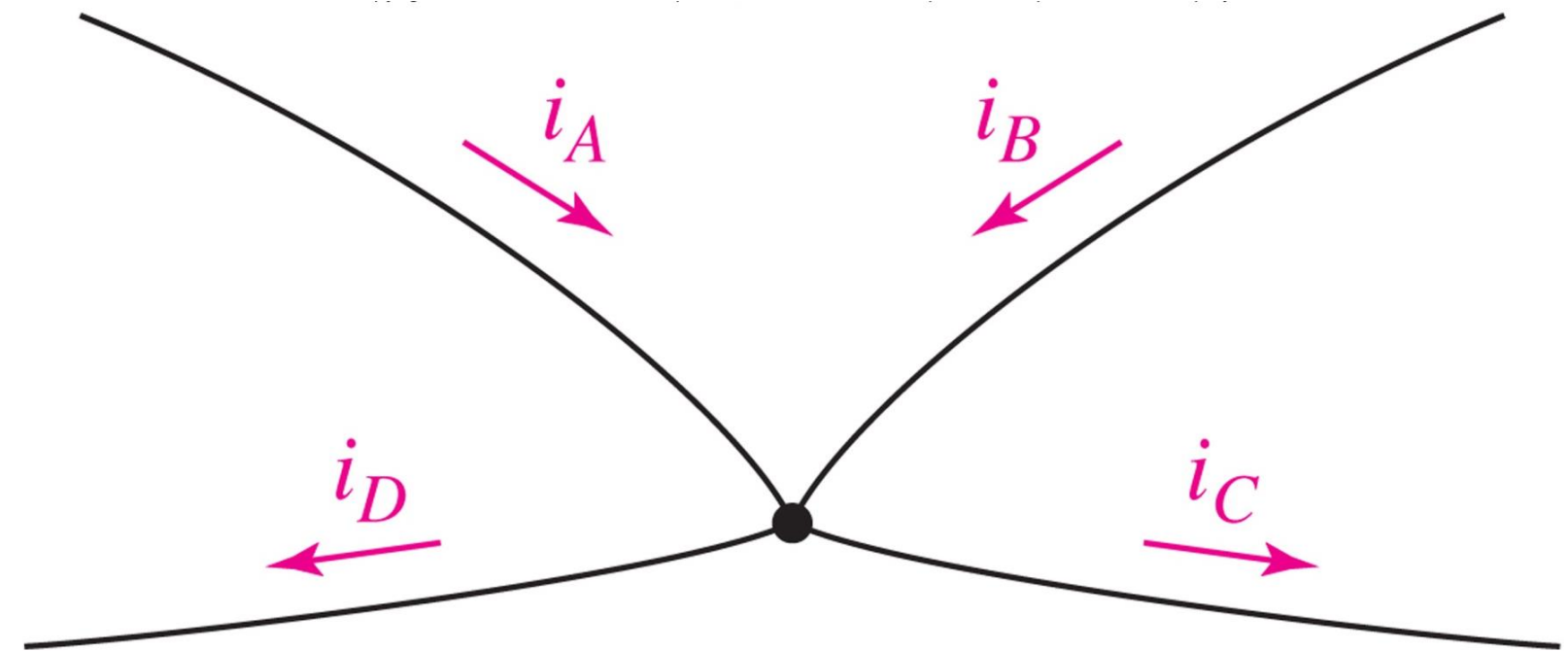
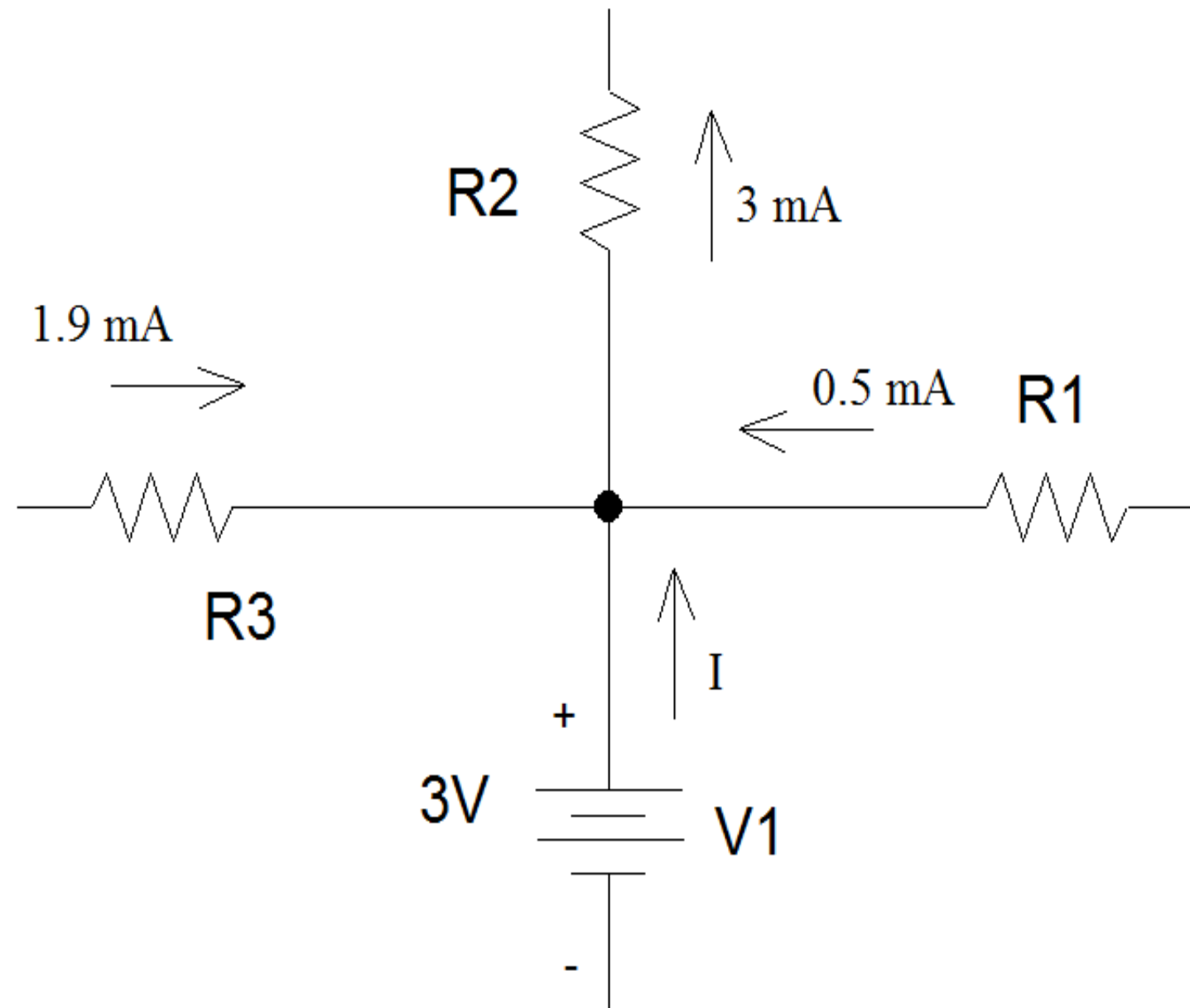
# Example

- Determine  $I$ , the current flowing out of the voltage source.



Use KCL


$1.9 \text{ mA} + 0.5 \text{ mA} + I$  are  
entering the node.  
 $3 \text{ mA}$  is leaving the node.

$$\begin{aligned} 1.9 \text{ mA} + 0.5 \text{ mA} + I &= 3 \text{ mA} \\ I &= 3 \text{ mA} - (1.9 \text{ mA} + 0.5 \text{ mA}) \\ I &= 0.6 \text{ mA} \end{aligned}$$

$V1$  is supplying power.
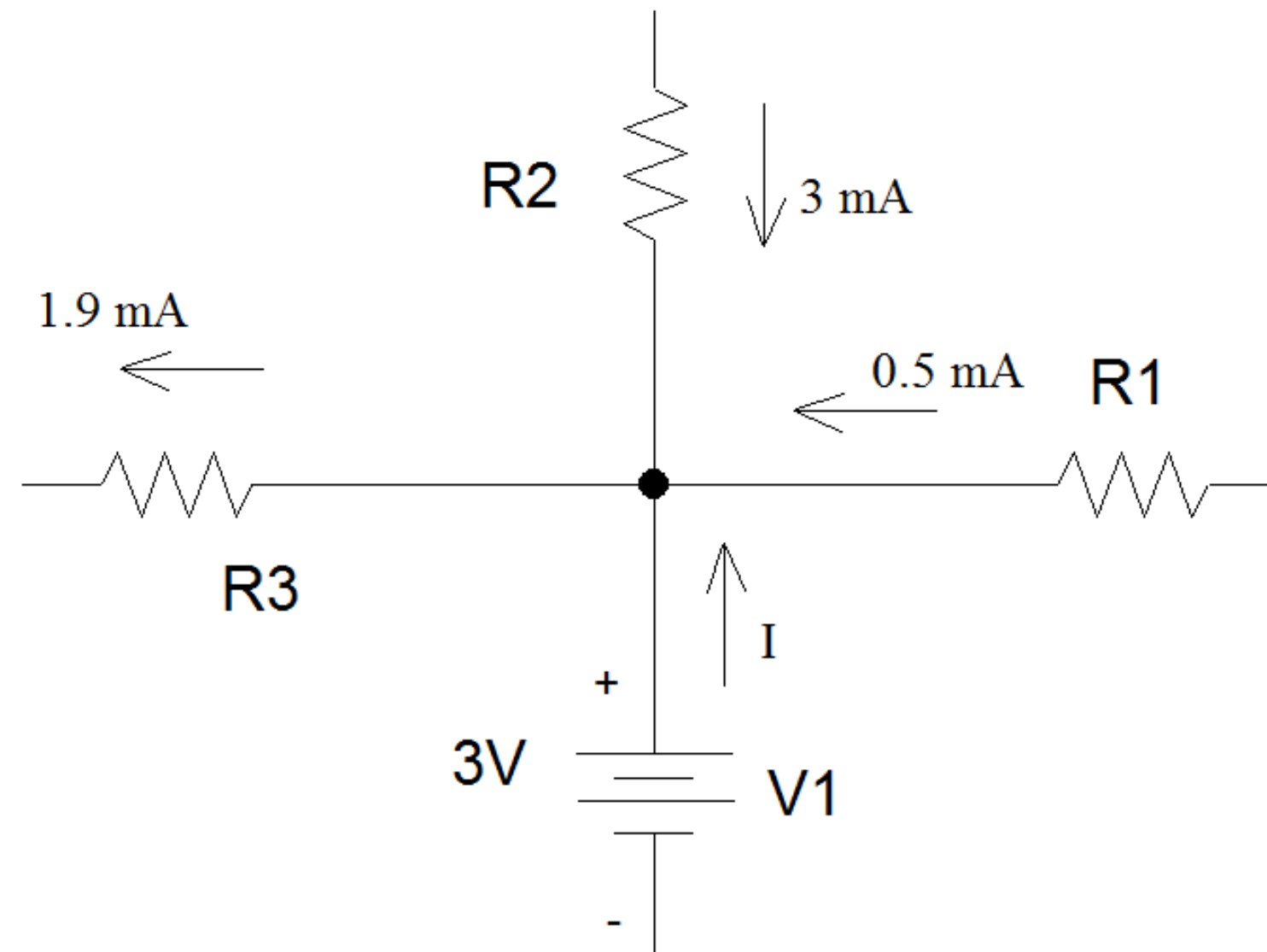
# Example

- Suppose the current through R2 was entering the node and the current through R3 was leaving the node.



Use KCL

3 mA + 0.5 mA + I are  
entering the node.

1.9 mA is leaving the node.

$$3mA + 0.5mA + I = 1.9mA$$

$$I = 1.9mA - (3mA + 0.5mA)$$


$$I = -1.6mA$$

V1 is absorbing power.
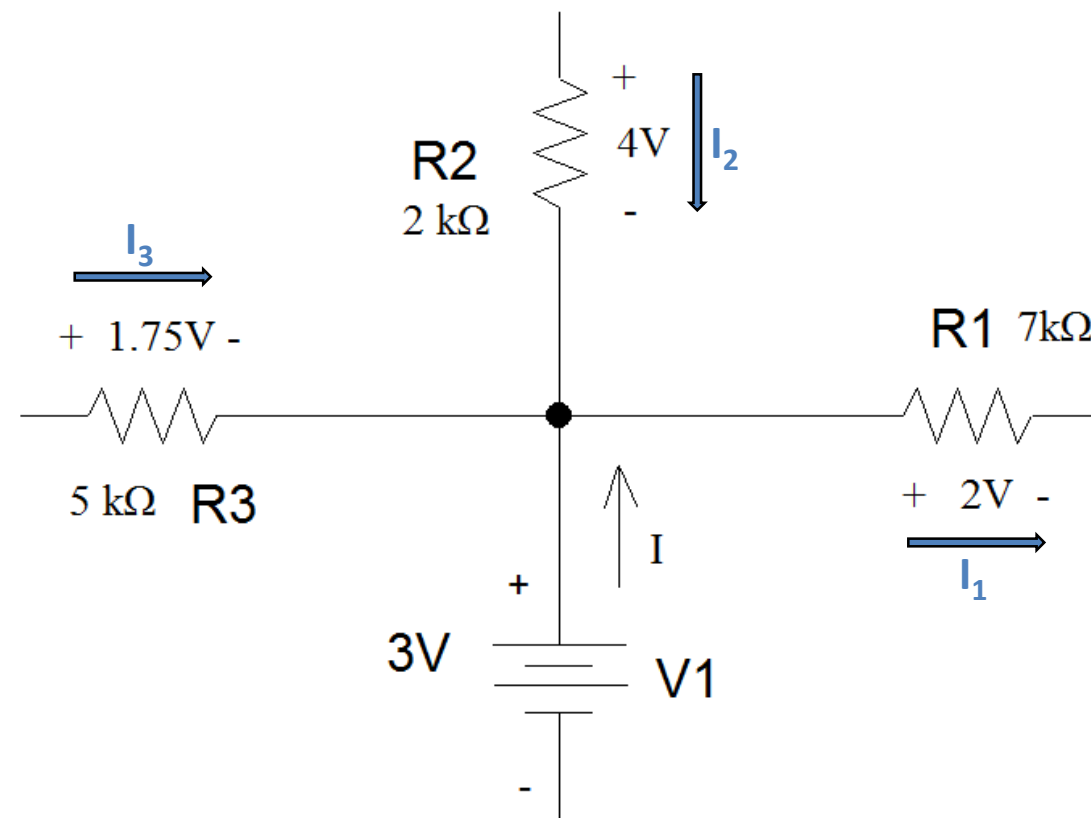
# Example

- If voltage drops are given instead of currents,

you need to apply **Ohm's Law** to determine the current flowing through each of the resistors before you can find the current flowing out of the voltage supply.



$$I_1 = 2V / 7k\Omega = 0.286mA$$

$$I_2 = 4V / 2k\Omega = 2mA$$

$$I_3 = 1.75V / 5k\Omega = 0.35mA$$

$$I_2 + I_3 + I = I_1$$


$$2mA + 0.35mA + I = 0.286mA$$

$$I = 0.286mA - 2.35mA = -2.06mA$$


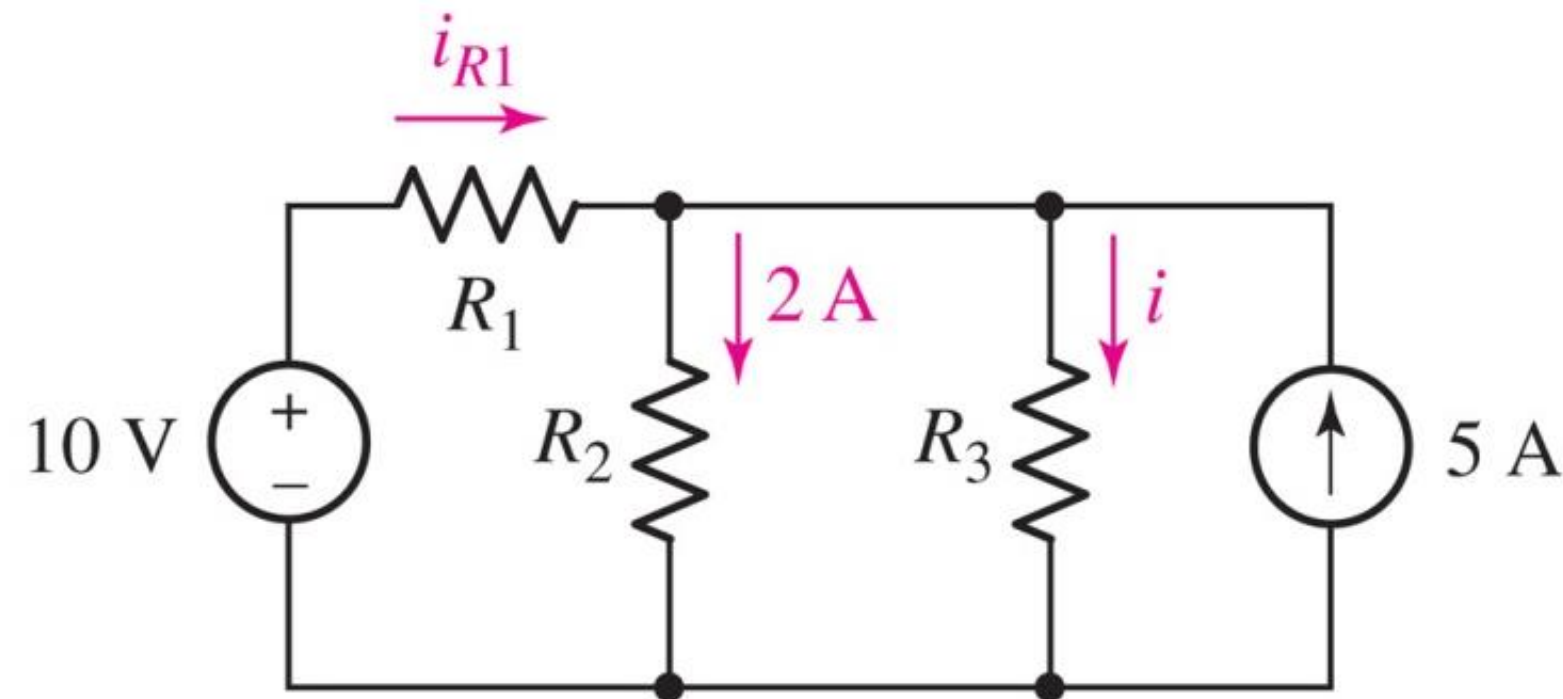
## Example of KCL Application


- Find the current through resistor  $R_3$  if it is known that the voltage source supplies a current of 3 A.



*Answer:  $i = 6\text{ A}$*
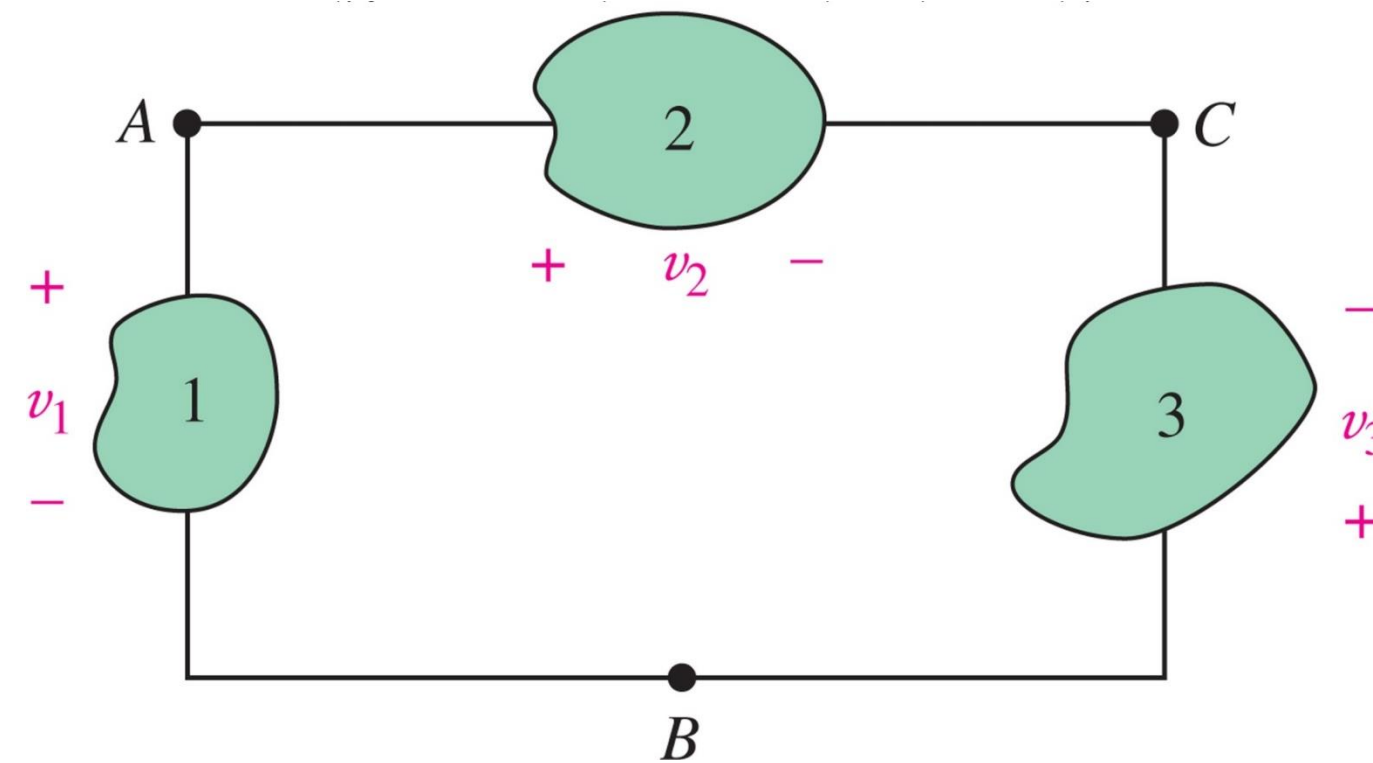
# Kirchhoff's Voltage Law

**KVL:** The algebraic sum of the voltages around any closed path is zero.



$$(-v_1) + v_2 + (-v_3) = 0$$

# KVL: Alternative Forms

- Sum of **DROPS** is zero (clockwise from B):


$$(-v_1) + v_2 + (-v_3) = 0$$

- Sum of **RISES** is zero (clockwise from B):

$$v_1 + (-v_2) + v_3 = 0$$


- Two paths, same voltage (A to B):

$$v_1 = v_2 + (-v_3)$$

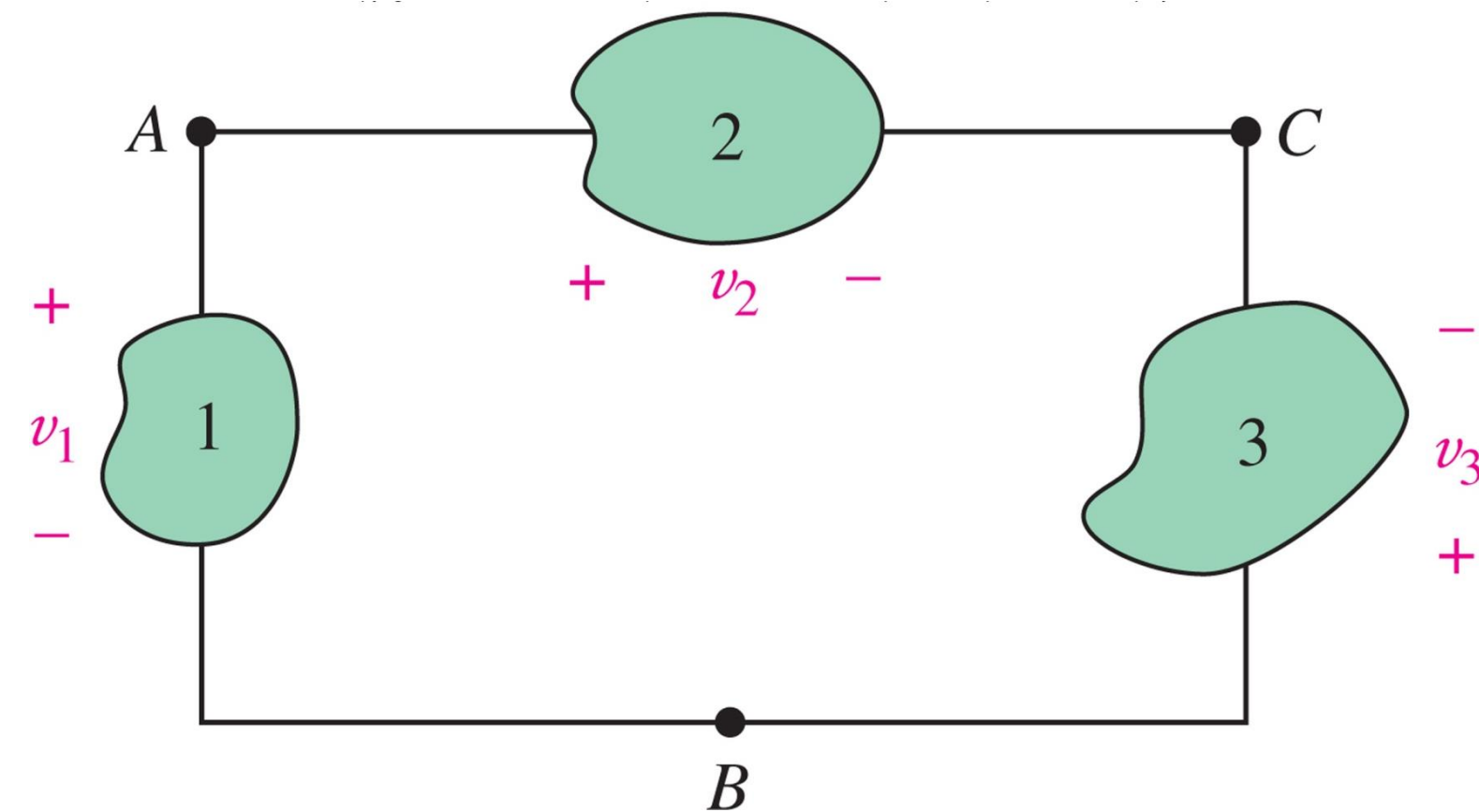
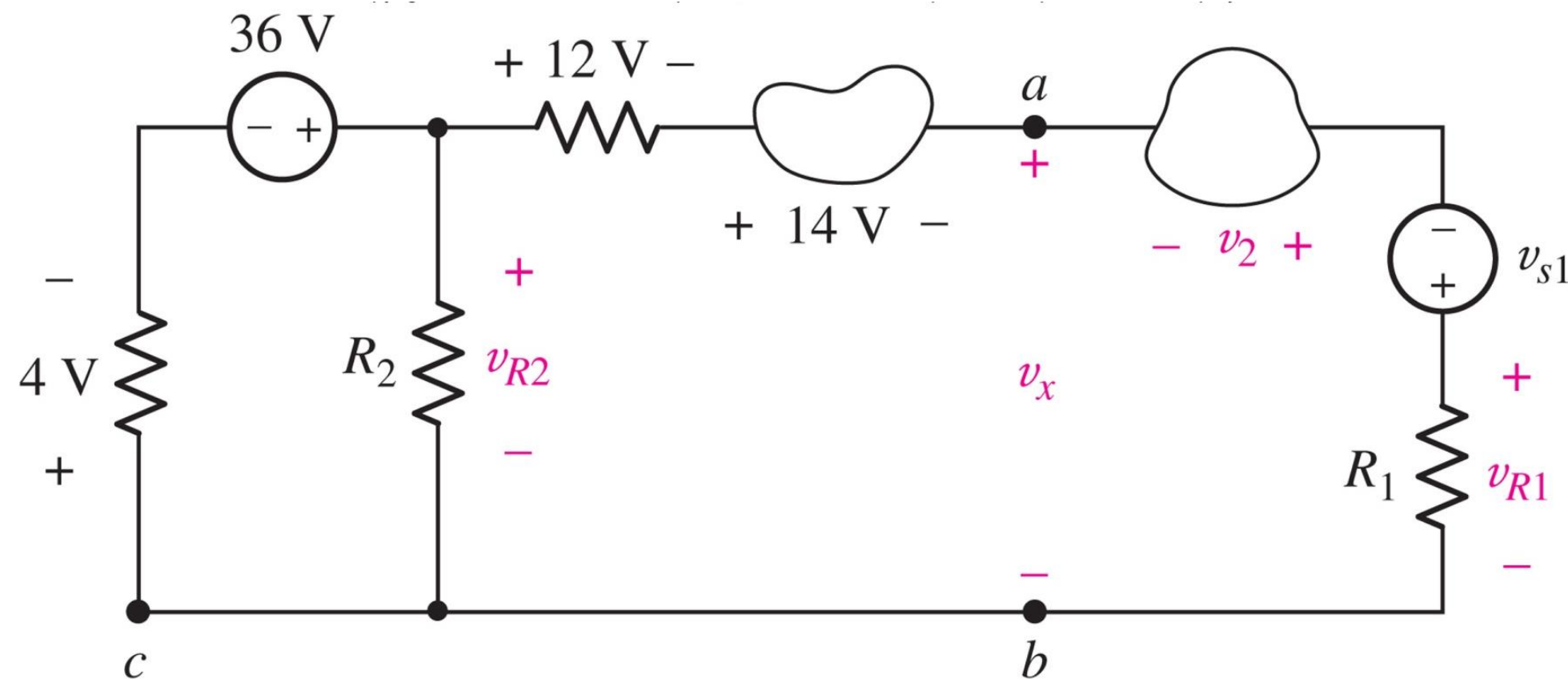
## Example: Applying KVL

- Find  $v_{R2}$  (the voltage across  $R_2$ ) and the voltage  $v_x$ .



$$4 - 36 + v_{R2} = 0$$


$$\text{Answer: } v_{R2} = 32$$

$$+4 - 36 + 12 + 14 + v_x = 0$$

$$\text{Answer: } v_x = 6 \text{ V.}$$


$$-32 + 12 + 14 + v_x = 0$$

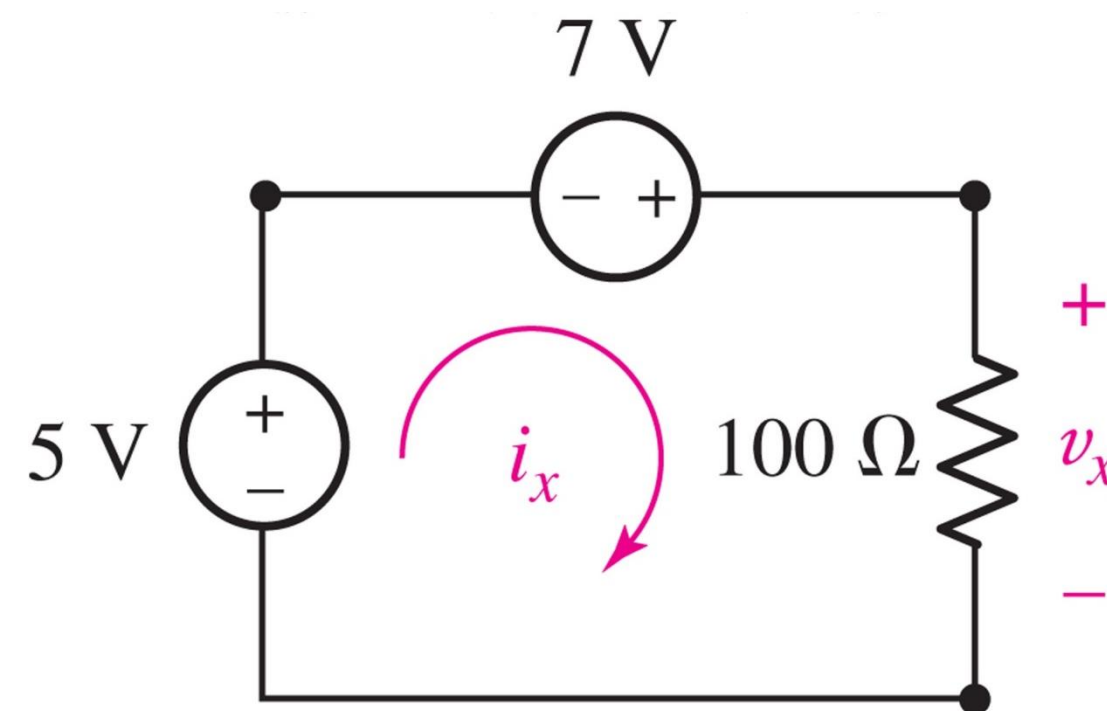Example: find the current  $i_x$  and the voltage  $v_x$



*Answer:  $v_x = 12\text{ V}$  and  $i_x = 120\text{ mA}$*

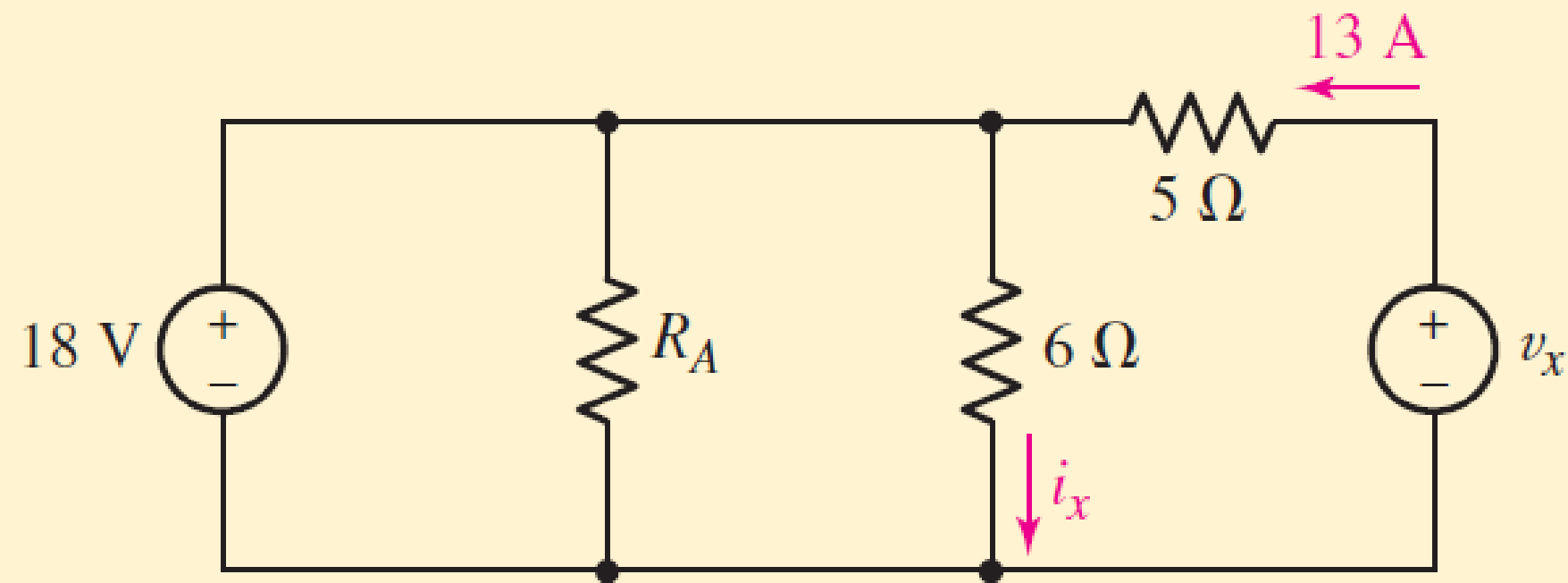3.1 Count the number of branches and nodes in the circuit in Fig. 3.4. If  $i_x = 3$  A and the 18 V source delivers 8 A of current, what is the value of  $R_A$ ? (*Hint: You need Ohm's law as well as KCL.*)





■ **FIGURE 3.4**

---



Ans: 5 branches, 3 nodes, 1  $\Omega$ .

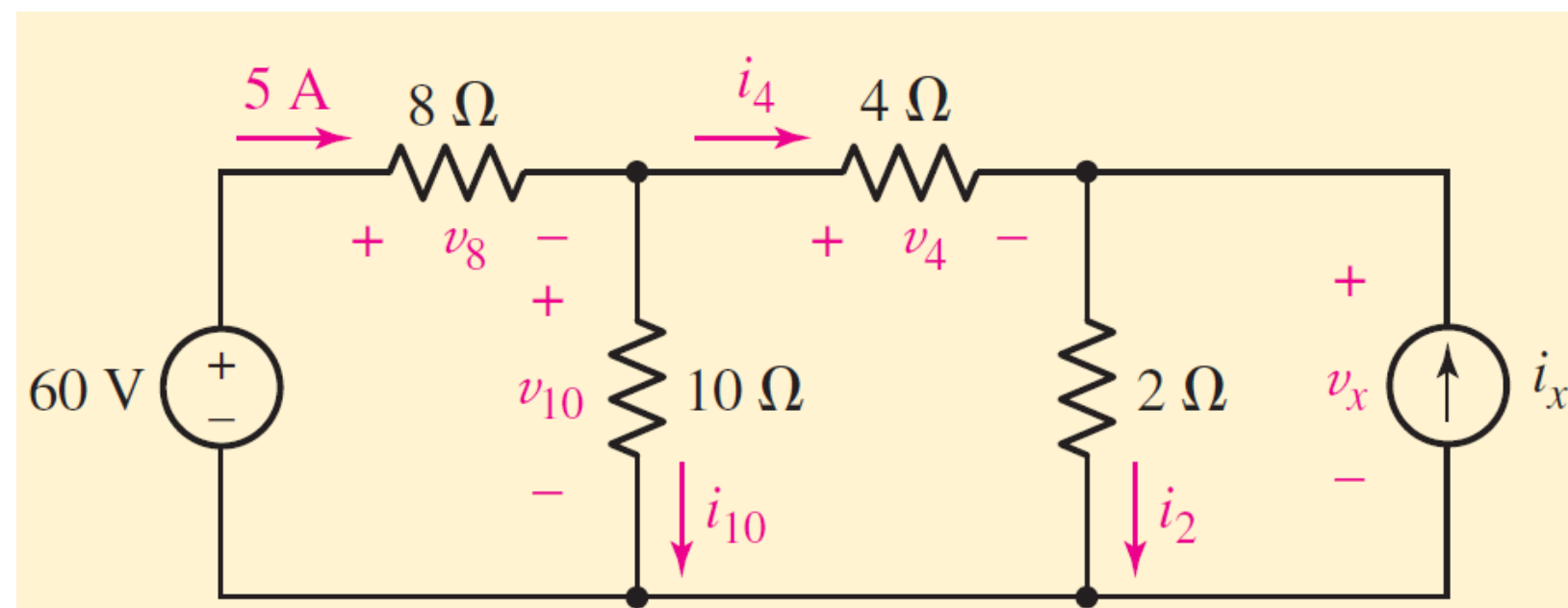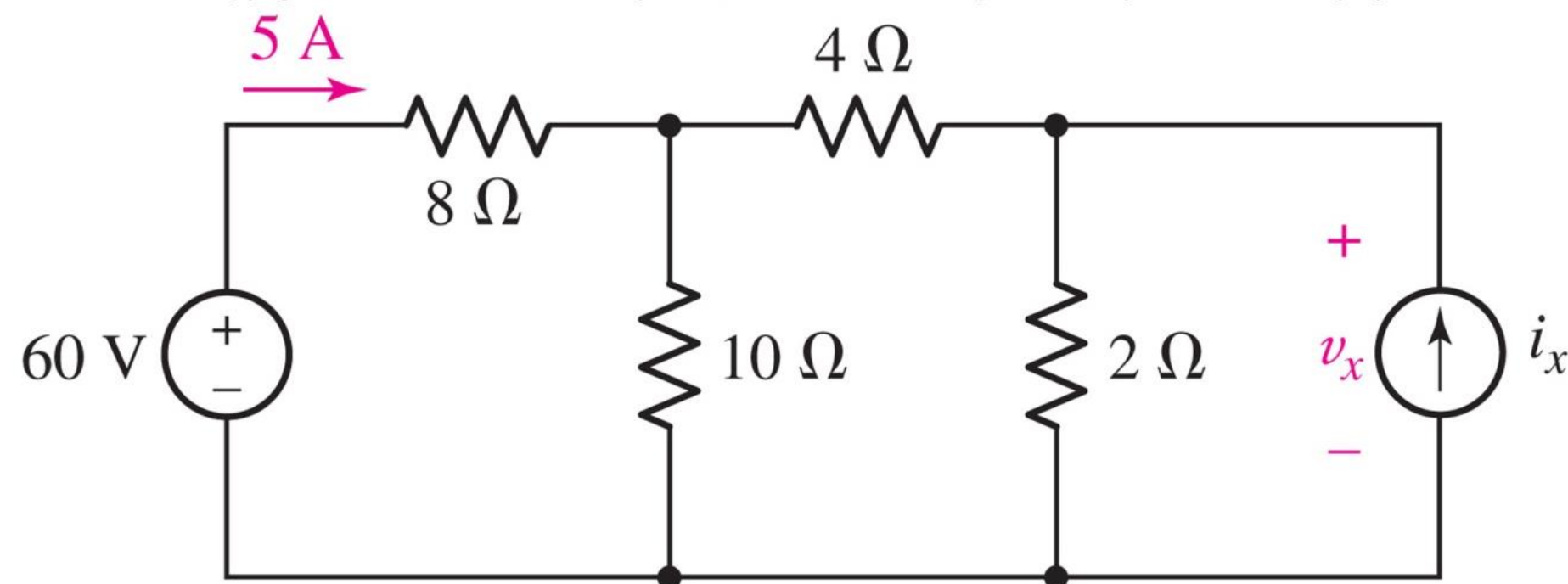Solve for the voltage  $v_x$  and the current  $i_x$


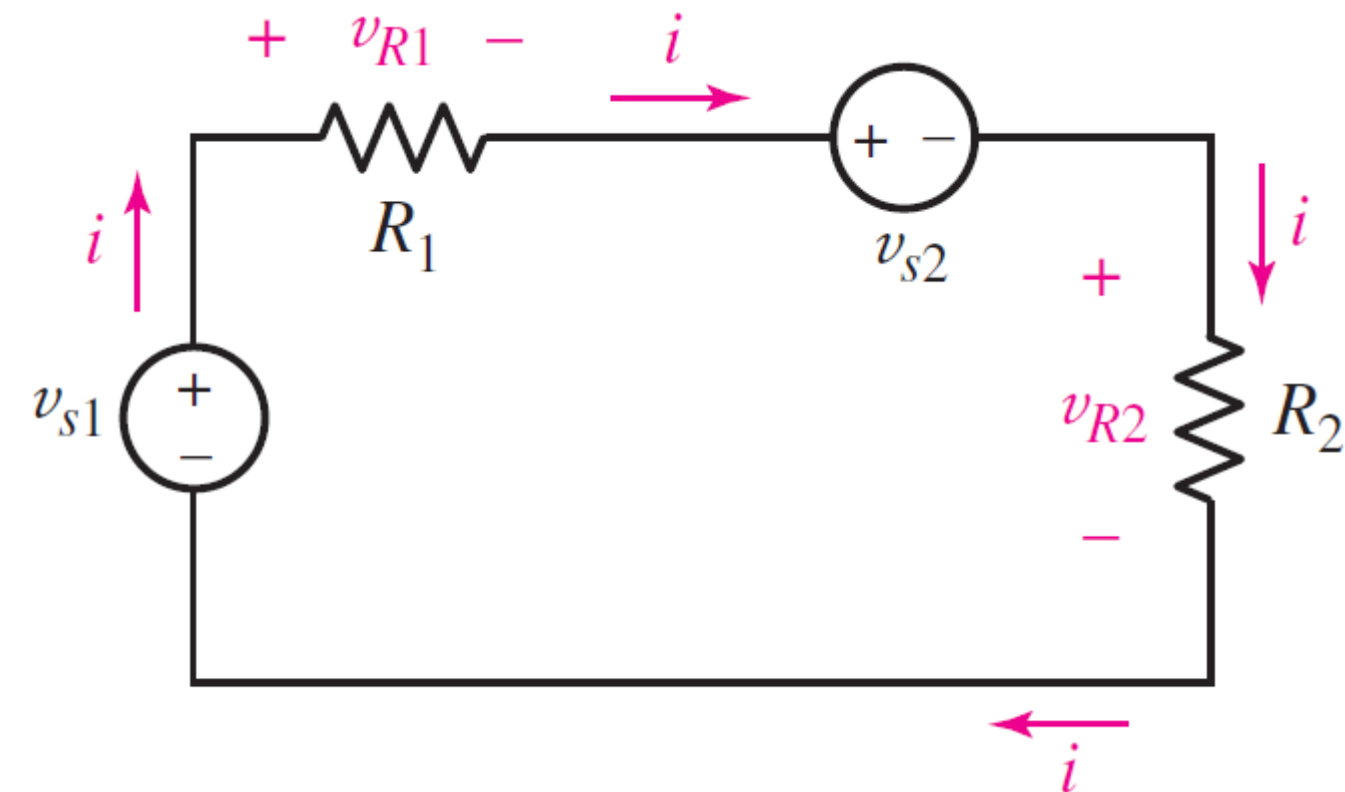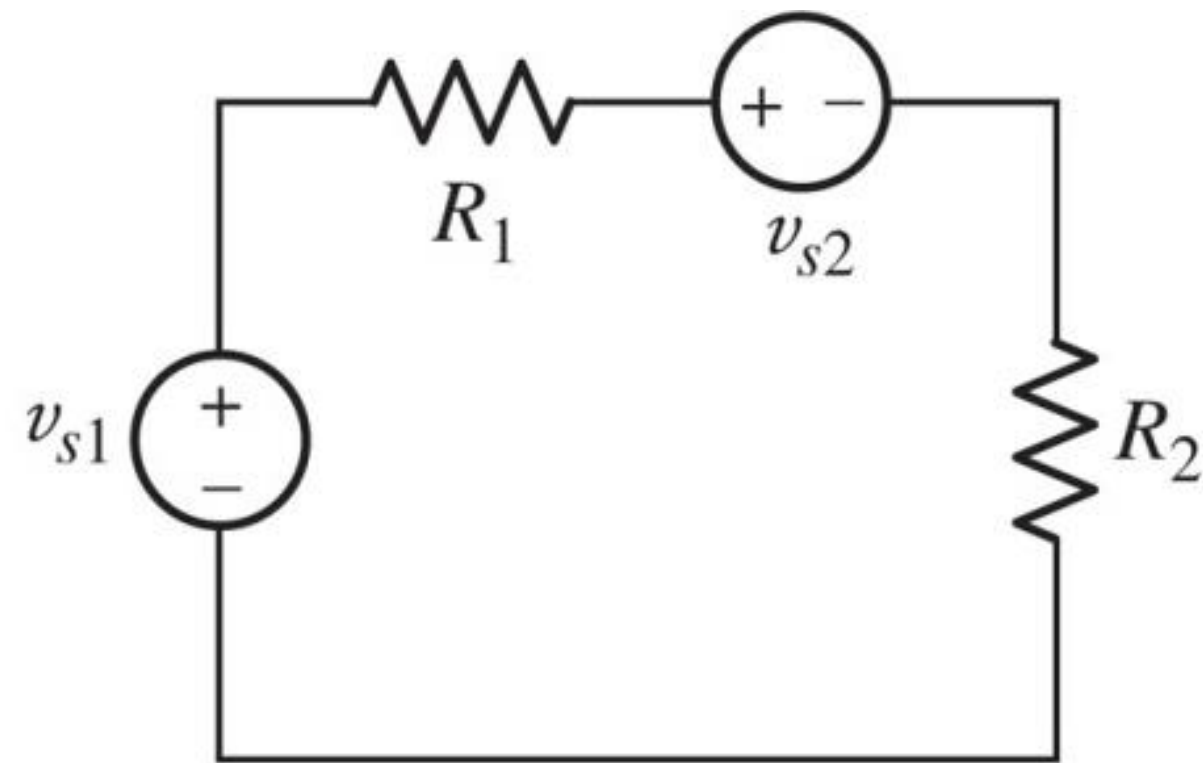
# Series Connections


- ❖ All of the elements in a circuit that carry **the same current** are said to be connected in **series**.





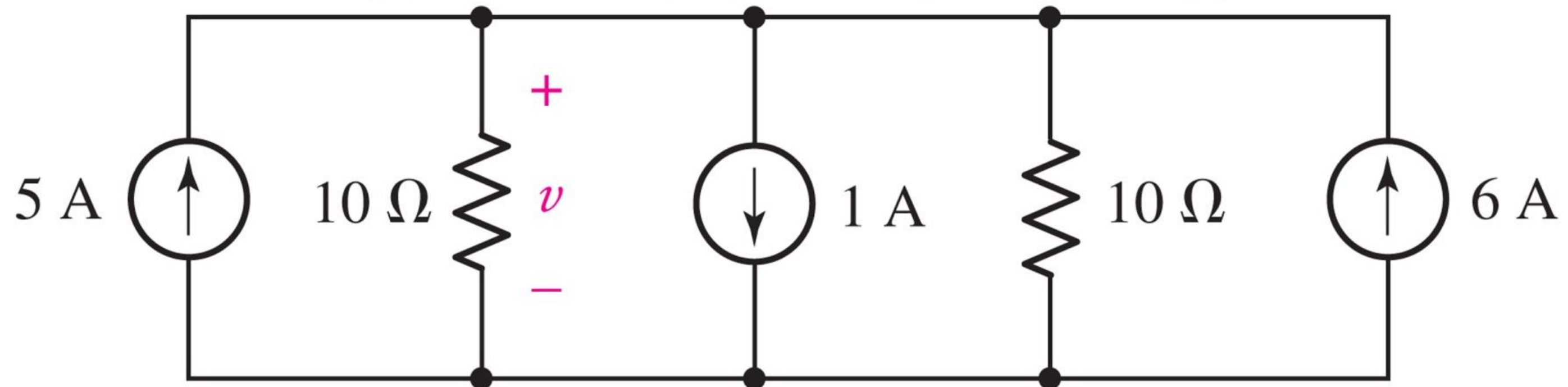
# Parallel Connections

❖ Elements in a circuit having a common voltage across them are said to be connected in *parallel*.



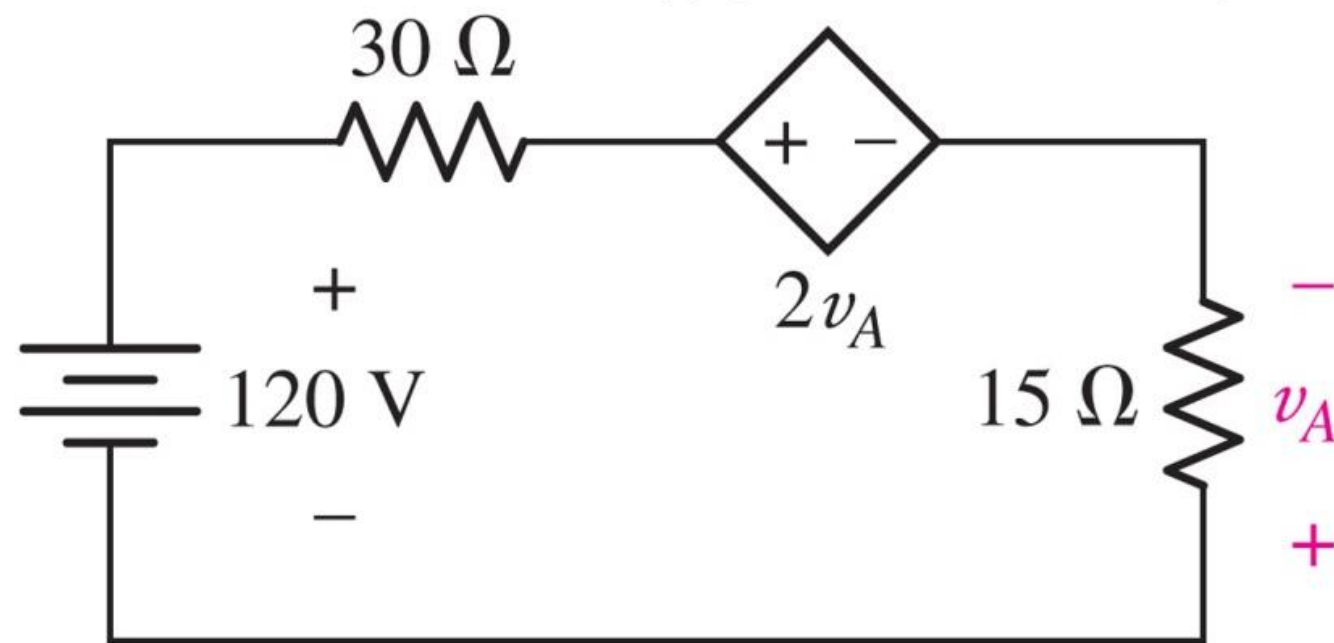
## Example: Single Loop Circuit

- Calculate the power absorbed by each circuit element.



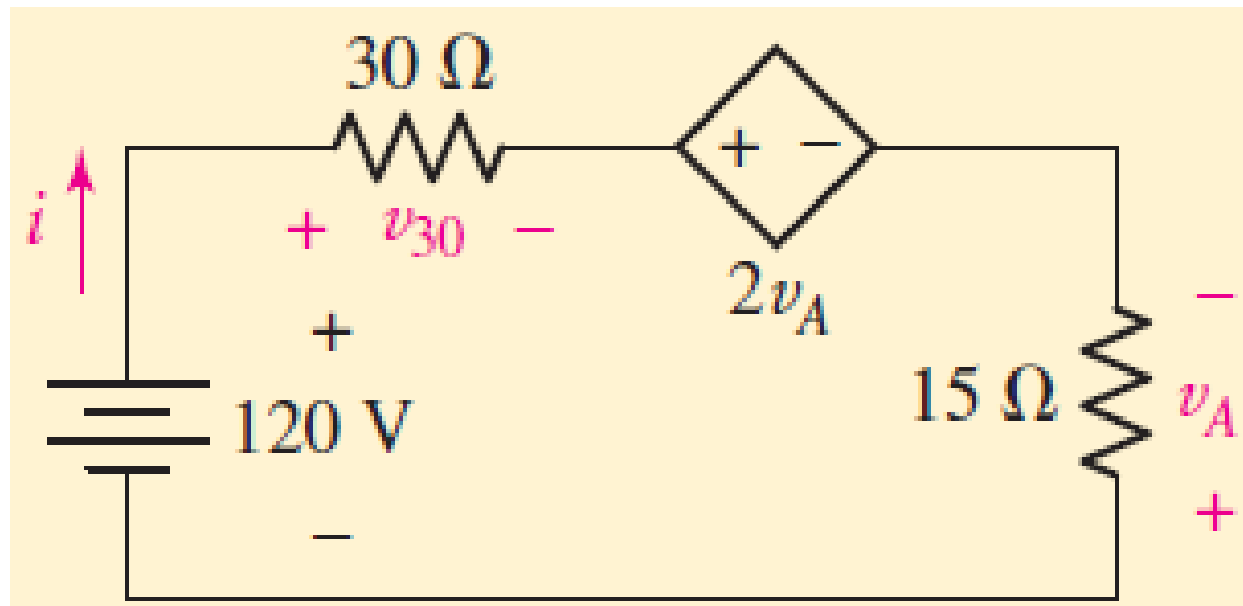
$$\begin{aligned} -120 + v_{30} + 2v_A - v_A &= 0 \\ v_{30} = 30i \quad \text{and} \quad v_A &= -15i \\ -120 + 30i - 30i + 15i &= 0 \\ i &= 8 \text{ A} \end{aligned}$$



$$\sum p_{\text{absorbed}} = \sum p_{\text{supplied}}$$
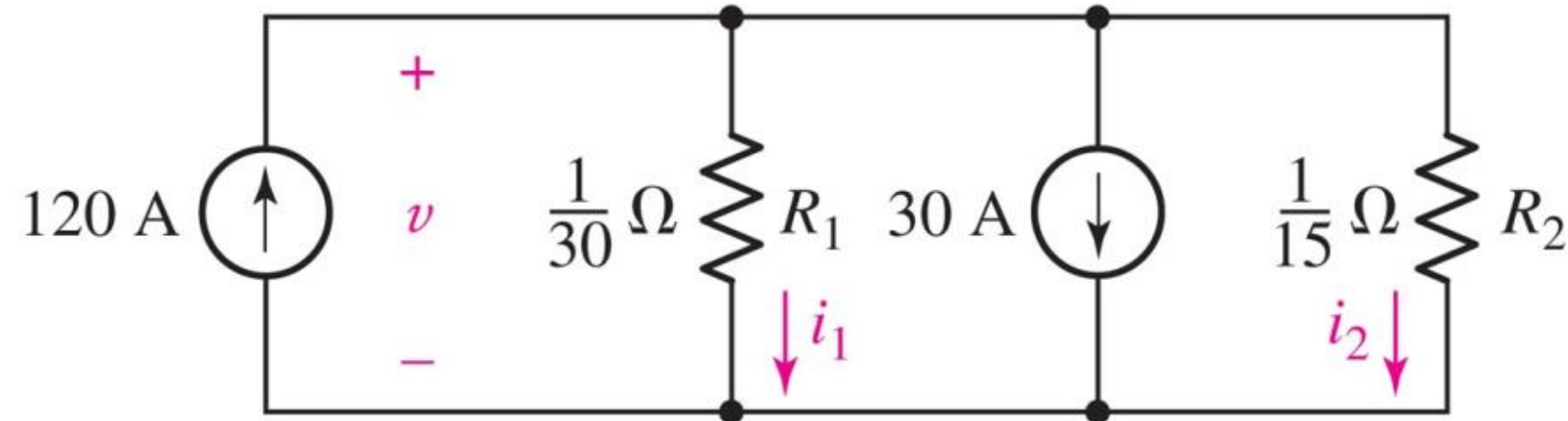
## Example: Single Node-Pair Circuit

Find the voltage  $v$  and the currents  $i_1$  and  $i_2$ .



$$-120 + i_1 + 30 + i_2 = 0$$

$$i_1 = 30v \quad \text{and} \quad i_2 = 15v$$


$$-120 + 30v + 30 + 15v = 0$$

$$v = 2 \text{ V}$$

$$i_1 = 60 \text{ A} \quad \text{and} \quad i_2 = 30 \text{ A}$$
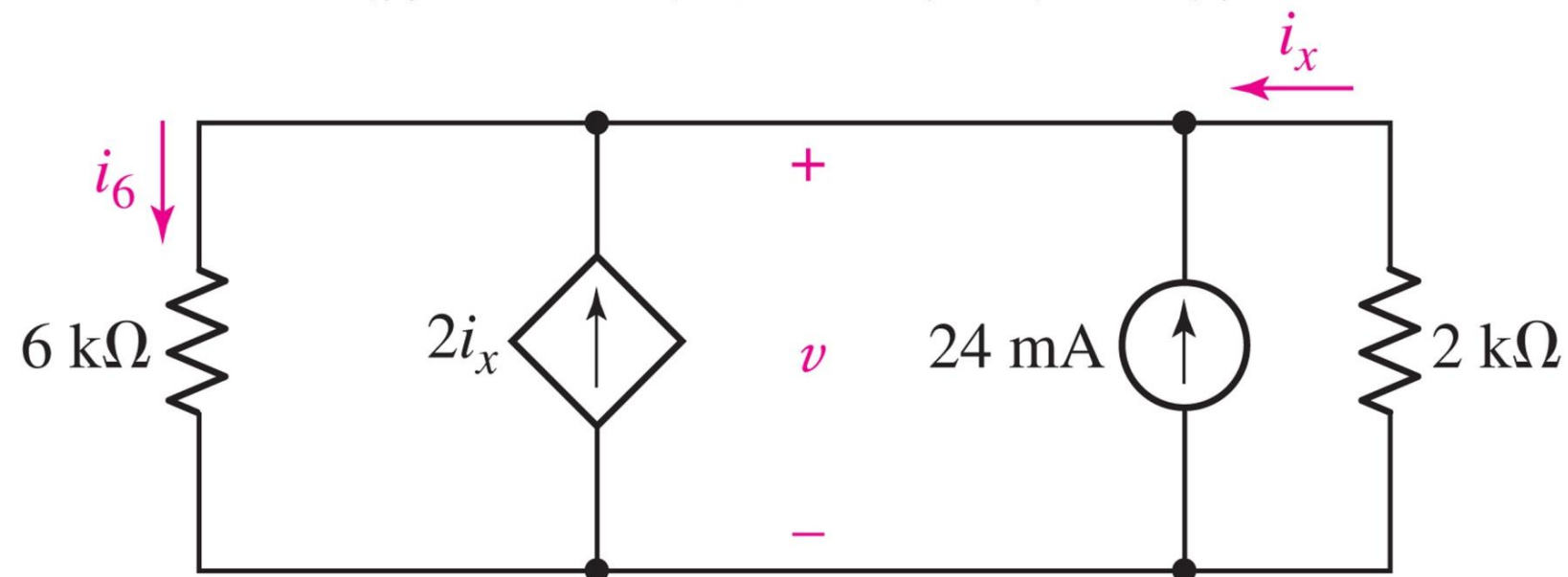
## Example: Single Node-Pair Circuit

Determine the value of  $v$  and the power supplied by the independent current source.



$$i_6 - 2i_x - 0.024 - i_x = 0$$

$$i_6 = \frac{v}{6000} \quad \text{and} \quad i_x = \frac{-v}{2000}$$


$$\frac{v}{6000} - 2\left(\frac{-v}{2000}\right) - 0.024 - \left(\frac{-v}{2000}\right) = 0$$

$$\text{and so } v = (600)(0.024) = 14.4 \text{ V.}$$

$$p_{24} = 14.4(0.024) = 0.3456 \text{ W (345.6 mW)}$$

## Example: Single Node-Pair Circuit

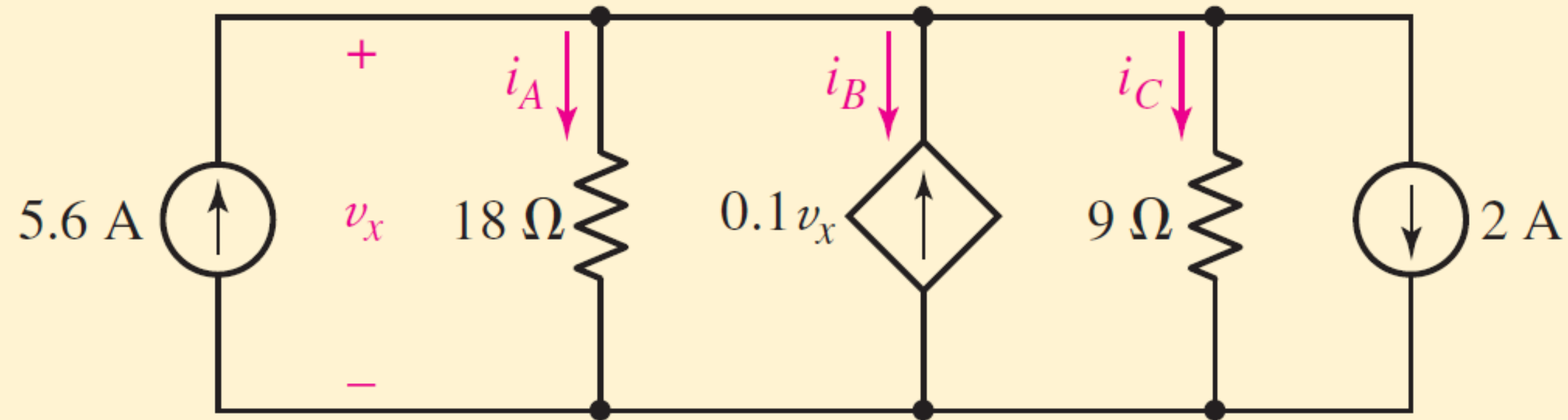
3.8 For the single-node-pair circuit of Fig. 3.18, find  $i_A$ ,  $i_B$ , and  $i_C$ .




■ **FIGURE 3.18**

Ans: 3 A;  $-5.4$  A; 6 A.

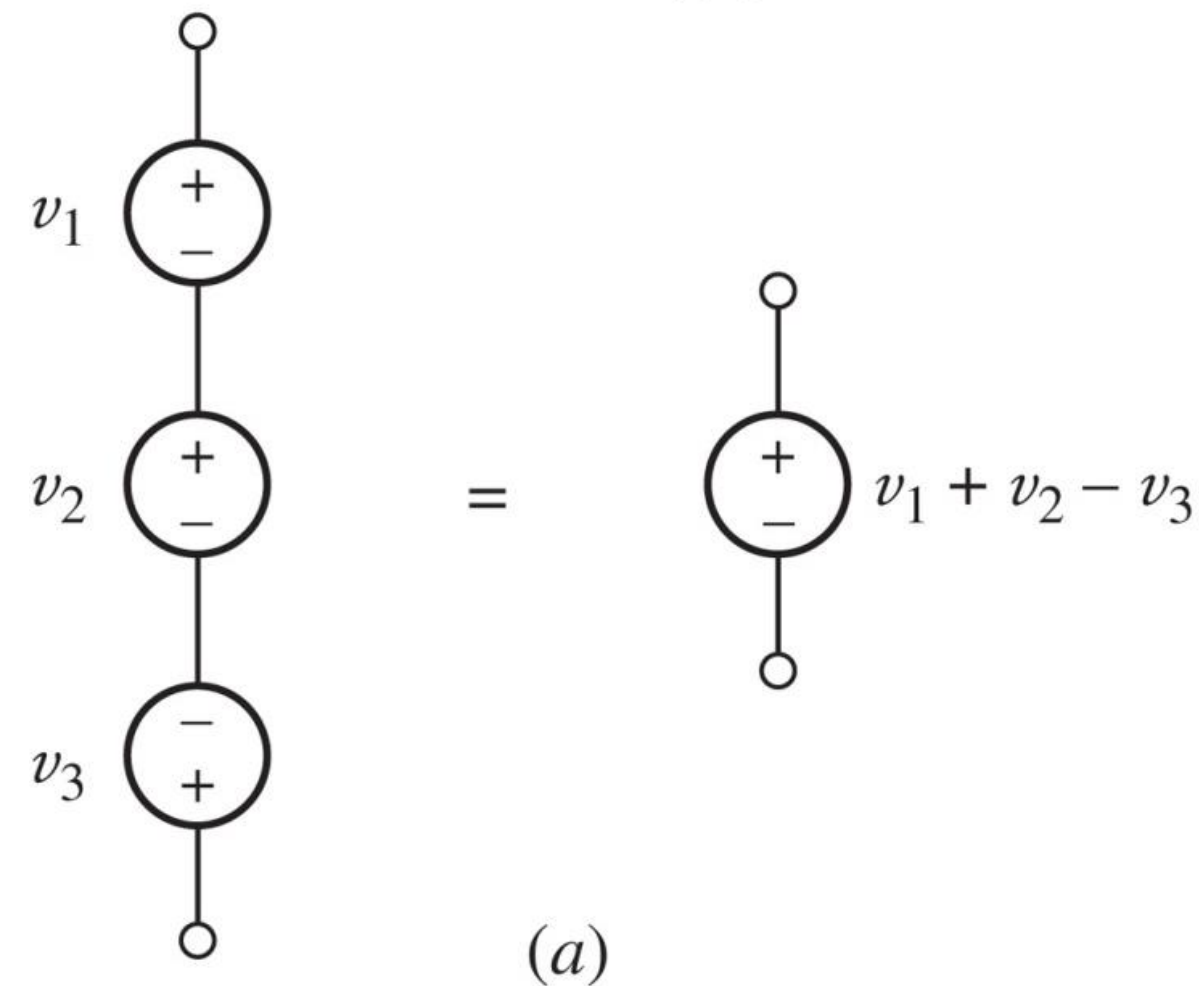
Voltage sources connected in series can be combined into an equivalent voltage source:



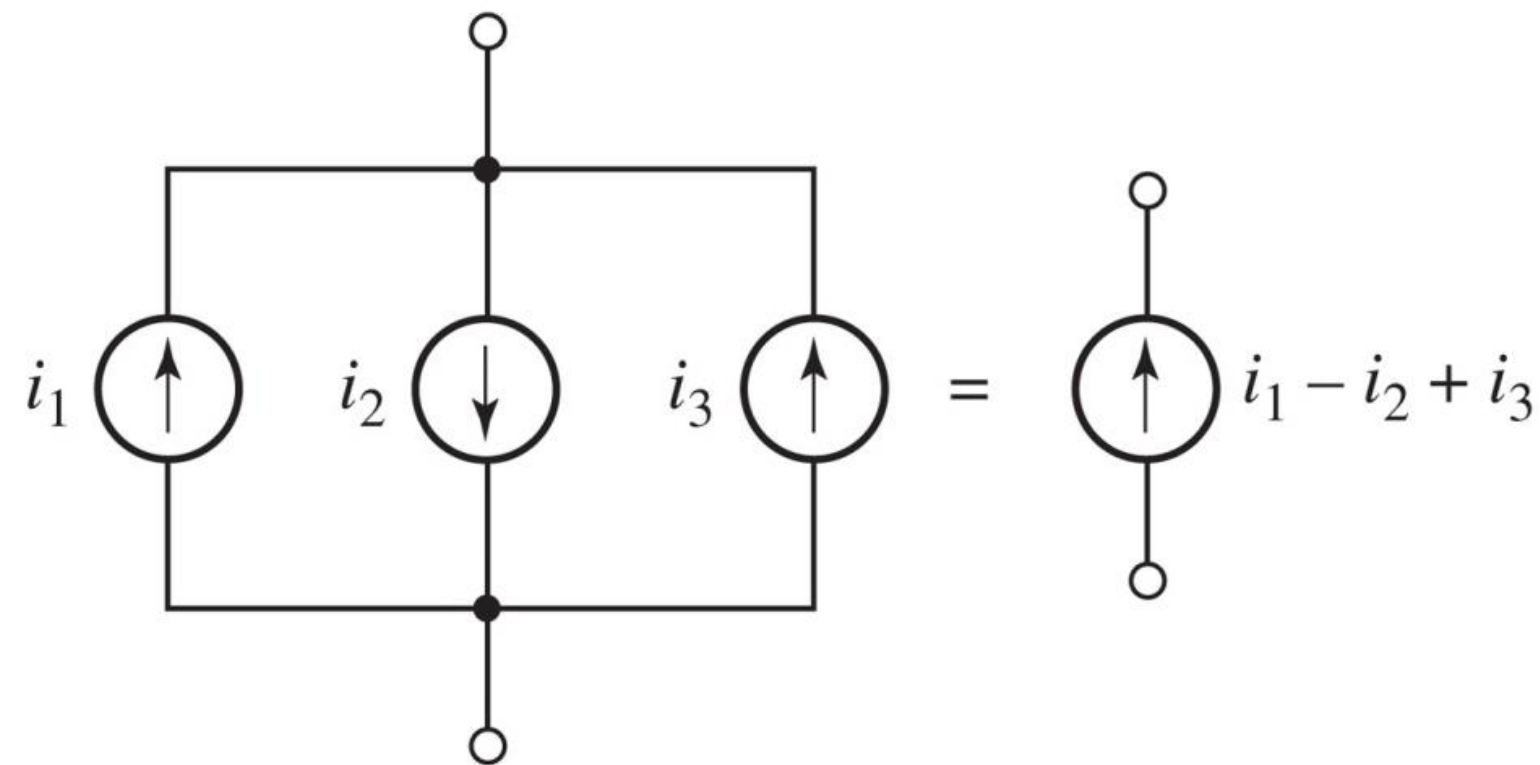Current sources connected in parallel can be combined into an equivalent current source:



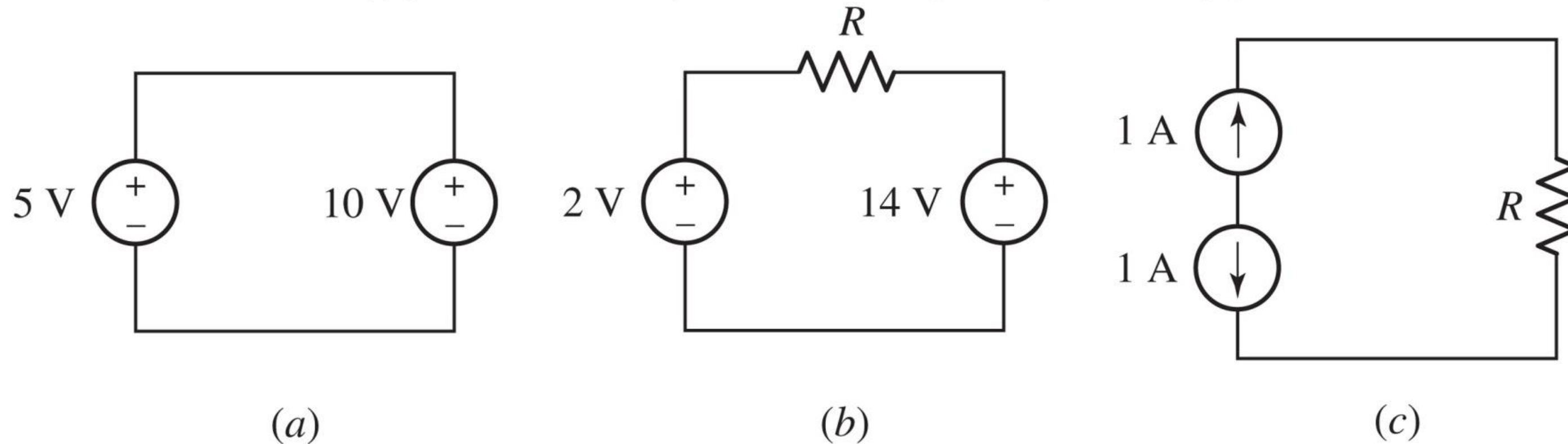
- Our circuit models are idealizations that can lead to apparent physical absurdities:



- $V_s$  in parallel (a) and  $I_s$  in series (c) can lead to “impossible circuits”



# Resistors in Series

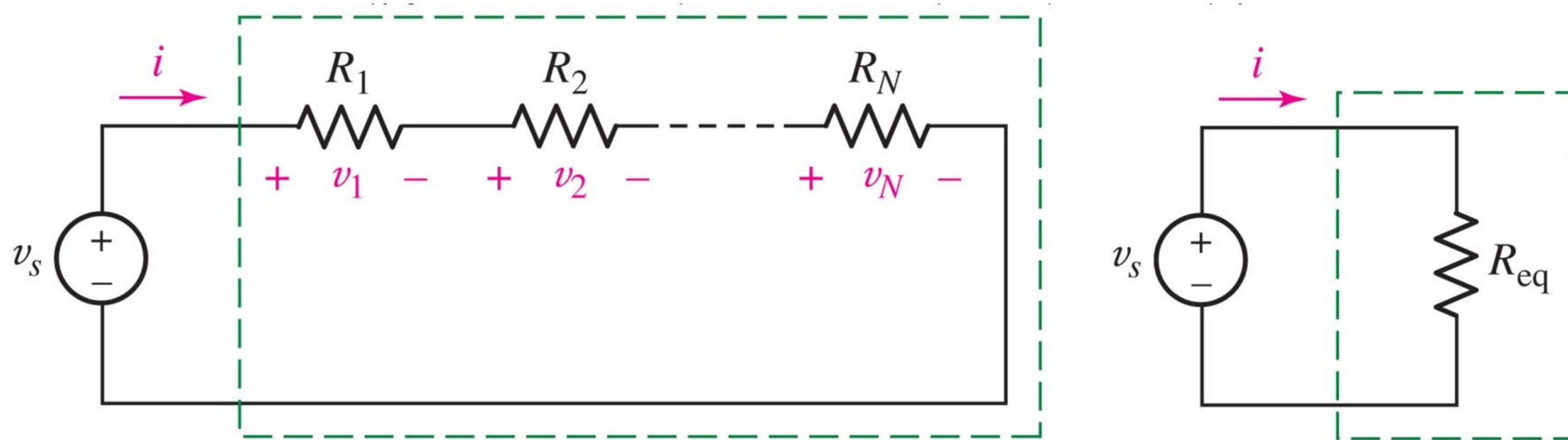


Using KVL shows:



$$R_{eq} = R_1 + R_2 + \dots + R_N$$
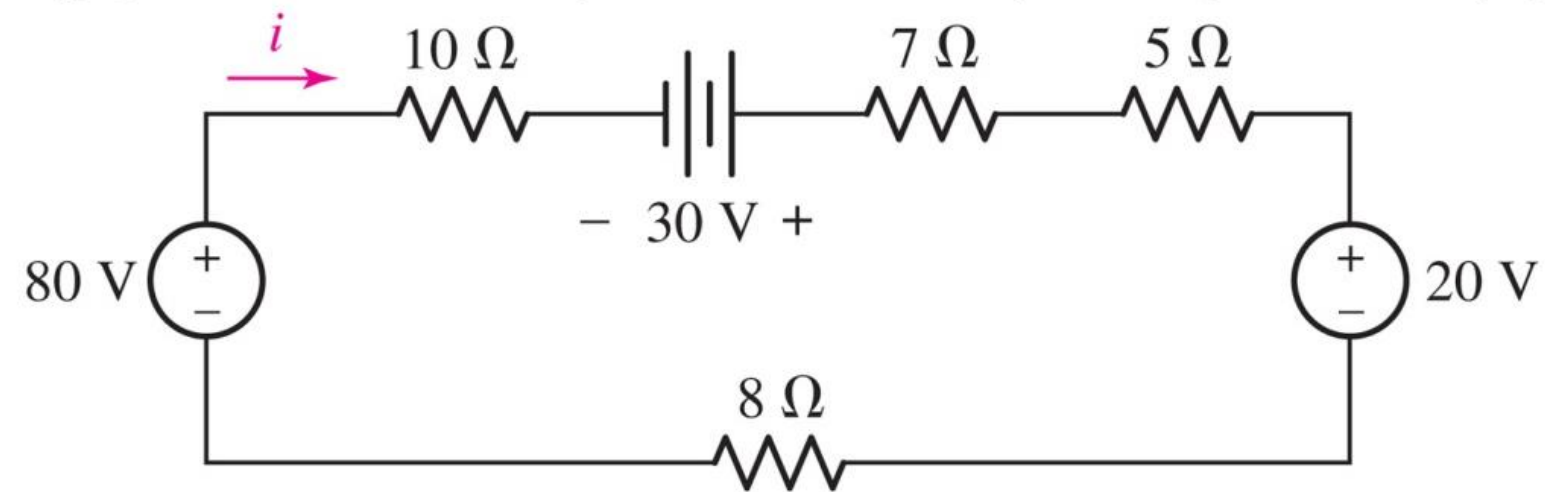
## Example: Circuit Simplifying



Find  $i$  and the power supplied by the 80 V source.



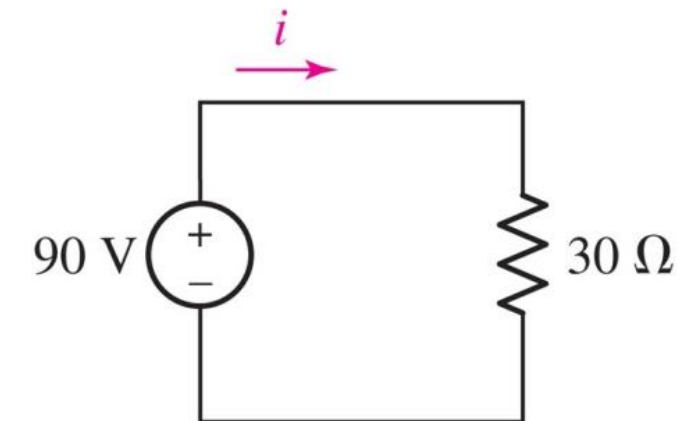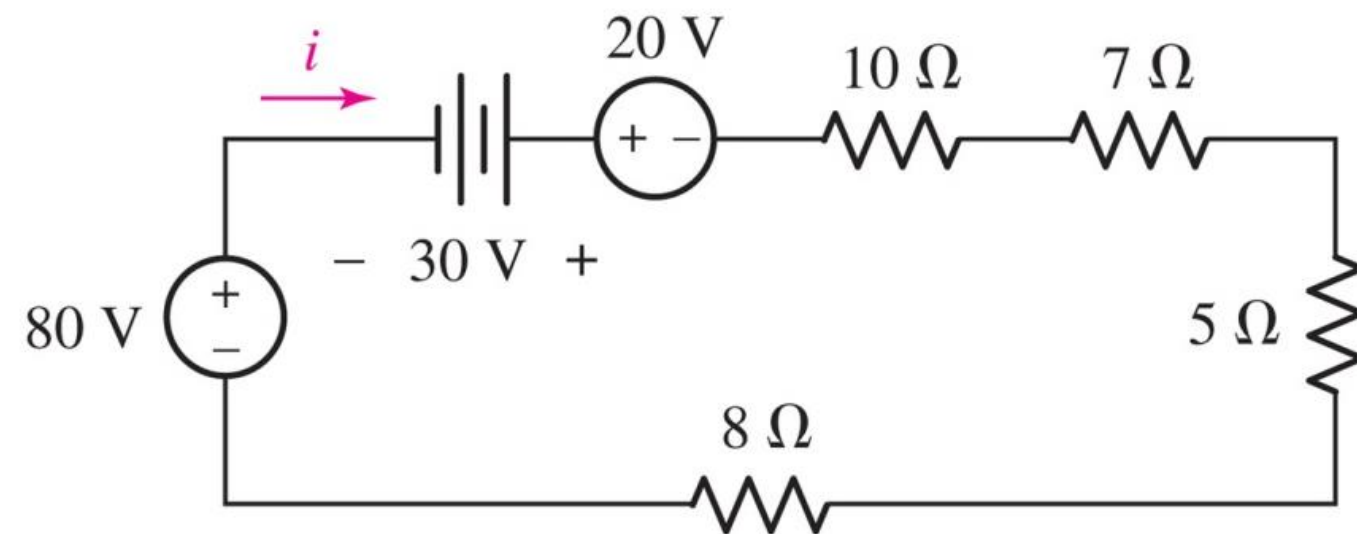Answer:  $i = 3\text{ A}$  and  $p = 240\text{ W}$  supplied



# Resistors in Parallel

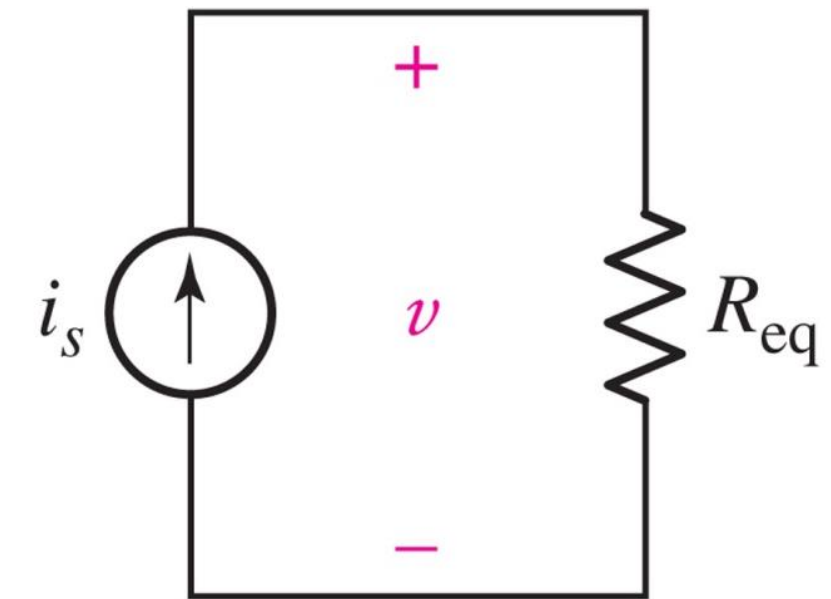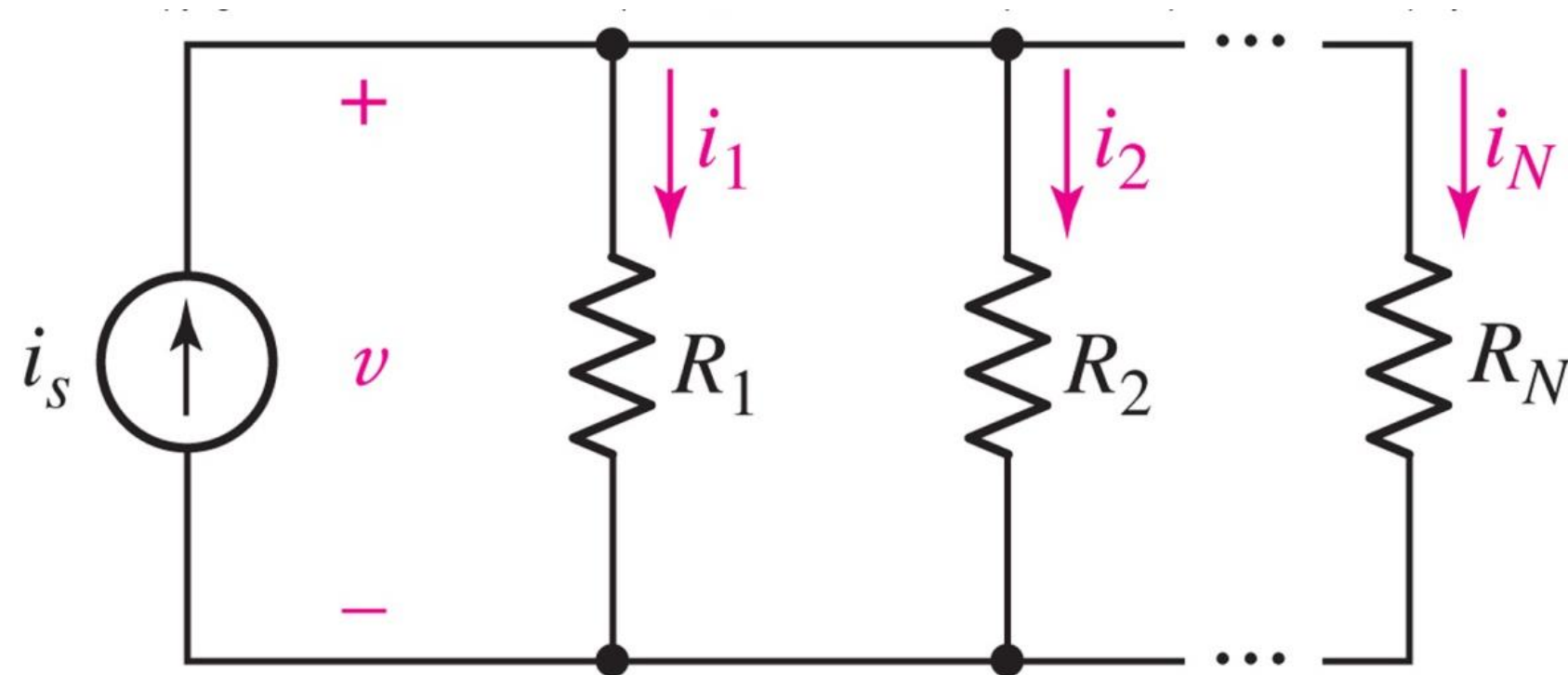

Using KCL shows:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

# Two Resistors in Parallel


Two resistors in parallel can be combined using the shortcut.

**product / sum**





$$R_{eq} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

# Example

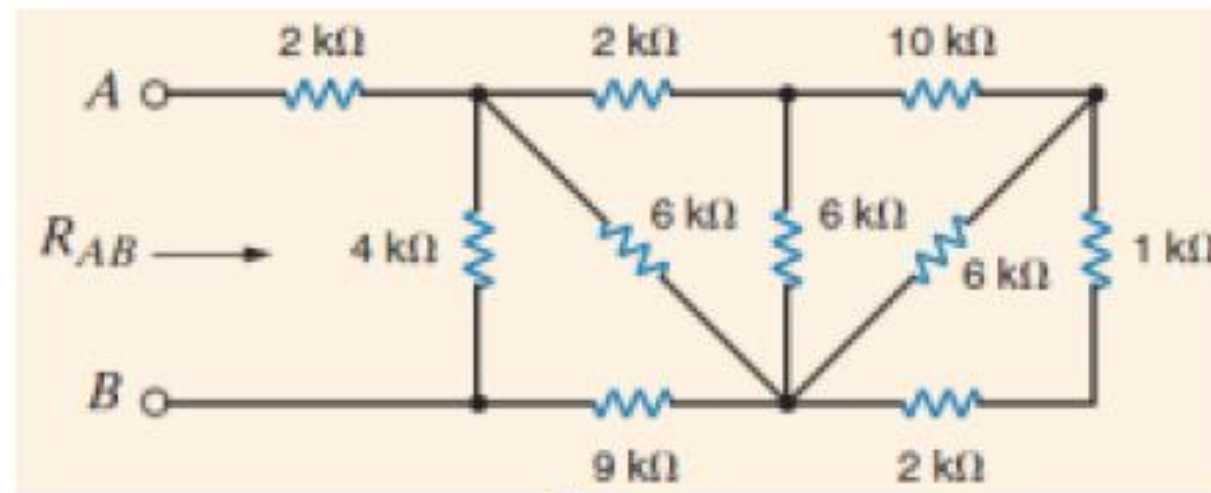


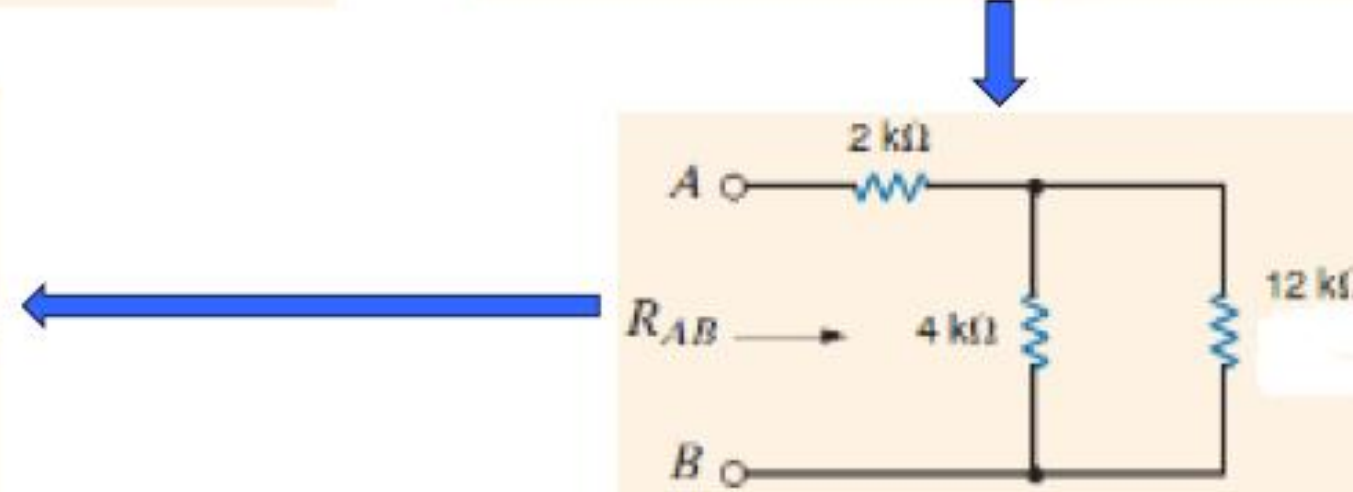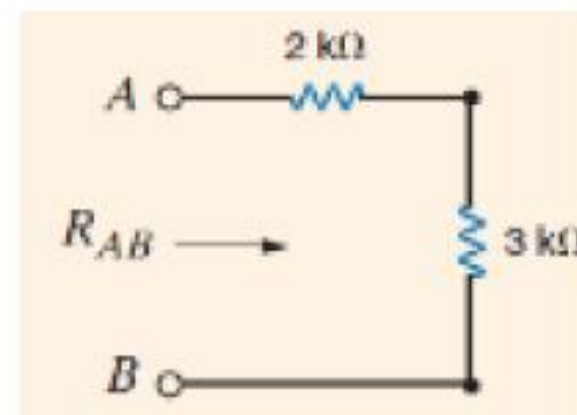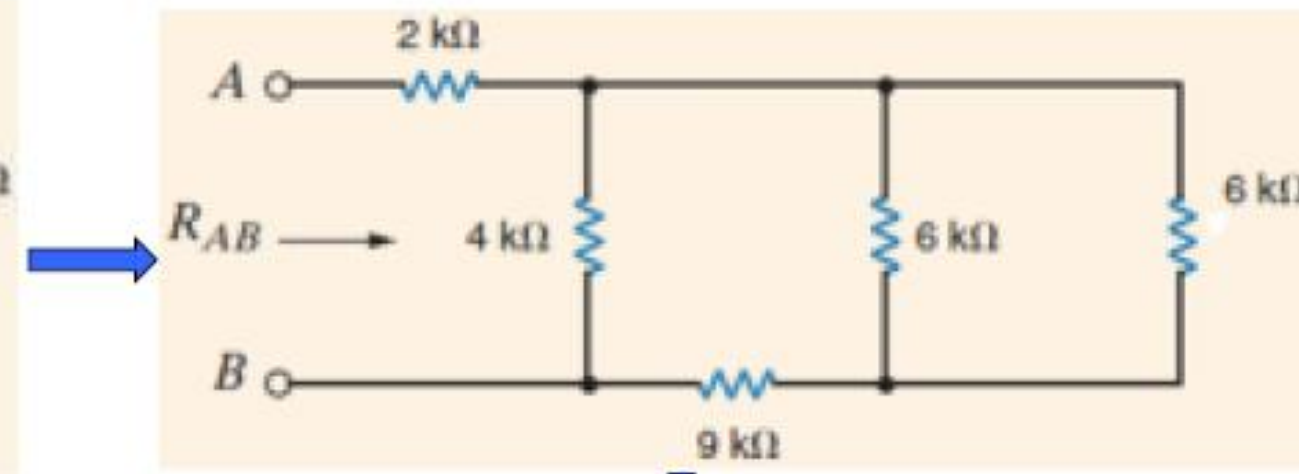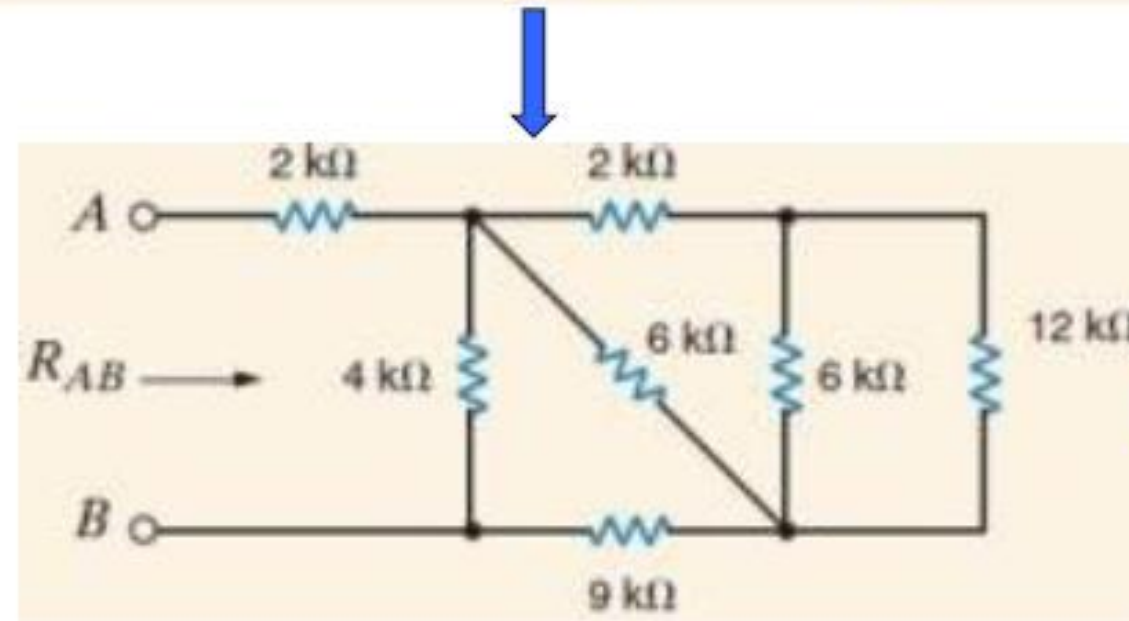- $R_{AB} = ?$
- $R_{AB} = 5 \text{ k}\Omega$


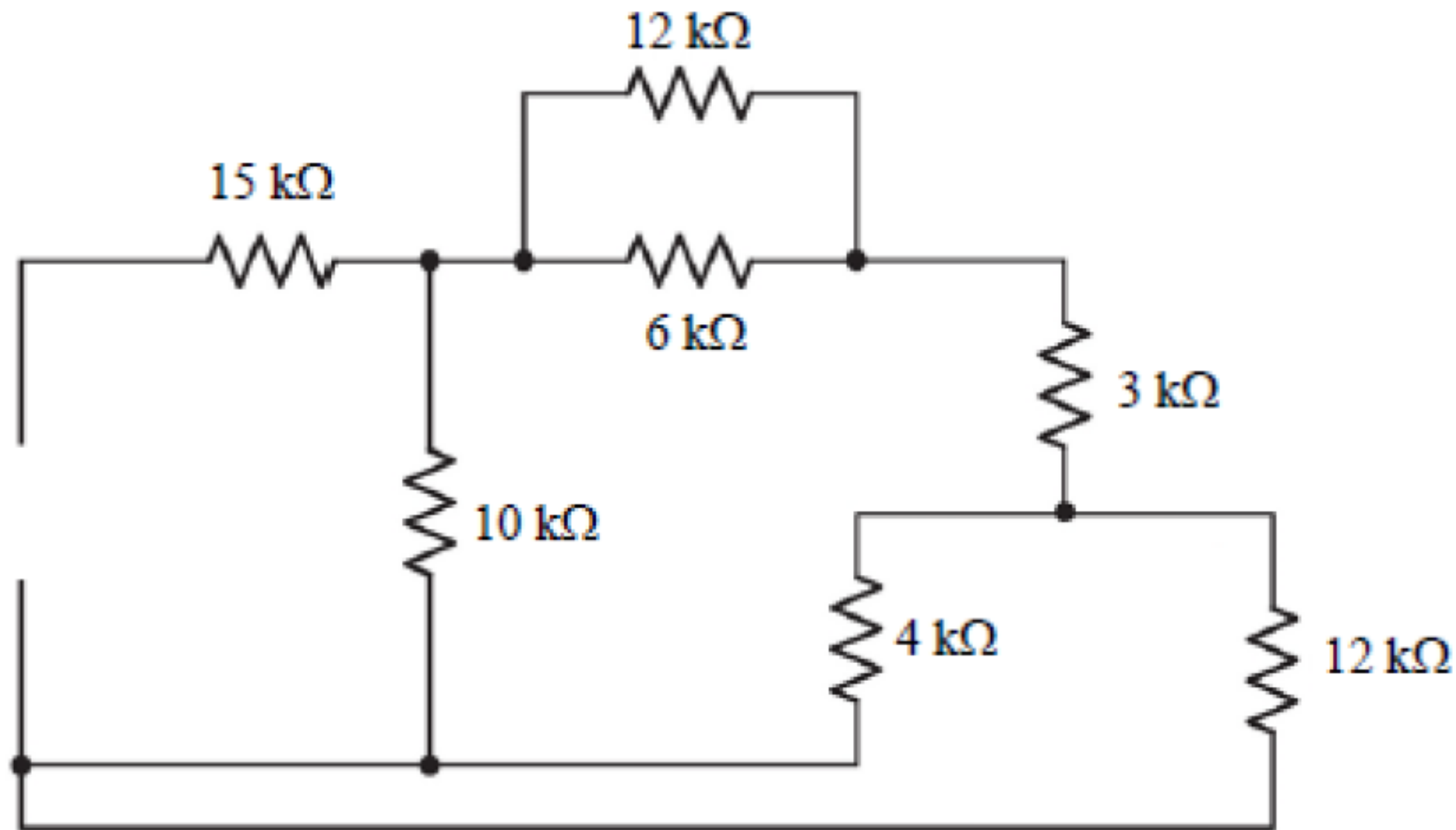
## Example




- Determine the equivalent resistance of this network between the open-circuit terminals.



- 20 kΩ
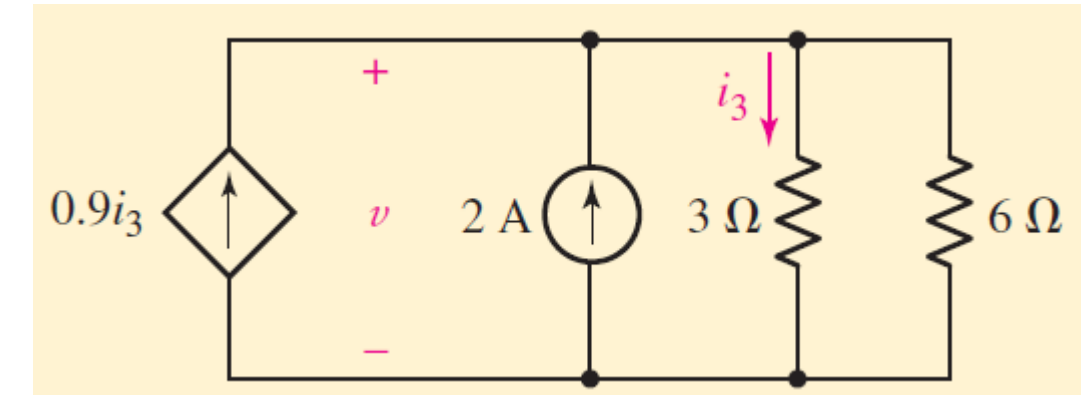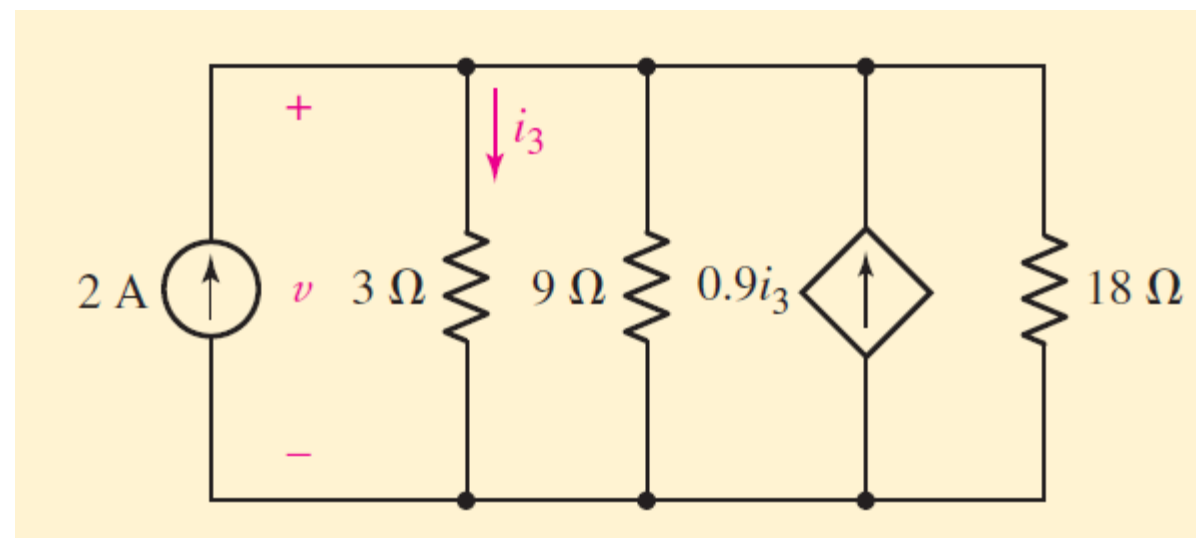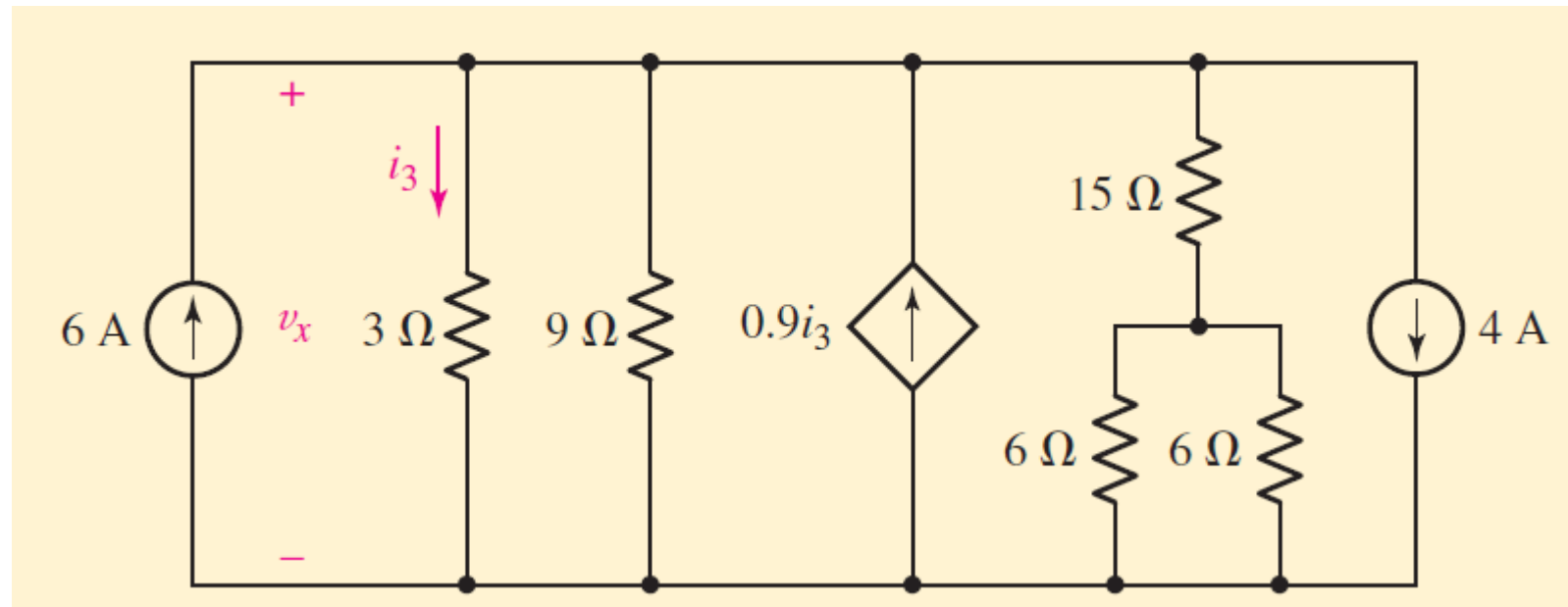
# Example

Calculate the power and voltage of the dependent source



$$-0.9i_3 - 2 + i_3 + \frac{v}{6} = 0$$

$$v = 3i_3$$

$$i_3 = \frac{10}{3} \text{ A}$$


$$v = 3i_3 = 10 \text{ V}$$

$$v \times 0.9i_3 = 10(0.9)(10/3) = 30 \text{ W}$$


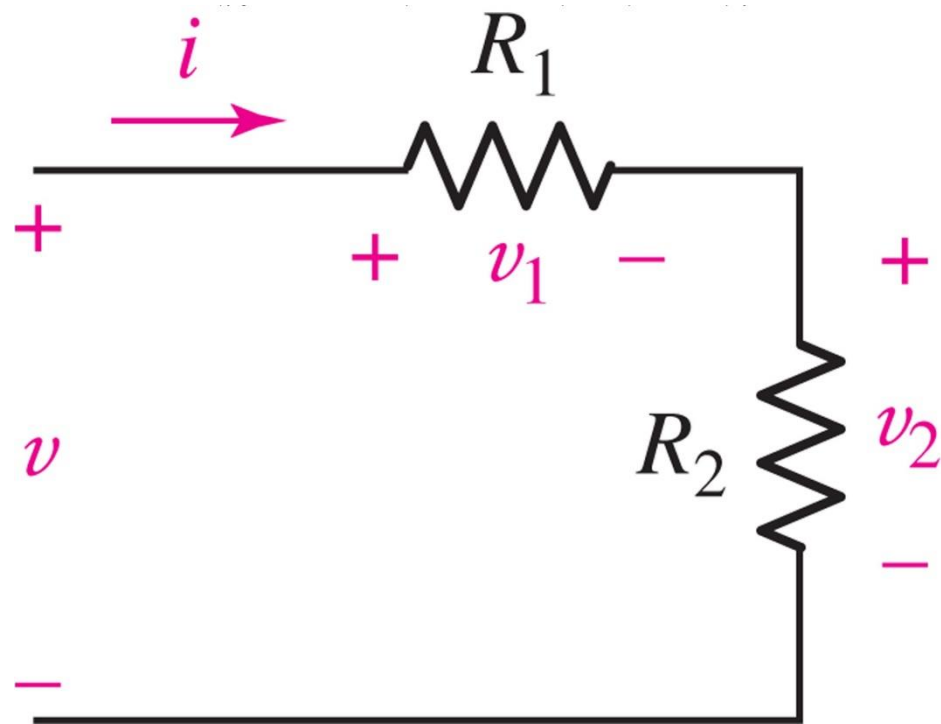
# Voltage Division

Resistors in series “share” the voltage applied to them.



$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$



$$v_k = \frac{R_k}{R_1 + R_2 + \dots + R_N} v$$


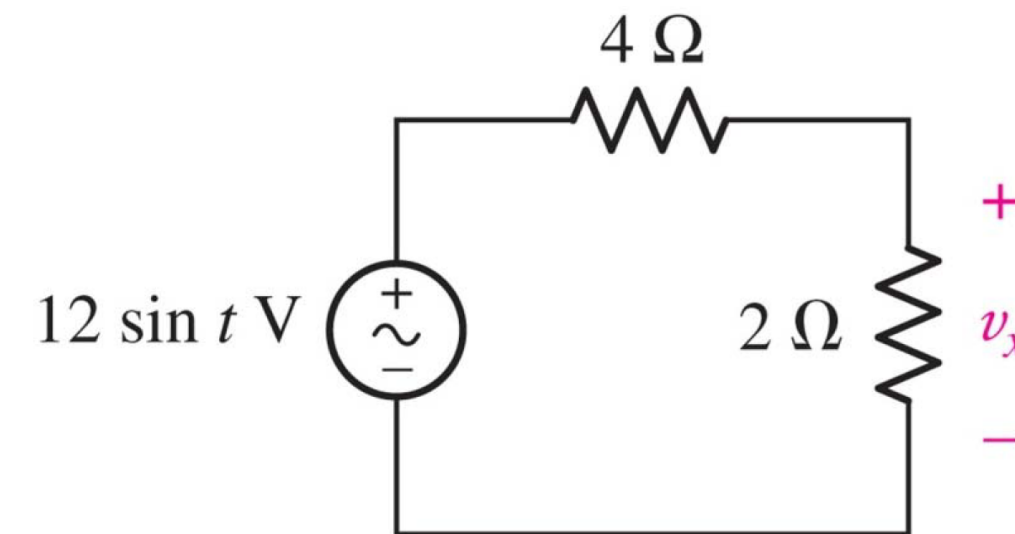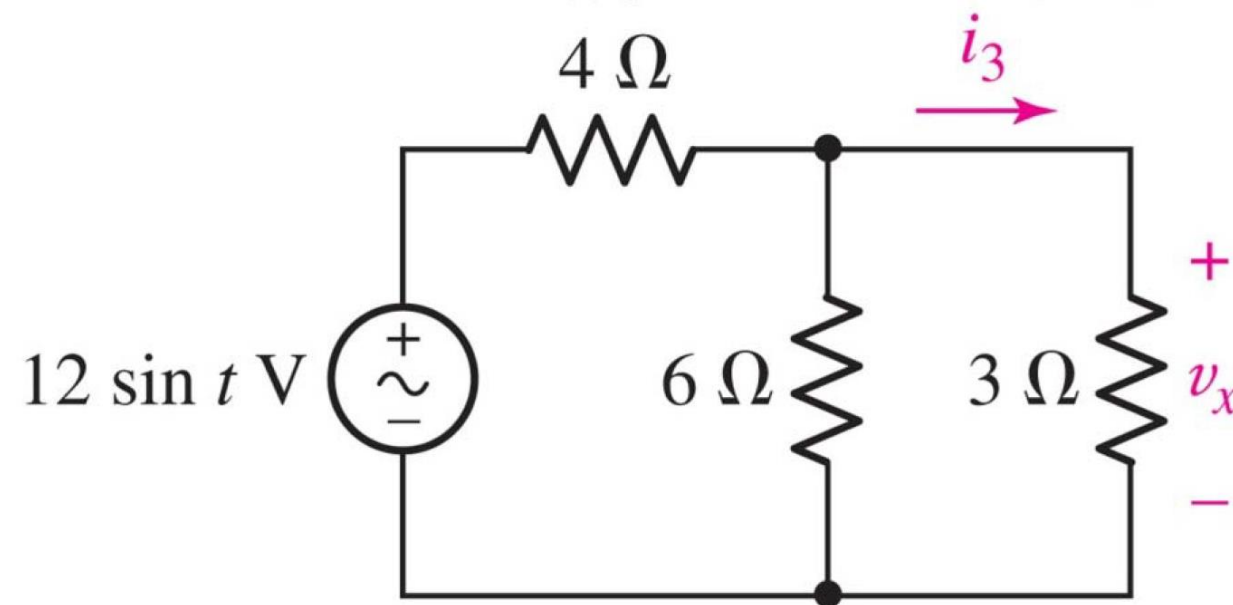
# Example: Voltage Division

Find  $v_x$


We first combine the  $6\ \Omega$  and  $3\ \Omega$  resistors, replacing them with  $(6)(3)/(6 + 3) = 2\ \Omega$ .



$$v_x = (12 \sin t) \frac{2}{4 + 2} = 4 \sin t \quad \text{volts}$$
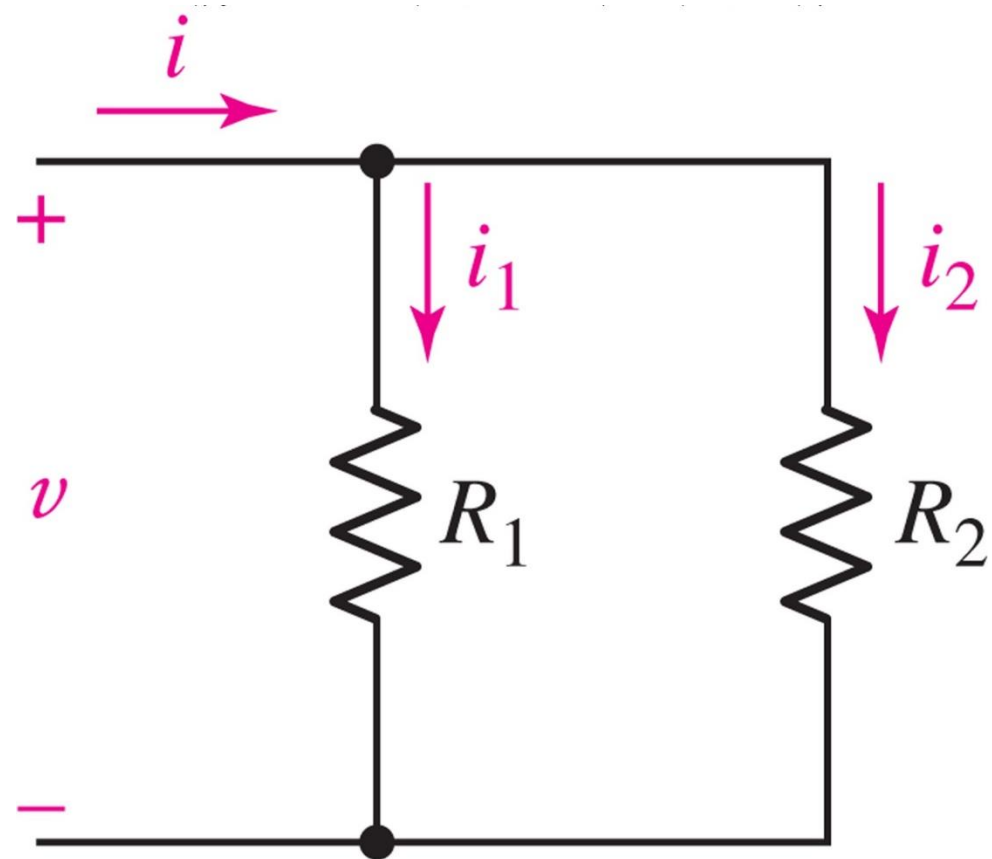
# Current Division

Resistors in parallel “share” the current through them.




$$i_1 = i \frac{R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

$$i_k = i \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

## Example: Current Division

Find  $i_3(t)$

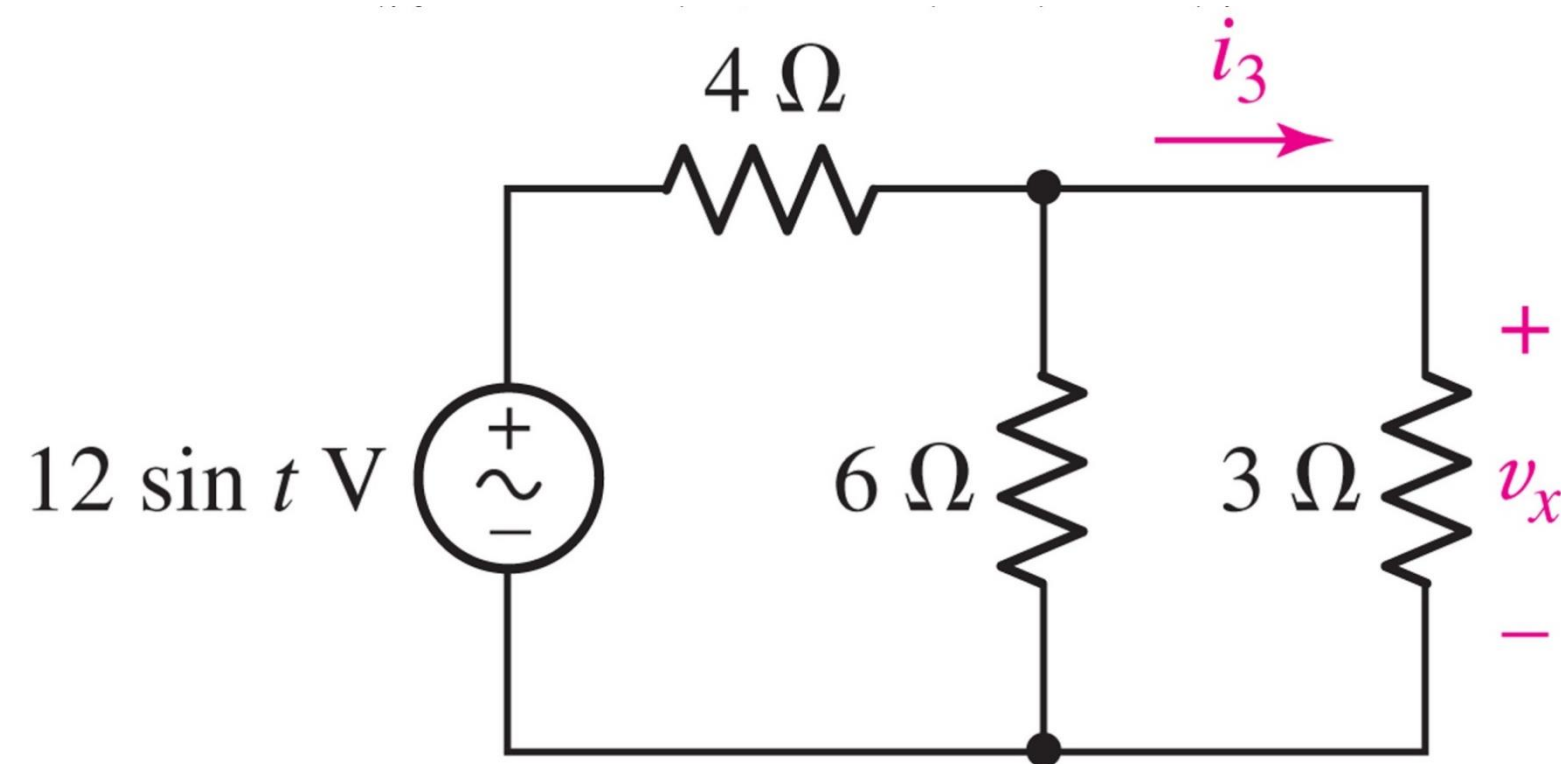

$$i(t) = \frac{12 \sin t}{4 + 3 \parallel 6} = \frac{12 \sin t}{4 + 2} = 2 \sin t \quad \text{A}$$


$$i_3(t) = (2 \sin t) \left( \frac{6}{6 + 3} \right) = \frac{4}{3} \sin t \quad \text{A}$$

- ❑ ***KCL***: the algebraic sum of the **currents entering any node is zero**.
- ❑ ***KVL***: the algebraic **sum of the voltages** around any closed path in a circuit is zero
- ❑ All elements in a circuit **that carry the same current** are said to be connected in ***series***.
- ❑ Elements in a circuit having **a common voltage across them** are said to be connected in ***parallel***.
- ❑ **Voltage sources** in series can be replaced by a single source.
- ❑ **Current sources** in parallel can be replaced by a single source.

- ❑ A series combination of  $N$  resistors can be replaced by a single resistor having the value  $R_{eq} = R1 + R2 + \dots + RN$ .
- ❑ A parallel combination of  $N$  resistors can be replaced by a single resistor having the value  $1/R_{eq} = 1/R1 + 1/R2 + \dots + 1/RN$
- ❑ **Voltage division** allows us to calculate what fraction of the total voltage across a **series string of resistors** is dropped across any one resistor (or group of resistors).
- ❑ **Current division** allows us to calculate what fraction of the total current into a **parallel string of resistors** flows through any one of the resistors.

# Practice 1


find  $i_1$ ,  $i_2$ , and  $v_3$ .

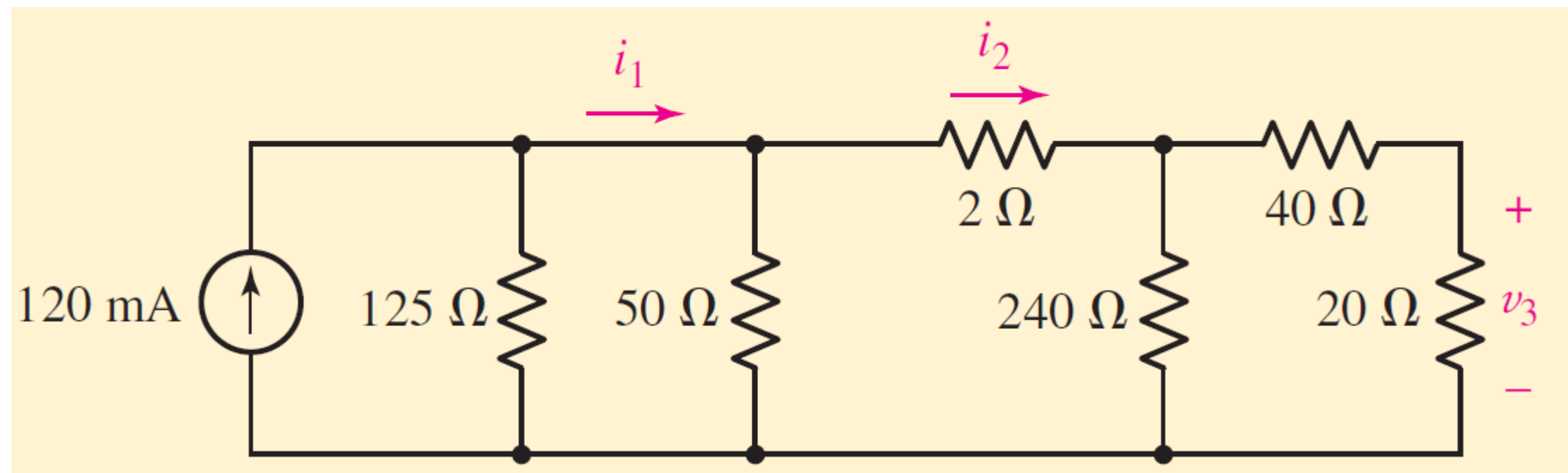

Ans: 100 mA; 50 mA; 0.8 V.
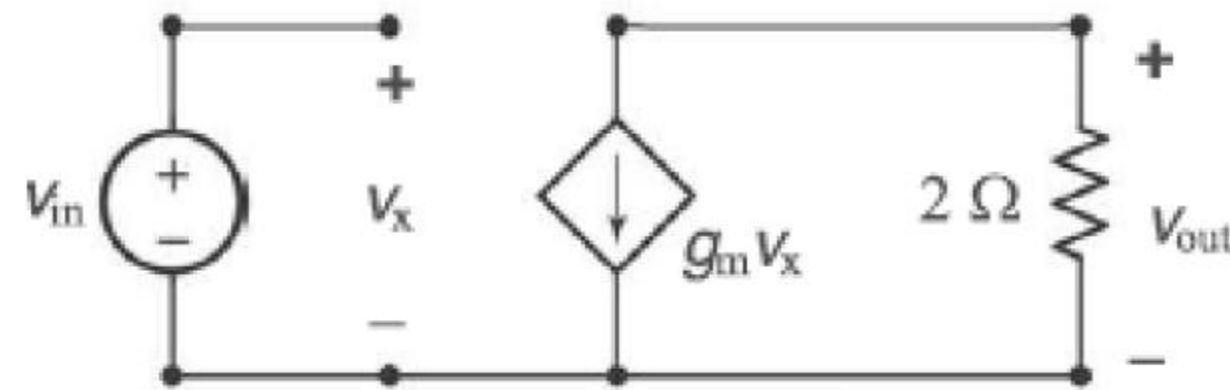
## Practice 2

In the circuit below,  $v_{in}=3\sin(\omega t)$  mV and  $g_m=10$  A/V.  
Determine  $v_{out}$ .




$$v_{out} = -g_m v_x \times R$$

$$v_{out} = -10 \times 3\sin(\omega t) \times 2$$

$$v_{out} = -60\sin(\omega t) \text{ mV}$$
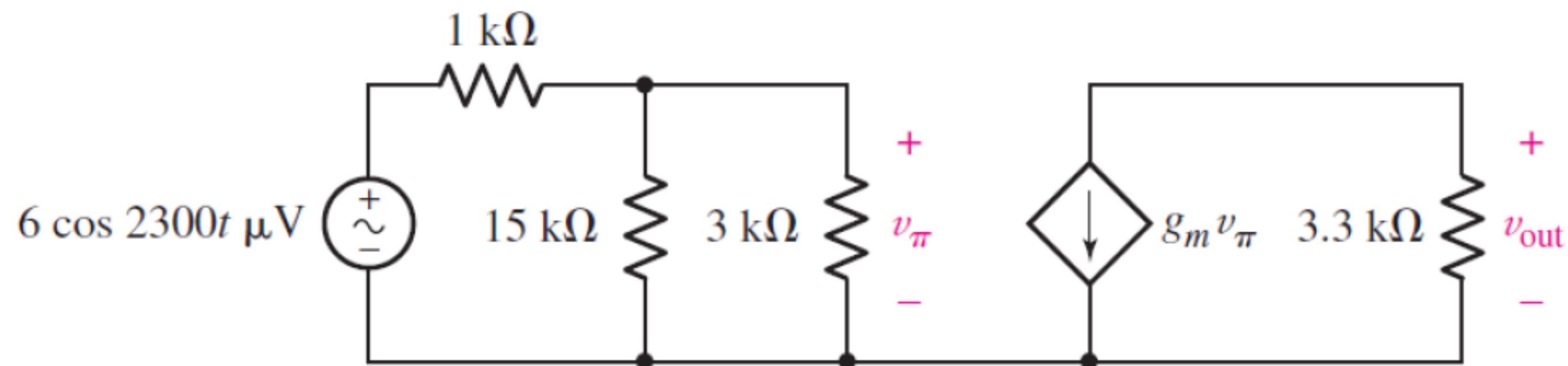
## Practice 2

Calculate the amplifier output  $v_{out}$  if the transconductance  $g_m$  is equal to 322 mS.







# Thanks

---